

# ENG PHYS 2A04 Tutorial 2

---

Electricity and Magnetism

# Your TAs today

- Tommy Kean

[keant1@mcmaster.ca](mailto:keant1@mcmaster.ca)

- Muhammad Munir


[munirm6@mcmaster.ca](mailto:munirm6@mcmaster.ca)

# Chapter 28: DC Circuits


## (Serway, 9<sup>th</sup> edition)
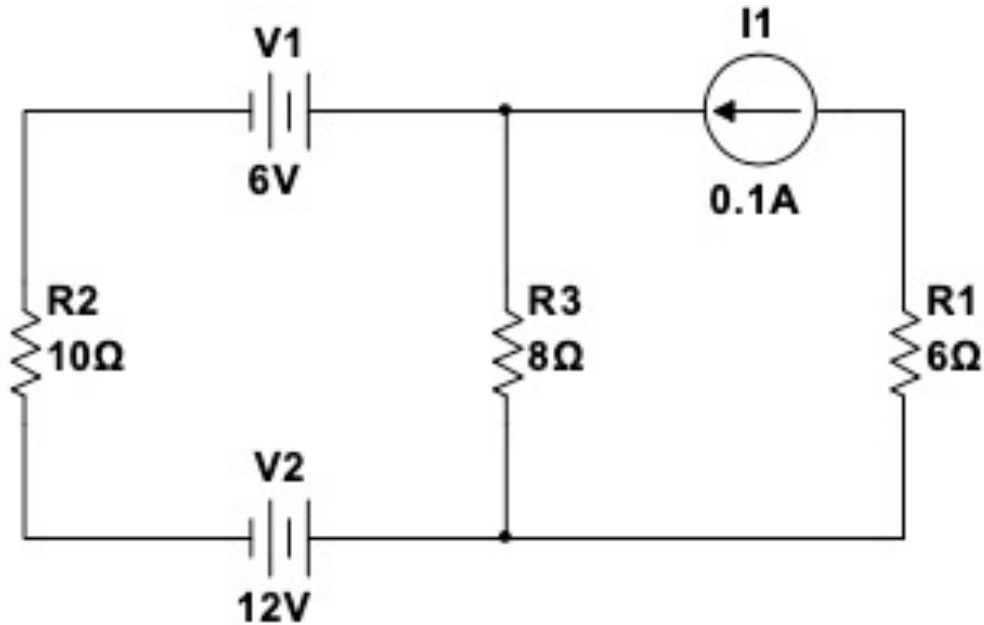
# Problem 1 Example in Lecture

Find the current across  $R_1$ ,  $R_2$  and  $R_3$




## Example in Lecture

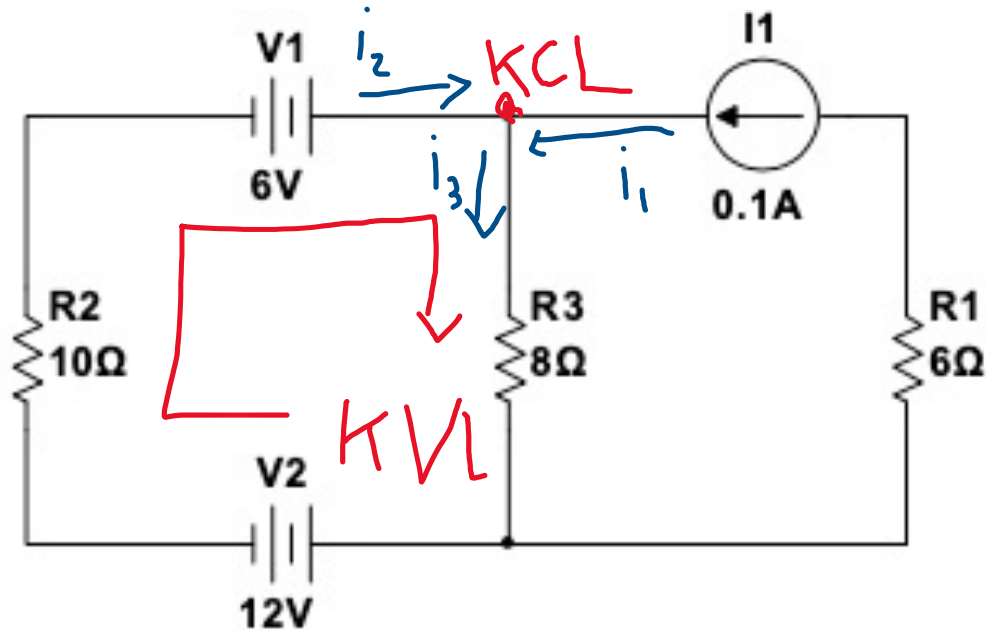

# Example in Lecture


Step 1 - Loop Rule (KCL) :

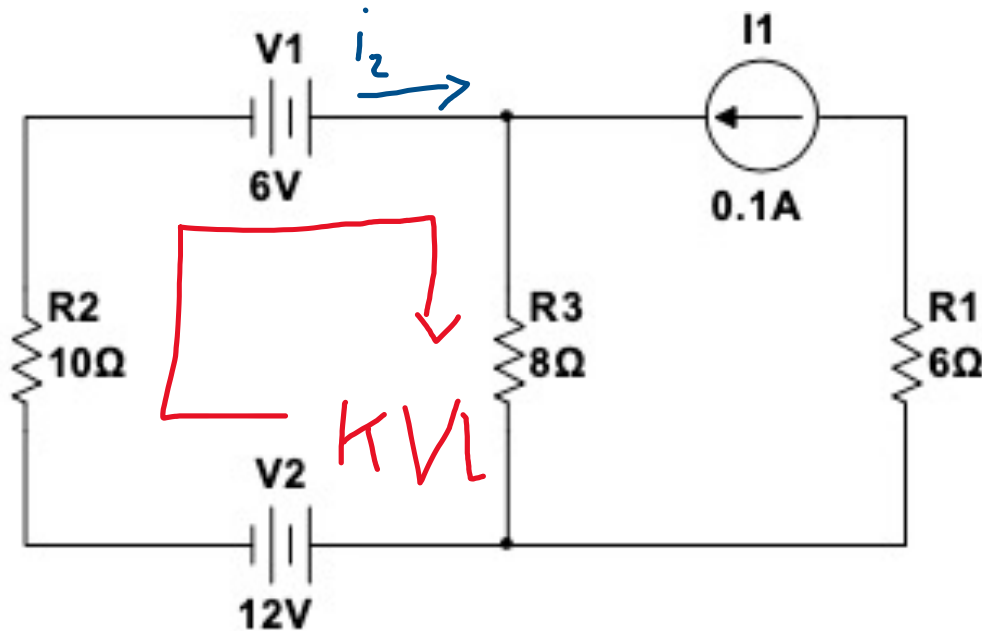

$$\sum_{\text{closed loop}} \Delta V = 0$$
$$V_1 + V_{R_3} + V_2 + V_{R_2} = 0$$
$$V_1 + (i_3 R_3) + V_2 + (i_2 R_2) = 0$$
$$V_1 + i_3 R_3 + V_2 + i_2 R_2 = 0$$
$$(-6) + (12) + i_3(8) + i_2(10) = 0$$
$$6 + 8i_3 + 10i_2 = 0$$


# Example in Lecture

Step 2 - Junction Rule :

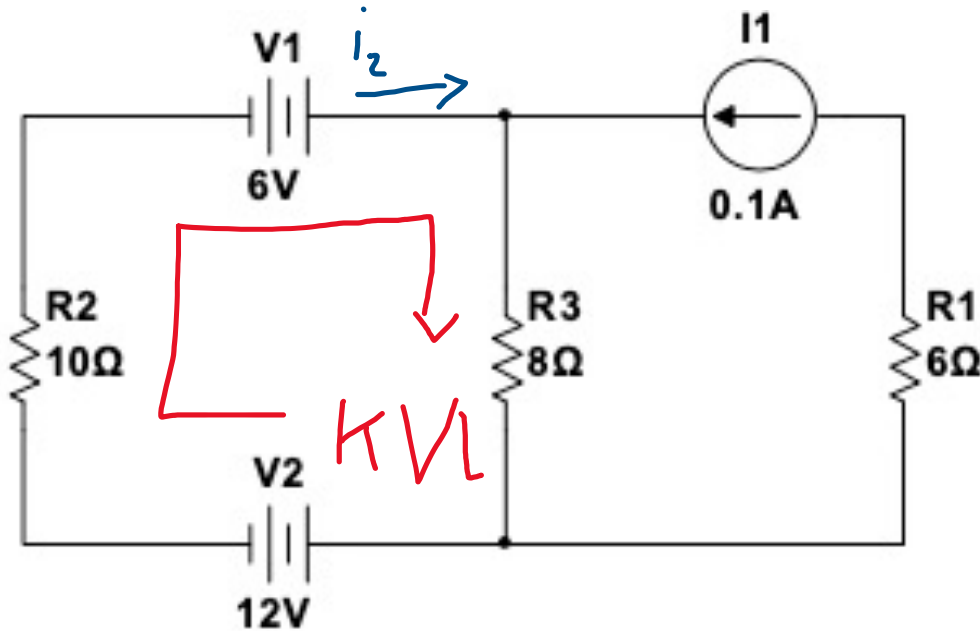

$$\sum_{\text{junction}} i = 0$$
$$i_1 + i_2 - i_3 = 0$$
$$0.1 + i_2 - i_3 = 0$$
$$i_3 = 0.1 + i_2$$

# Example in Lecture

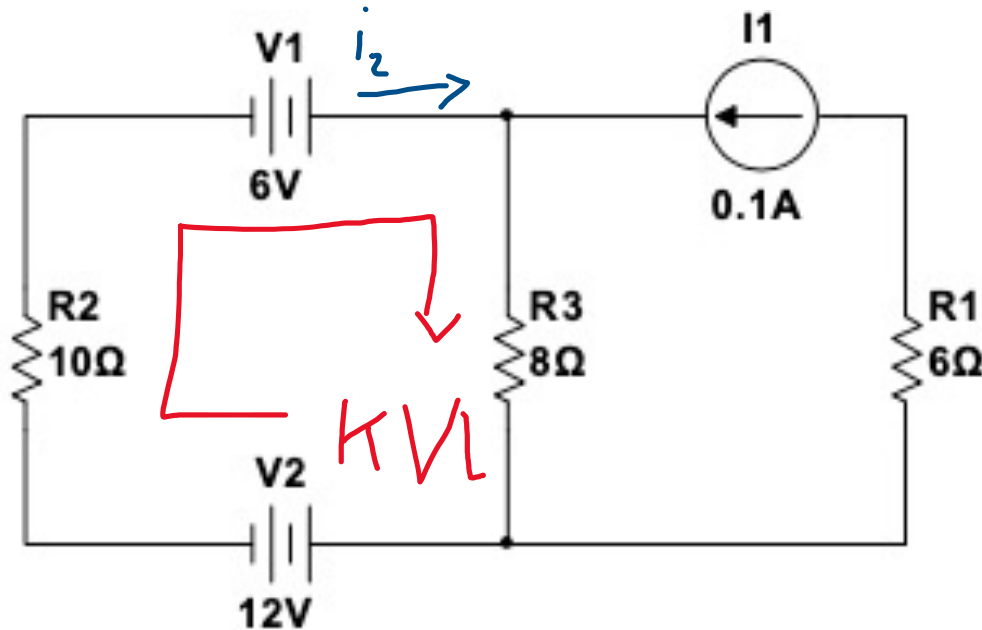

**Step 3 - Substitute:**

$$6 + 8i_3 + 10i_2 = 0$$

$$6 + 8(0.1 + i_2) + 10i_2 = 0$$

$$6 + 0.8 + 8i_2 + 10i_2 = 0$$

$$6.8 + 18i_2 = 0$$

$$i_2 = \frac{-6.8}{18}$$

$$i_2 = -0.377$$

$$i_3 = 0.1 + i_2$$

$$i_3 = 0.1 + (-0.377)$$

$$i_3 = -0.277$$

$$i_1 = 0.1 \text{ A}, i_2 = -0.377 \text{ A}, i_3 = -0.277 \text{ A}$$




# Chapter 33: AC Circuits


## (Serway, 9<sup>th</sup> edition)
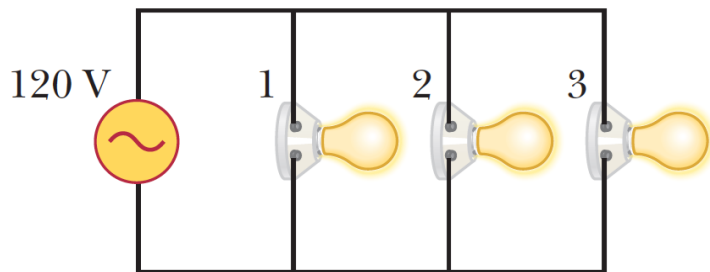
## Problem 2

The figure below shows three lightbulbs connected to a 120-V AC (rms) household supply voltage. Bulb 1 has a power rating of 40 W, bulb 2 has a 75 W rating and bulb 3 has a 60 W rating. Find (a) the rms current in each bulb and (b) the resistance of each bulb. (c) What is the total resistance of the combination of the three lightbulbs:



## Problem 2

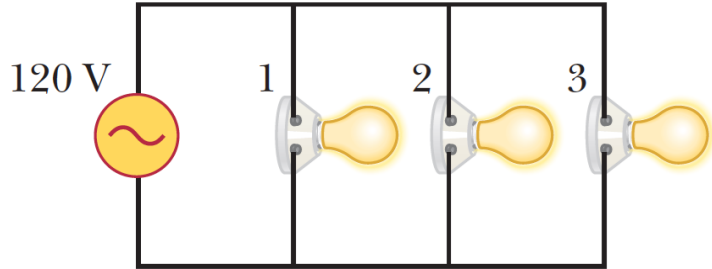


Find the RMS Current:

$$I_{1,rms} = \frac{P_1}{V} = \frac{40W}{120V} = 0.33A$$

$$I_{2,rms} = \frac{P_2}{V} = \frac{75W}{120V} = 0.625A$$

$$I_{3,rms} = \frac{P_3}{V} = \frac{60W}{120V} = 0.5A$$

## Problem 2

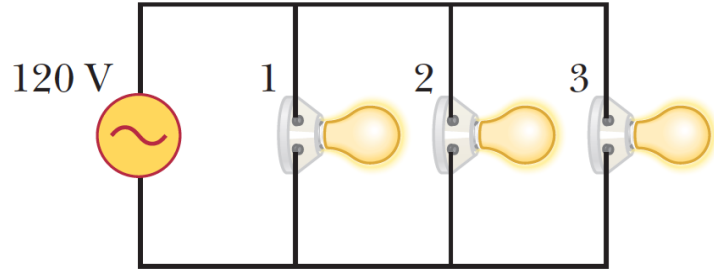


Find the resistance of each bulb :

$$R_1 = \frac{V^2}{P_1} = \frac{(120V)^2}{40W} = 360 \, \Omega$$

$$R_2 = \frac{V^2}{P_2} = \frac{(120V)^2}{75W} = 192 \, \Omega$$

$$R_3 = \frac{V^2}{P_3} = \frac{(120V)^2}{60W} = 240 \, \Omega$$

## Problem 2

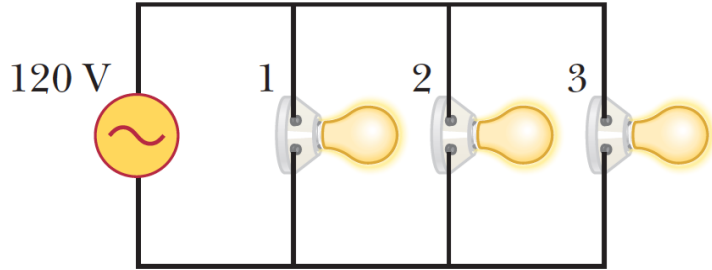

the total resistance of the combination of the three lightbulbs :

$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{total} = \left( \frac{1}{360} + \frac{1}{192} + \frac{1}{240} \right)^{-1} = 82.3 \, \Omega$$

## Problem 3

What maximum current is delivered by an AC source M with  $\Delta V_{max} = 48.0 \text{ V}$  and  $f=90.0 \text{ Hz}$  when connected across a  $3.70\text{-}\mu\text{F}$  capacitor?

## Problem 3

What maximum current is delivered by an AC source with  $\Delta V_{max} = 48.0 \text{ V}$  and  $f=90.0 \text{ Hz}$  when connected across a  $3.70\text{-}\mu\text{F}$  capacitor?

1. Find the  $V_{RMS}$

$$\Delta V_{RMS} = \frac{\Delta V_{max}}{\sqrt{2}}$$

$$\Delta V_{RMS} = 33.94 \text{ V}$$

## Problem 3

What maximum current is delivered by an AC source M with  $\Delta V_{max} = 48.0 \text{ V}$  and  $f=90.0 \text{ Hz}$  when connected across a  $3.70\text{-}\mu\text{F}$  capacitor?

2. Find the reactance

$$x_c = \frac{1}{2\pi f C}$$

$$x_c = \frac{1}{2\pi(90 \text{ Hz})(3.7 \times 10^{-6})}$$

$$x_c = 477.94 \Omega$$



## Problem 3

What maximum current is delivered by an AC source M with  $\Delta V_{max} = 48.0 \text{ V}$  and  $f=90.0 \text{ Hz}$  when connected across a  $3.70\text{-}\mu\text{F}$  capacitor?

3. Find the  $I_{rms}$

$$I_{rms} = \frac{\Delta V_{RMS}}{x_c}$$

$$I_{rms} = \frac{33.94 \text{ V}}{477.94 \Omega}$$

$$I_{rms} = 0.071 \text{ A}$$

## Problem 3

What maximum current is delivered by an AC source M with  $\Delta V_{max} = 48.0 \text{ V}$  and  $f=90.0 \text{ Hz}$  when connected across a  $3.70\text{-}\mu\text{F}$  capacitor?

3. Find the  $I_{rms}$

$$I_{peak} = I_{rms}\sqrt{2}$$

$$I_{peak} = (0.071 \text{ A})\sqrt{2}$$


$$I_{peak} = 0.100 \text{ A}$$

# Section 1-7: Review of Phasors (Ulaby, 8<sup>th</sup> ed.)
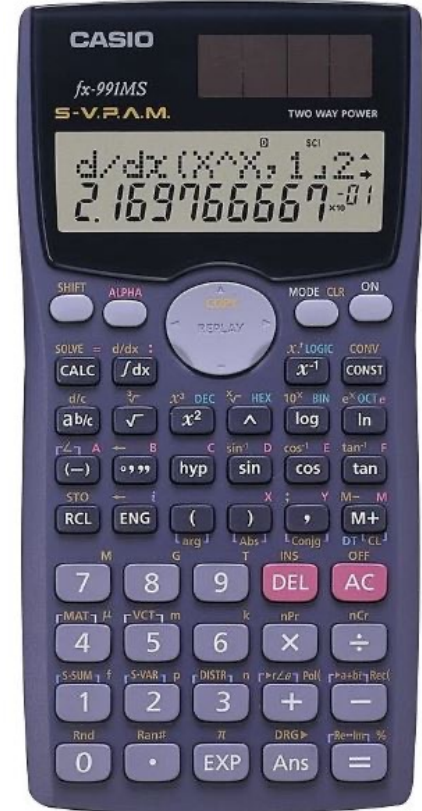
# McMaster's Standard Calculator

- Casio FX-991MS
- 2<sup>nd</sup> Edition (left) available at McMaster Bookstore: \$21.99 (link below)
- Will need to solve phasor equations

<https://campusstore.mcmaster.ca/cgi-mcm/ws/gmdetail.pl?pwsPRODIDG1=2207018&sType=gm&proddesc=Casio%20fx%2D991%20Calculator&pwsGROUP=>





# Phasor Conversion – Calculator Setup

Enable complex numbers:


- “CMPLX” appears at top of display

Ensure calculator is in degree mode

- For consistent units in polar form

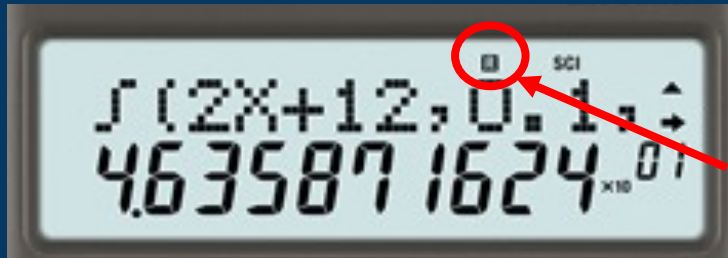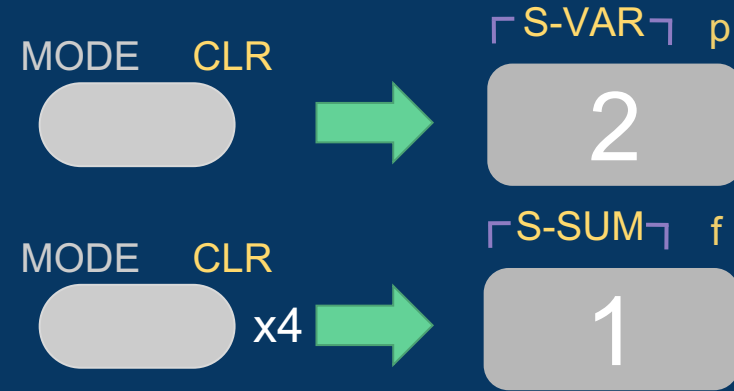


BAD!

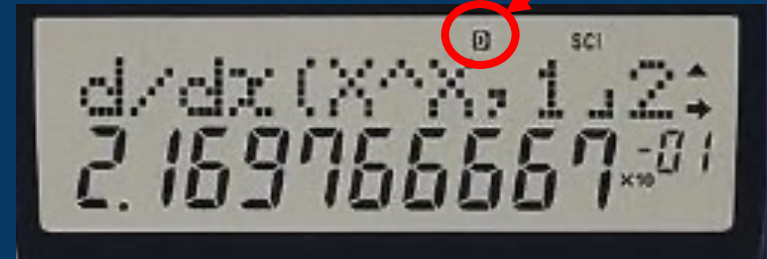

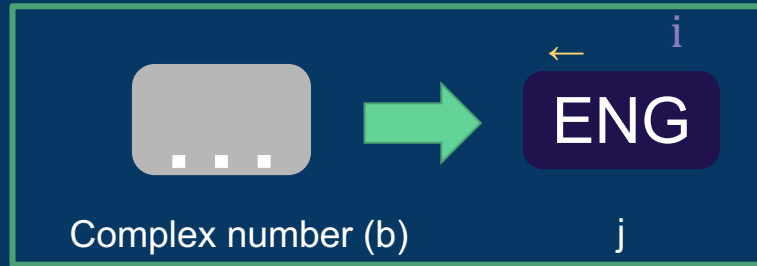
# Phasor Conversion – Inputting Complex Values

To enter complex number in rectangular form:




To enter angle value in polar form:

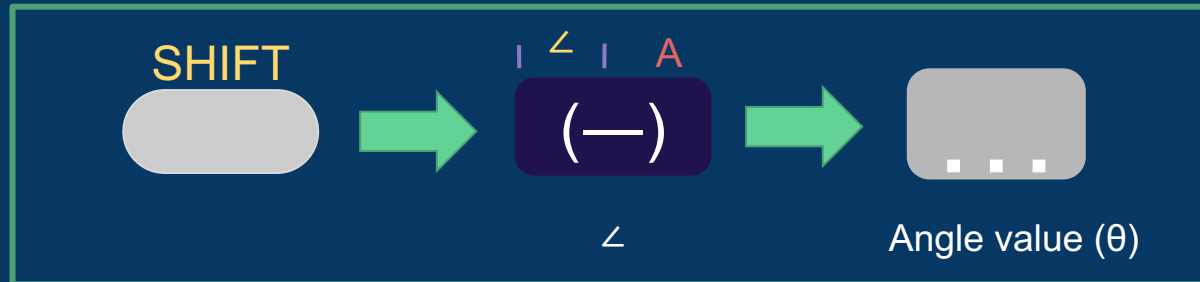


# Phasor Conversion – Output Viewing


To view answer in rectangular form:

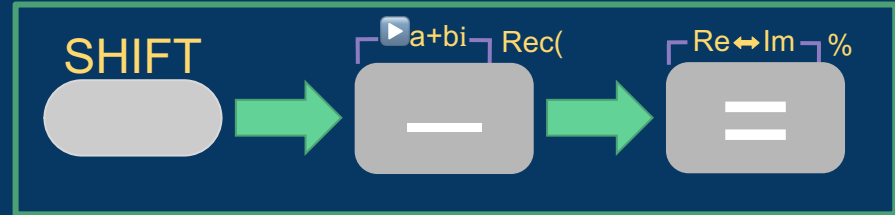

To view answer in polar form:

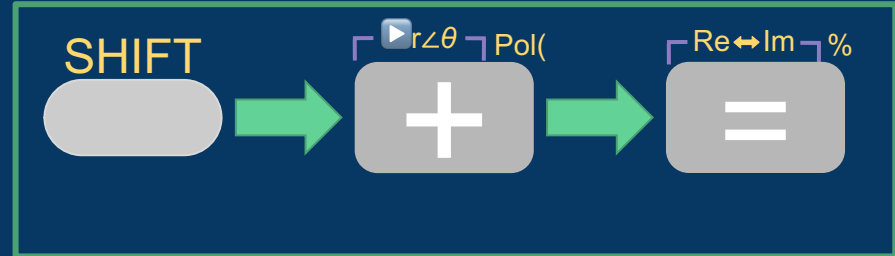

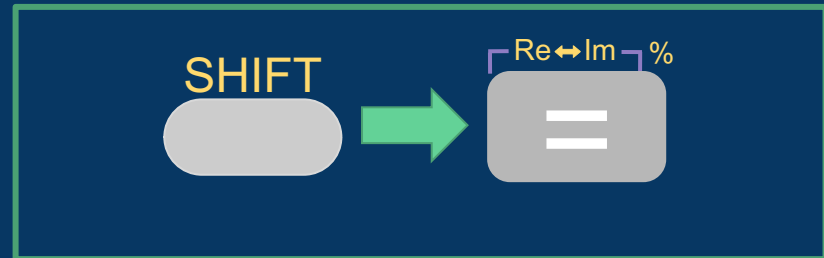To change between real and imaginary (rectangular) or radius and angle (polar):



## Phasor Conversion - Question

Convert the following phasors to rectangular form ( $a + bj$ ):

a)  $9 \angle -60^\circ$

b)  $12 \angle -45^\circ$

Convert the following phasors to polar form ( $r \angle \theta$ ):



a)  $3 + 9j$

b)  $-0.4 + 0.3j$



# Phasor Conversion - Solution

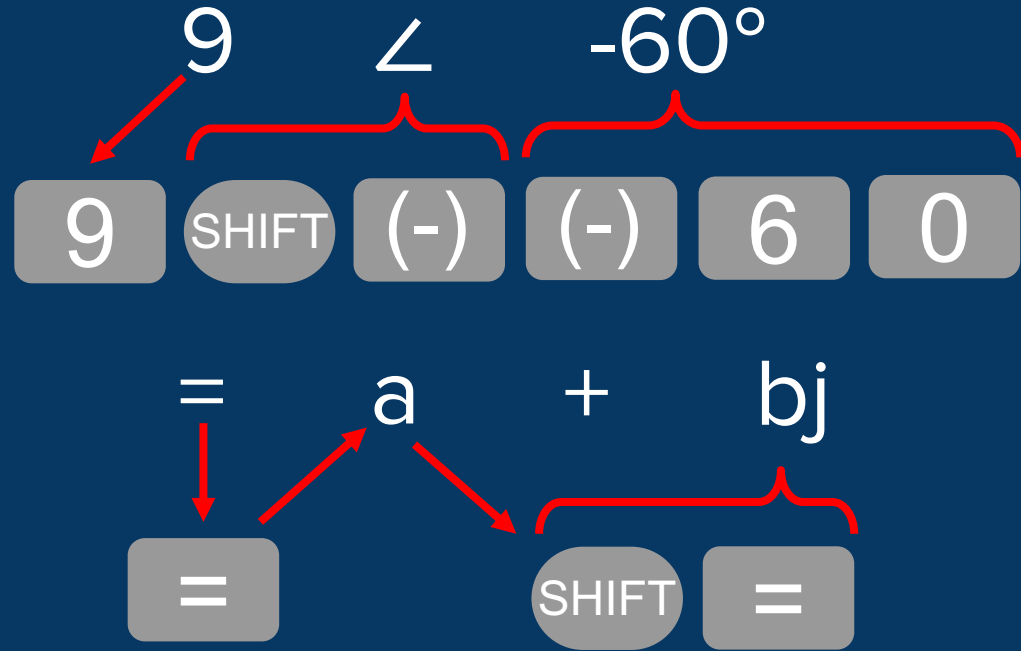
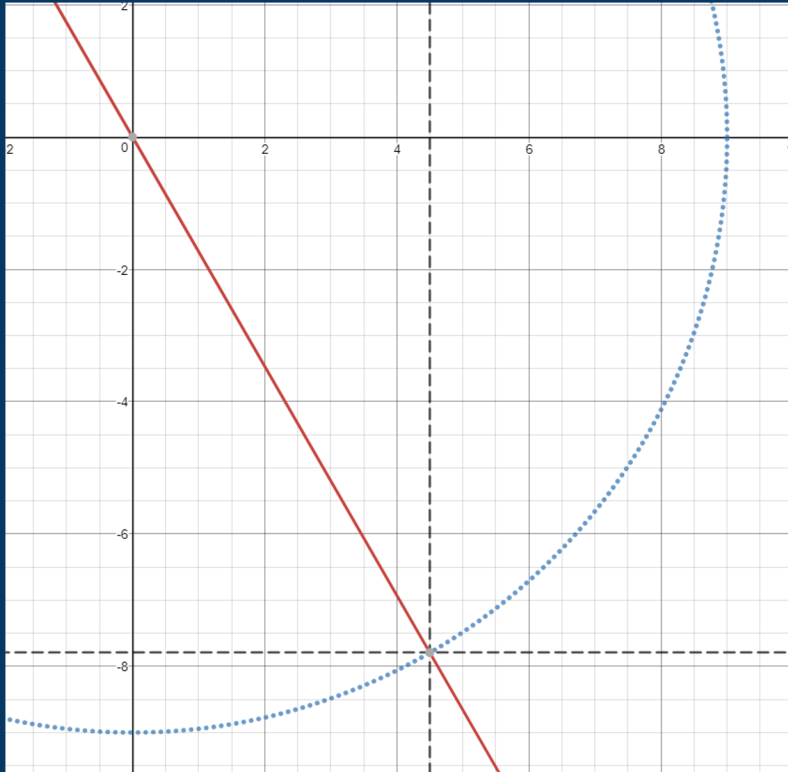
a) Convert the following to rectangular form ( $a + bj$ ):



Answer:  $4.5 - 7.79j$

# Phasor Conversion - Solution

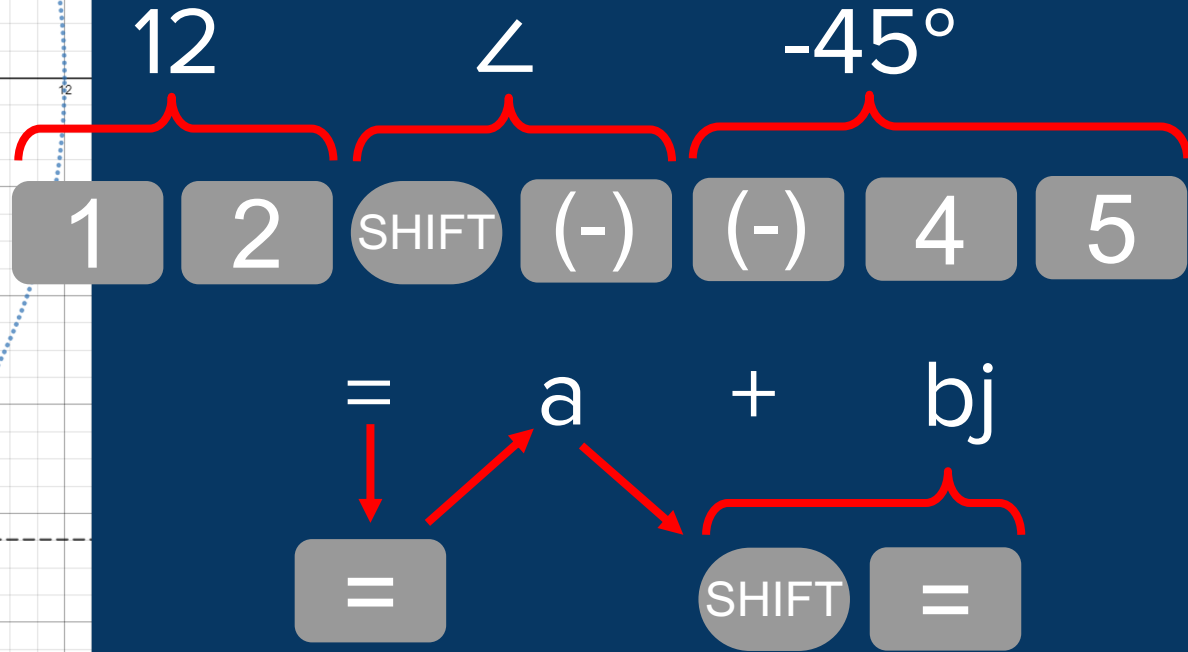
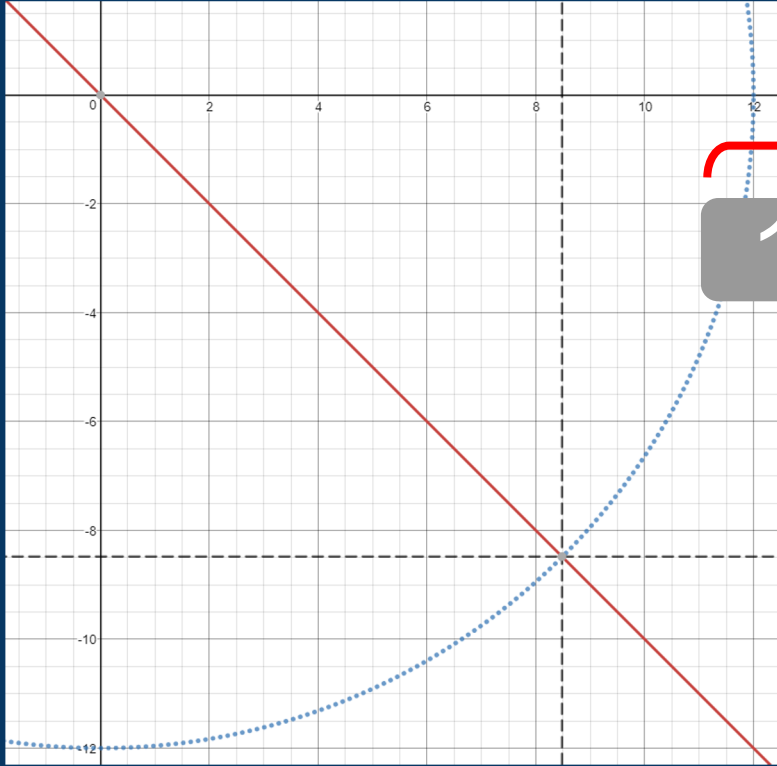
b) Convert the following to rectangular form ( $a + bj$ ):



Answer:  $8.48 - 8.48j$

# Phasor Conversion - Solution

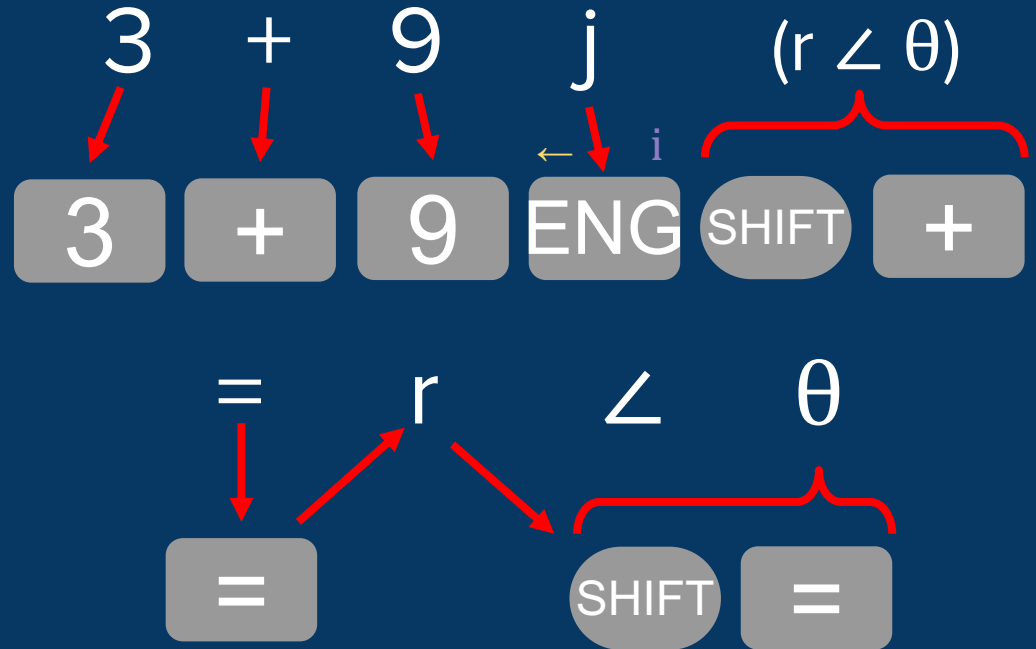
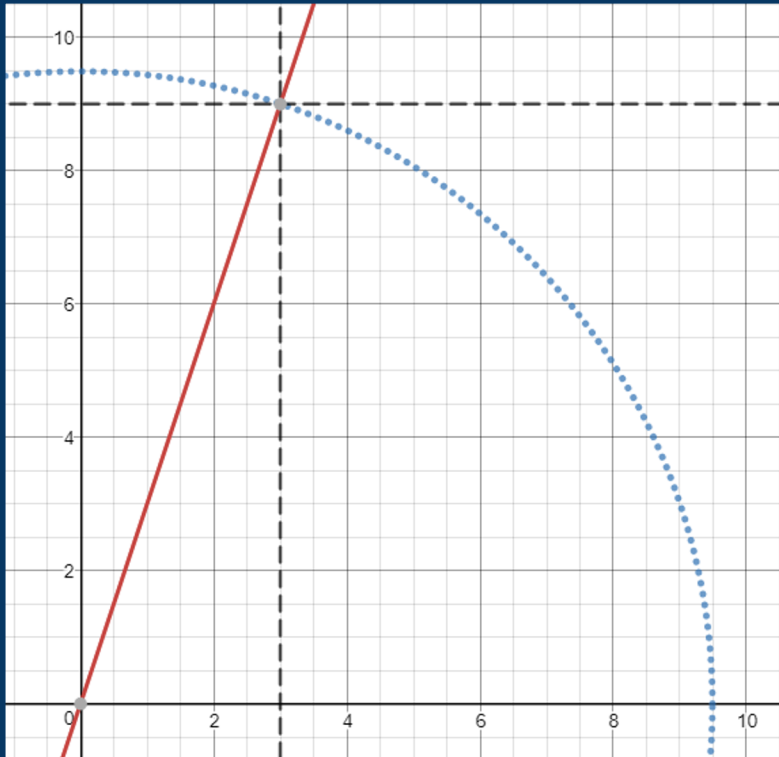
a) Convert the following to polar form ( $r \angle \theta$ ):



Answer:  $9.49 \angle 71.56^\circ$

# Phasor Conversion - Solution

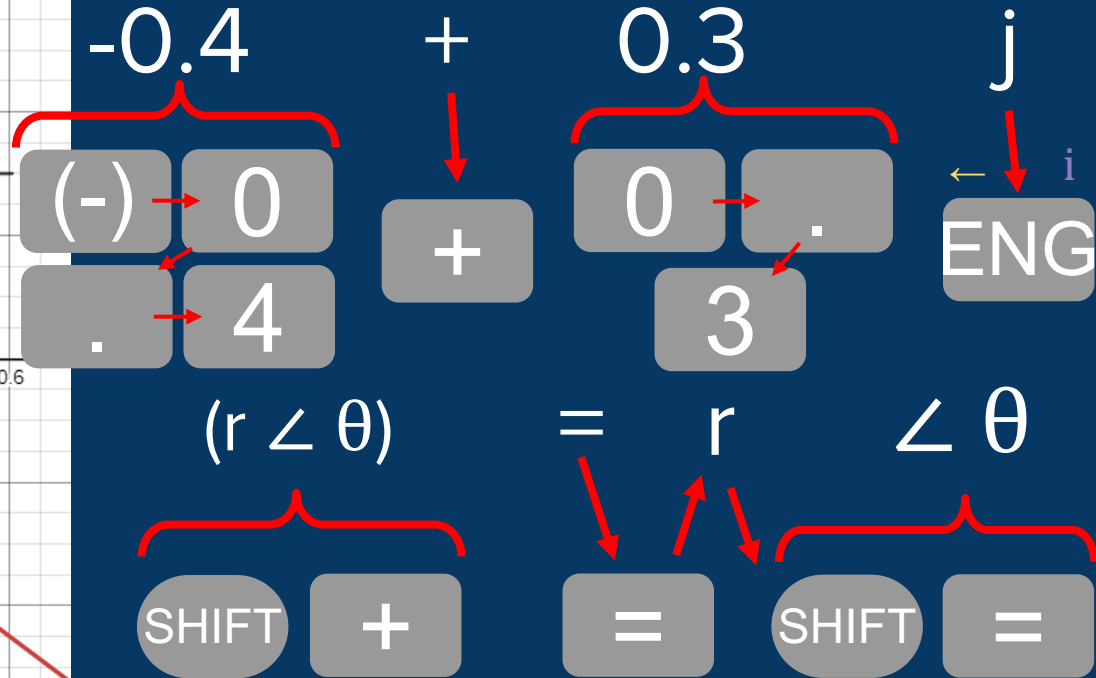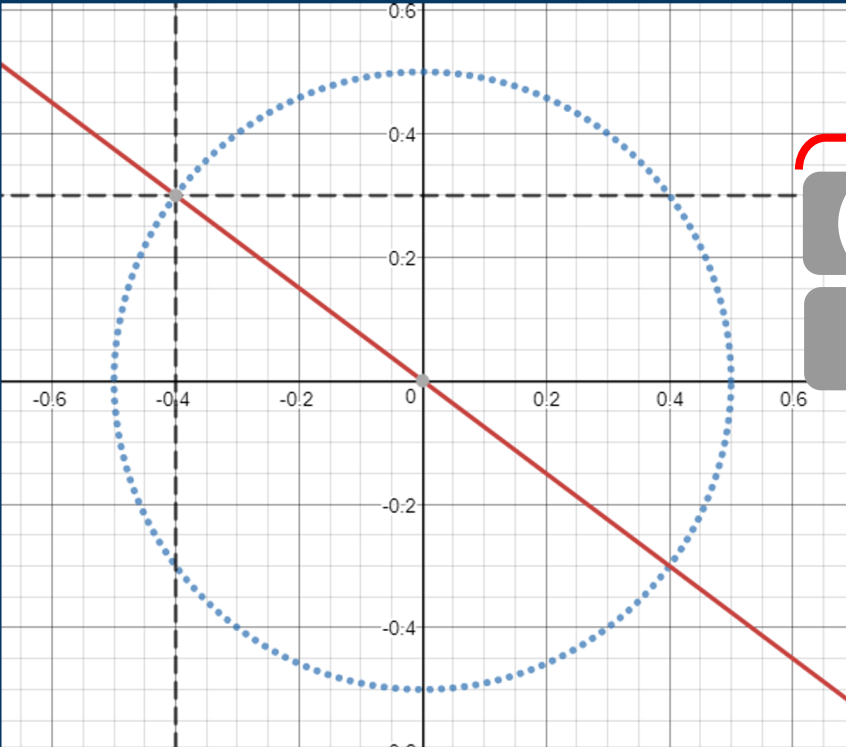a) Convert the following to polar form ( $r \angle \theta$ ):



Answer:  $0.5 \angle 143.13^\circ$

## Problem 1.28 – Question

Find the phasors of the following time functions:

$$a) \quad v(t) = 9 \cos\left(\omega t - \frac{\pi}{3}\right) \text{ (V)}$$

$$b) \quad v(t) = 12 \sin\left(\omega t + \frac{\pi}{4}\right) \text{ (V)}$$

$$c) \quad i(x, t) = 5e^{-3x} \sin\left(\omega t + \frac{\pi}{6}\right) \text{ (A)}$$

$$d) \quad i(t) = -2 \cos\left(\omega t + \frac{3\pi}{4}\right) \text{ (A)}$$

$$e) \quad i(t) = 4 \sin\left(\omega t + \frac{\pi}{3}\right) + 3 \cos\left(\omega t - \frac{\pi}{6}\right) \text{ (A)}$$

## Problem 1.28 – Solution (a)

a)  $v(t) = 9 \cos\left(\omega t - \frac{\pi}{3}\right)$  (V)

Adopt cosine reference ( $v(t) = V_0 \cos(\omega t + \phi)$ ). Is this already done?

- Yes!  $V_0 = 9$ ,  $\phi = -\frac{\pi}{3}$

From sinusoidal time domain to phasor domain:

- $v(t) = V_0 \cos(\omega t + \phi) \rightarrow \mathbf{V} = V_0 e^{j\phi}$

$$\therefore v(t) = 9 \cos\left(\omega t - \frac{\pi}{3}\right) \text{ (V)} \rightarrow \mathbf{V} = 9e^{-j\frac{\pi}{3}} \text{ (V)}$$

## Problem 1.28 – Solution (b)

b)  $v(t) = 12 \sin\left(\omega t + \frac{\pi}{4}\right) \text{ (V)}$

Adopt cosine reference ( $v(t) = V_0 \cos(\omega t + \phi)$ ). Is this already done?

- No!  $\rightarrow v(t) = 12 \sin\left(\omega t + \frac{\pi}{4}\right) = 12 \cos\left(\omega t + \frac{\pi}{4} - \frac{\pi}{2}\right) = 12 \cos\left(\omega t - \frac{\pi}{4}\right)$
- $V_0 = 12, \phi = -\frac{\pi}{4}$

Sinusoidal time domain  $\rightarrow$  phasor domain:  $v(t) = V_0 \cos(\omega t + \phi) \rightarrow \mathbf{V} = V_0 e^{j\phi}$

$$\therefore v(t) = 12 \sin\left(\omega t + \frac{\pi}{4}\right) \text{ (V)} = 12 \cos\left(\omega t - \frac{\pi}{4}\right) \text{ (V)} \rightarrow \mathbf{V} = 12e^{-j\frac{\pi}{4}} \text{ (V)}$$

## Problem 1.28 – Solution (c)

c)  $i(x, t) = 5e^{-3x} \sin\left(\omega t + \frac{\pi}{6}\right)$  (A)

Adopt cosine reference ( $i(t) = V_0 \cos(\omega t + \phi)$ ). Is this already done?

- No!  $\rightarrow i(x, t) = 5e^{-3x} \sin\left(\omega t + \frac{\pi}{6}\right) = 5e^{-3x} \cos\left(\omega t + \frac{\pi}{6} - \frac{\pi}{2}\right) = 5e^{-3x} \cos\left(\omega t - \frac{\pi}{3}\right)$

- $V_0 = 5e^{-3x}, \phi = -\frac{\pi}{3}$

Sinusoidal time domain  $\rightarrow$  phasor domain:  $v(t) = V_0 \cos(\omega t + \phi) \rightarrow \mathbf{V} = V_0 e^{j\phi}$

$$\therefore i(x, t) = 5e^{-3x} \sin\left(\omega t + \frac{\pi}{6}\right) \text{ (A)} = 5e^{-3x} \cos\left(\omega t - \frac{\pi}{3}\right) \text{ (A)} \rightarrow \mathbf{\tilde{V}} = 5e^{-3x} e^{-j\frac{\pi}{3}} \text{ (V)}$$



## Problem 1.28 – Solution (d)

d)  $i(t) = -2 \cos\left(\omega t + \frac{3\pi}{4}\right)$  (A)

Adopt cosine reference ( $i(t) = I_0 \cos(\omega t + \phi)$ ). Is this already done?

- Yes!  $I_0 = -2$ ,  $\phi = \frac{3\pi}{4}$
- One missing step:  $-1 = e^{-j\pi} \rightarrow I_0 = -2 = 2(-1) = 2e^{-j\pi}$

Sinusoidal time domain  $\rightarrow$  phasor domain  $i(t) = I_0 \cos(\omega t + \phi) \rightarrow \mathbf{I} = I_0 e^{j\phi}$

$$\therefore i(t) = -2 \cos\left(\omega t + \frac{3\pi}{4}\right) \text{ (A)} \rightarrow \mathbf{I} = 2e^{-j\pi} e^{j\frac{3\pi}{4}} \text{ (A)} \rightarrow \mathbf{I} = 2e^{-j\frac{\pi}{4}} \text{ (A)}$$

## Problem 1.28 – Solution (e)

e)  $i(t) = 4 \sin\left(\omega t + \frac{\pi}{3}\right) + 3 \cos\left(\omega t - \frac{\pi}{6}\right)$  (A)

Adopt cosine reference ( $i(t) = I_0 \cos(\omega t + \phi)$ ). Is this already done?

- Kinda...  $\rightarrow 4 \sin\left(\omega t + \frac{\pi}{3}\right) = 4 \cos\left(\omega t + \frac{\pi}{3} - \frac{\pi}{2}\right) = 4 \cos\left(\omega t - \frac{\pi}{6}\right)$

- $I_0 = 4, \phi = -\frac{\pi}{6}$  and  $I_0 = 3, \phi = -\frac{\pi}{6}$

Sinusoidal time domain  $\rightarrow$  phasor domain  $i(t) = I_0 \cos(\omega t + \phi) \rightarrow \mathbf{I} = I_0 e^{j\phi}$

$$\therefore i(t) = 4 \sin\left(\omega t + \frac{\pi}{3}\right) + 3 \cos\left(\omega t - \frac{\pi}{6}\right) \text{ (A)} \rightarrow \mathbf{I} = 4e^{-j\frac{\pi}{6}} + 3e^{-j\frac{\pi}{6}} \rightarrow \mathbf{I} = 7e^{-j\frac{\pi}{6}} \text{ (A)}$$