

Example for Transistor's Parameters

Problem 1: Determine I_B , I_C , I_E , V_{BE} , V_{CE} , and V_{CB} in the circuit given below. The transistor has a $\beta_{DC} = 150$.

Solution 1:

The forward bias voltage drop


$$V_{BE} = 0.7 \text{ V}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega}$$

$$I_B = 0.43 \text{ mA}$$

$$I_C = \beta_{DC} I_B = 150 \times 0.43 \text{ mA} = 64.5 \text{ mA}$$
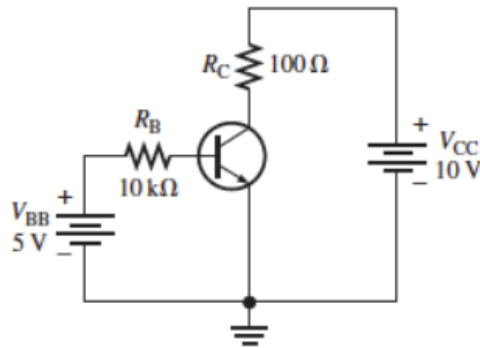
$$I_E = I_C + I_B = 64.5 \text{ mA} + 0.43 \text{ mA} = 64.93 \text{ mA}$$




$$V_{CC} = I_C R_C + V_{CE}$$

$$V_{CE} = 10 - 64.5 \text{ mA} \times 100 \, \Omega$$

$$V_{CE} = 3.55 \text{ V}$$

$$V_{CB} = V_C - V_B = V_C - V_E - (V_B - V_E)$$
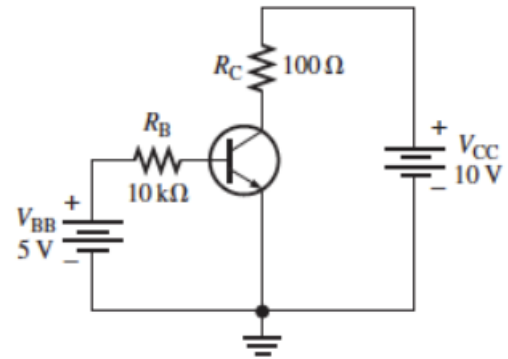
$$V_{CB} = V_{CE} - V_{BE} = 3.55 \text{ V} - 0.7 \text{ V} = 2.85 \text{ V}$$





Example for Current Gain

Problem 2: Sketch an ideal family of collector curves for the shown transistor with $\beta_{DC} = 100$ for I_B varying from $5\ \mu\text{A}$ to $25\ \mu\text{A}$.

Solution 2:

For active region $I_C = \beta_{DC} I_B$

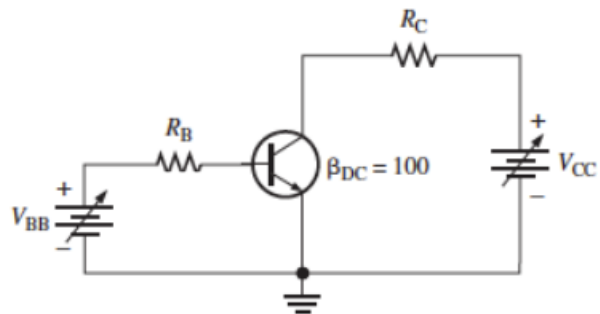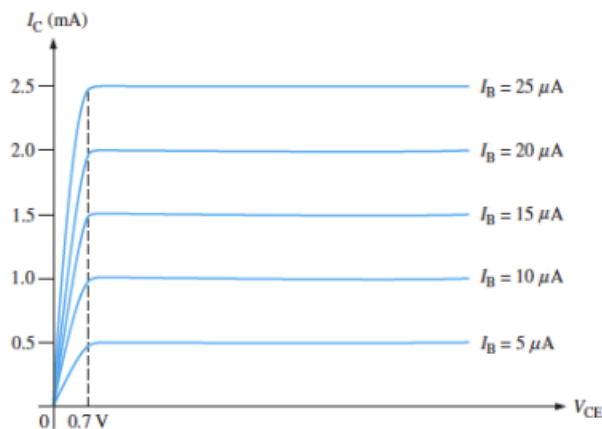

Problem 1: Determine whether or not the following BJT transistor is in saturation. Assume $V_{CE(sat)} = 0.2 \text{ V}$.

Solution 1:


The collector saturation current, $I_{C(sat)}$ is given by

$$I_{C(sat)} = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$

$$I_{C(sat)} = \frac{10 \text{ V} - 0.2 \text{ V}}{1 \text{ k}\Omega} = 9.8 \text{ mA}$$

$$I_{B(sat)} = \frac{I_{C(sat)}}{\beta_{DC}}$$

$$I_{B(sat)} = \frac{9.8 \text{ mA}}{50} = 0.196 \text{ mA}$$

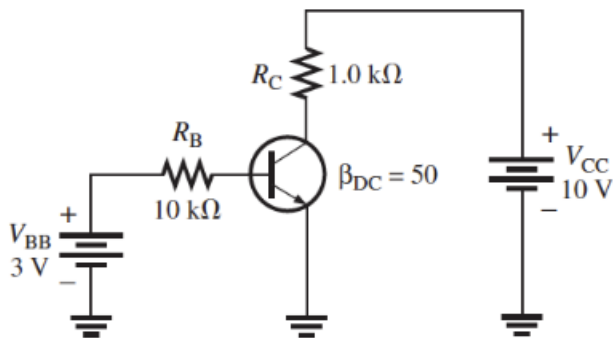

Solution 1:

Now we will see I_B is sufficient to produce $I_{C(sat)}$.


$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_B = \frac{3\text{ V} - 0.7\text{ V}}{10\text{ k}\Omega} = 0.23\text{ mA}$$

Since $I_B > I_{B(sat)}$, BJT is saturated.

$$I_C = I_{C(sat)} = 9.8\text{ mA}$$

$$V_{CE} = V_{CE(sat)} = 0.2\text{ V}$$

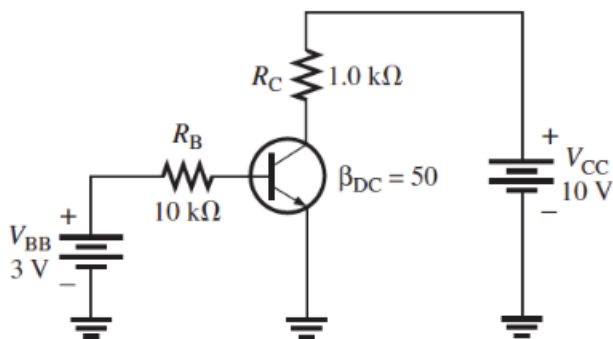

- Problem 2:** (a) For the transistor circuit given below, what is V_{CE} when $V_{IN}=0$ V?
- (b) What minimum value of I_B is required to saturate this transistor if β_{DC} is 200? Neglect $V_{CE(sat)}$.
- (c) Calculate the maximum value of R_B that will put the transistor in saturation assuming $\beta_{DC}=200$ when $V_{IN} = 5$ V.


Solution 2:

(a) When $V_{IN}=0$ V, $V_{BE} = 0$ V

The transistor is in cut-off.

BJT is in cut-off, $I_C=0$ A

$$V_{CE} = V_{CC} = 10 \text{ V}$$

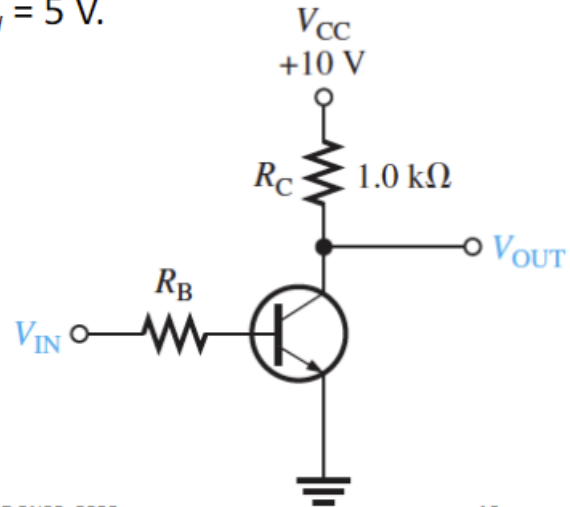


Solution 2:

$$(b) \quad I_{C(sat)} = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$

$$I_{C(sat)} = \frac{10 - 0}{1 \text{ k}\Omega} = 10 \text{ mA}$$

$$I_{B(min)} = I_{B(sat)} = \frac{I_{C(sat)}}{\beta_{DC}}$$
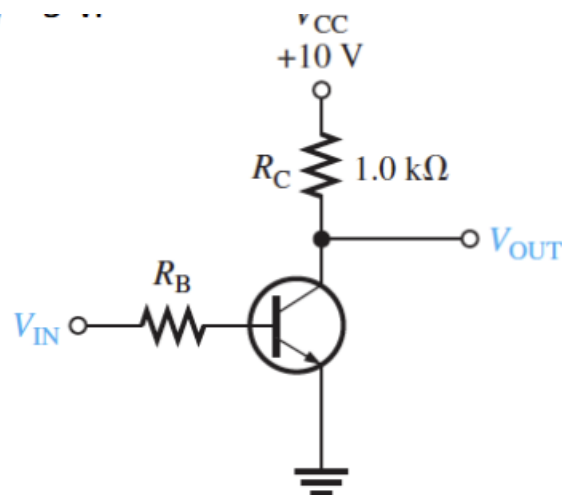
$$I_{B(min)} = \frac{10 \text{ mA}}{200} = 50 \mu\text{A}$$



2023-01-15

Dr. Matiar Howlader, ELECENG 3N03, 2023


11

Solution 2:

$$(c) \quad R_B = \frac{V_{IN} - V_{BE}}{I_B}$$

$$\begin{aligned} R_{B(max)} &= \frac{V_{IN} - V_{BE}}{I_{B(min)}} \\ &= \frac{5 - 0.7}{50 \mu\text{A}} = 86 \text{ k}\Omega \end{aligned}$$

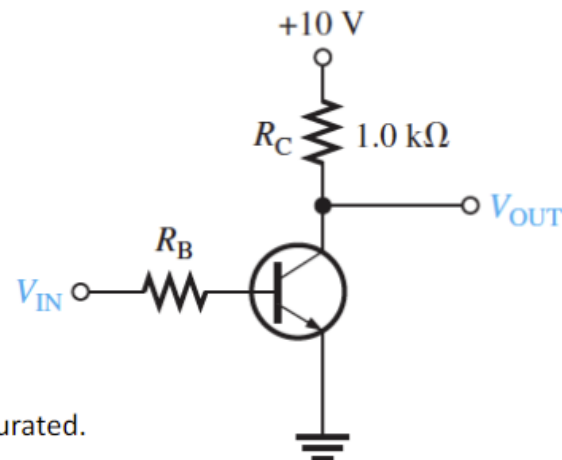If $R_B > 86 \text{ k}\Omega$, the transistor will not be saturated.



2023-01-15

Dr. Matiar Howlader, ELECENG 3N03, 2023

12

Problem 1: Determine V_{CE} and I_C in the shown voltage-divider biased transistor circuit if $\beta_{DC} = 100$, and $V_{CE(sat)} = 0.2$ V. Is this transistor in saturation?

Solution 1:

$$V_{TH} = \frac{R_2}{R_1 + R_2} \times V_{CC}$$



$$V_{TH} = \frac{5.6 \text{ k}\Omega}{10 \text{ k}\Omega + 5.6 \text{ k}\Omega} \times 10 \text{ V}$$

$$V_{TH} = 3.59 \text{ V}$$

$$R_{TH} = R_1 || R_2$$

$$R_{TH} = \frac{10 \text{ k}\Omega \times 5.6 \text{ k}\Omega}{10 \text{ k}\Omega + 5.6 \text{ k}\Omega}$$

$$R_{TH} = 3.59 \text{ k}\Omega$$

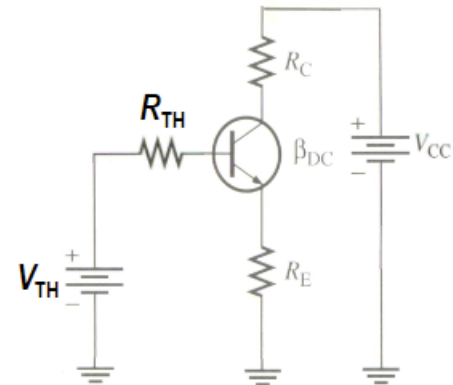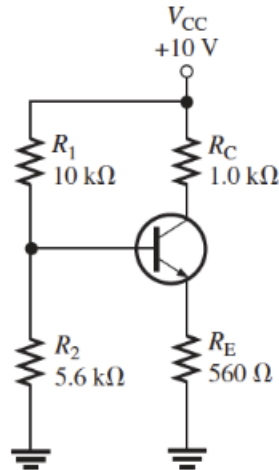

Solution 1:

$$V_{TH} = R_{TH}I_B + V_{BE} + I_ER_E$$

$$V_{TH} = R_{TH}I_B + 0.7 + (\beta_{DC} + 1)I_B \times 560 \, \Omega$$


$$I_B = \frac{V_{TH} - 0.7}{R_{TH} + (\beta_{DC} + 1)I_B \times 560 \, \Omega} = \frac{3.59 \, V - 0.7 \, V}{3.59 \, k\Omega + (101) \times 560 \, \Omega}$$

$$I_B = 51.1 \, \mu A$$

$$I_C = \beta_{DC} \times I_B = 100 \times 51.1 \, \mu A = 5.1 \, mA$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$V_{CE} = 10 \, V - 5.1 \, mA \times 1 \, k\Omega - (\beta_{DC} + 1)I_B \times 560 \, \Omega = 2.01 \, V \quad \mathbf{V_{CE} = 2.01 \, V \gg V_{CE(sat)}}$$

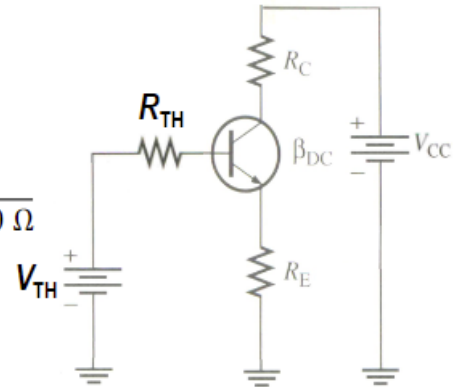

Problem 2: Determine the Q-point (I_C , V_{CE}) for the shown circuit if $\beta_{DC}=200$ and $V_{CE(sat)}=0.2$ V.


Solution 2:

$$I_B = \frac{12\text{ V} - 0.7\text{ V}}{330\text{ k}\Omega} = 34.2\text{ }\mu\text{A}$$

$$I_C = \beta_{DC} \times I_B = 200 \times 34.2\text{ }\mu\text{A} = 6.8\text{ mA}$$

$$V_{CE} = 12 - 6.8\text{ mA} \times 560\Omega = 8.2\text{ V}$$

$$V_{CE} = 8.2\text{ V} \gg V_{CE(sat)}$$

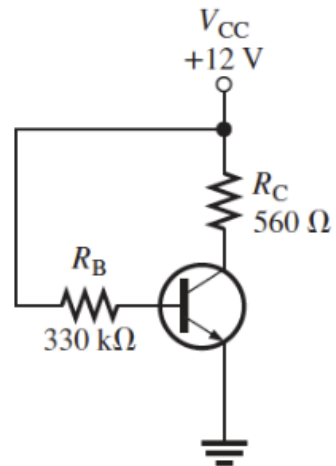

Problem 3: Find the Q-point values (I_C and V_{CE}) for the given circuit if $\beta_{DC}=100$ and $V_{CE(sat)}=0.2$ V.

Solution 3:

$$V_{CC} = I_E R_C + I_B R_B + V_{BE}$$


$$I_E = (\beta_{DC} + 1)I_B$$

$$I_B = \frac{V_{CC} - V_{CE}}{(\beta_{DC} + 1)R_C + R_B}$$

$$I_B = \frac{10\text{ V} - 0.7\text{ V}}{101 \times 10\text{ k}\Omega + 180\text{ k}\Omega} = 7.82\text{ }\mu\text{A}$$

$$I_C = \beta_{DC} \times I_B = 100 \times 7.82\text{ }\mu\text{A} = 0.782\text{ mA}$$
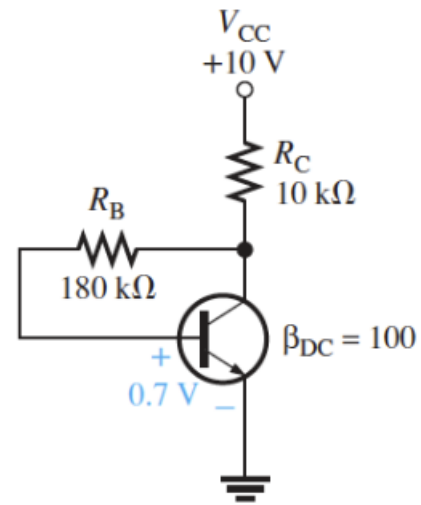
$$V_{CE} = V_{CC} - I_E R_C = 10 - 0.782\text{ mA} \times 10\text{ k}\Omega = 2.18\text{ V}$$



$$V_{CE} = 2.18\text{ V} \gg V_{CE(sat)}$$

Problem 1: Determine the Q-point for the circuit given below and draw the dc load line. Find the maximum peak value of base current and collector current to avoid distortion. Assume $V_{CE(sat)}=0$, and $\beta_{DC} = 200$

Solution 1:

$$I_{C(sat)} = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$


$$I_{C(sat)} = \frac{20\text{ V} - 0}{330\ \Omega} = 60.6\text{ mA}$$

$$I_{B(sat)} = \frac{I_{C(sat)}}{\beta_{DC}} = 303\ \mu\text{A}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_B = \frac{10\text{ V} - 0.7\text{ V}}{47\text{ k}\Omega}$$

$$I_B = 198\ \mu\text{A} < I_{B(sat)}$$

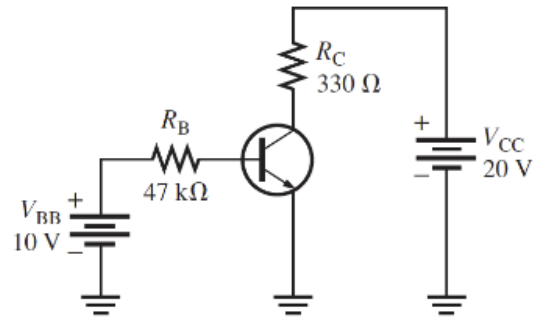

Solution 1:

$$I_C = \beta_{DC} I_B = 200 \times 198 \mu A$$

$$I_C = \beta_{DC} I_B = 39.6 \text{ mA}$$


$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = 20 \text{ V} - 39.6 \text{ mA} \times 330 \Omega$$

$$V_{CE} = 6.93 \text{ V}$$

$$Q \text{ point } V_{CE} = 6.93 \text{ V}, I_C = 39.6 \text{ mA}$$

$$I_B = 198 \mu A$$

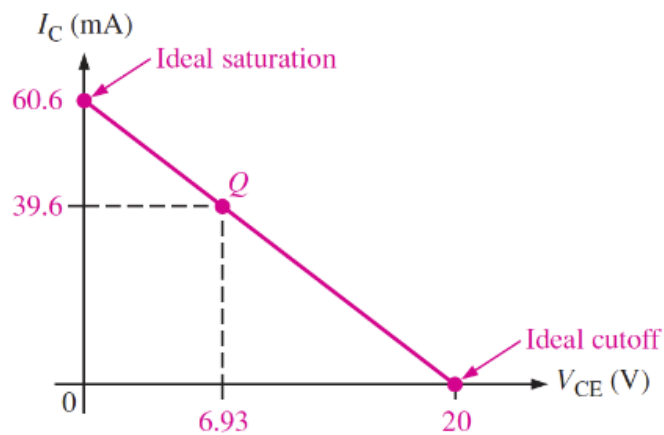

Solution 1:


$$I_{c(peak)} = \min\{(I_{c(sat)} - I_{cQ}), (I_{cQ} - I_{c(off)})\}$$

$$I_{c(peak)} = \min\{(60.6 \text{ mA} - 39.6 \text{ mA}), (39.6 \text{ mA} - 0)\}$$

$$I_{c(peak)} = \min\{(21 \text{ mA}), (39.6 \text{ mA})\}$$

$$I_{c(peak)} = 21 \text{ mA}$$

$$I_{b(peak)} = \frac{I_{c(peak)}}{\beta_{DC}} = \frac{21 \text{ mA}}{200} = 0.105 \text{ mA}$$

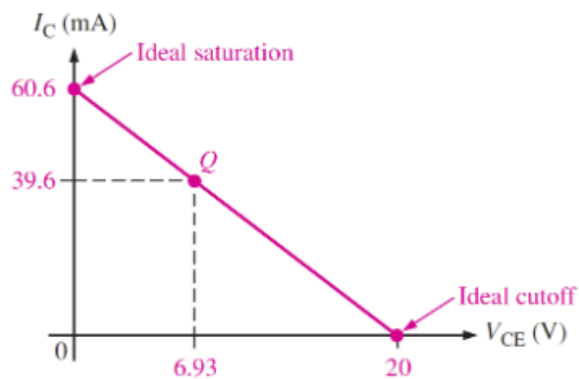

Problem 2: Determine the r_e' of a transistor that is operating with a dc emitter current of 1.62 mA.

Solution 2:

$$r_e' = \frac{25 \text{ mV}}{I_E} = \frac{25 \text{ mV}}{1.62 \text{ mA}} = 15.4 \Omega$$