

# ENGPHYS 2A04

## Tutorial 3

Electricity and Magnetism



# Your TAs Today


- Joanne Lee  
[leej298@mcmaster.ca](mailto:leej298@mcmaster.ca)
- Fatemeh Bakhshandeh  
[bakhshaf@mcmaster.ca](mailto:bakhshaf@mcmaster.ca)

# Your Textbook

Fundamentals of Applied Electromagnetics Eighth Edition.

Ulaby & Ravaioli

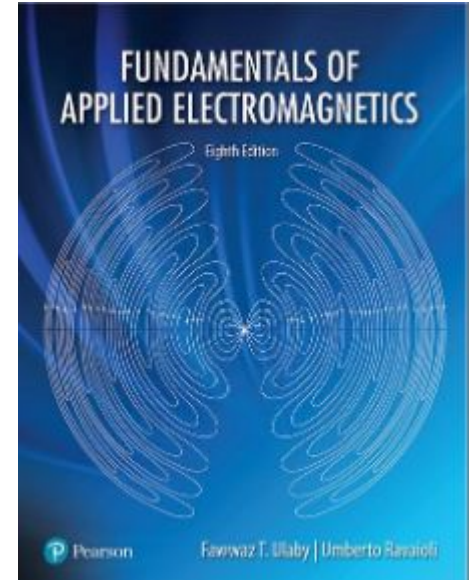
Seventh edition also acceptable, with some inconsistencies


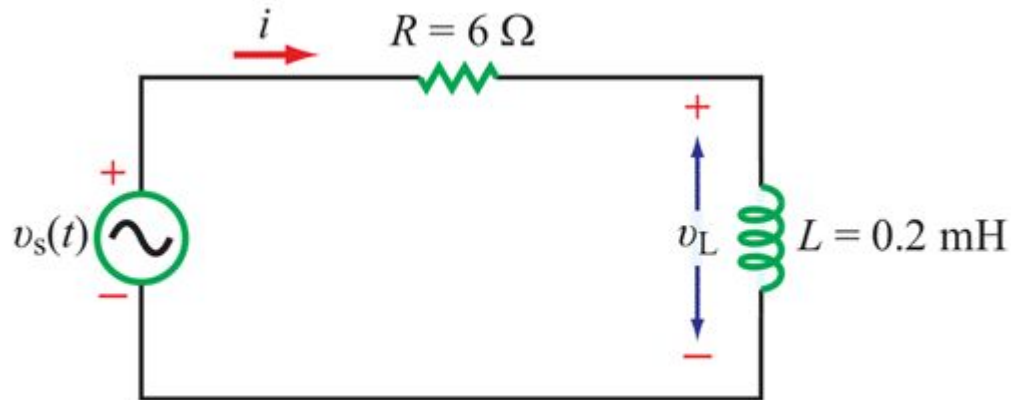
## Lecture Problem (Example 1-4 Page 40)

The voltage source of the RL circuit shown below is given by:

$V_s(t) = 5 \sin(4 \times 10^4 t - 30^\circ)$ . Find an expression for the voltage across the inductor.





## Lecture Problem Solution

Before converting to the phasor domain, we express the initial equation in terms of cosine.

$$\begin{aligned} v_s(t) &= 5 \sin(4 \times 10^4 t - 30^\circ) \\ &= 5 \cos(4 \times 10^4 t - 120^\circ) \quad (\text{V}). \end{aligned}$$

The corresponding voltage phasor equation is

$$\tilde{V}_s = 5e^{-j120^\circ} \quad (\text{V}),$$



## Lecture Problem Solution

The voltage loop equation of the RL circuit is  $Ri + L \frac{di}{dt} = v_s(t)$ .

The corresponding phasor equation is  $R\tilde{I} + j\omega L\tilde{I} = \tilde{V}_s$ .

Solving for current phasor  $I$  the equation becomes:

$$I = \frac{V_s}{R + j\omega L}$$
$$I = \frac{5e^{-j120^\circ}}{6 + j4 * 10^4 * 2 * 10^{-4}}$$

$$I = \frac{5e^{-j120^\circ}}{6 + j8}$$

$$I = \frac{5e^{-j120^\circ}}{10e^{j53.1^\circ}}$$

$$I = 0.5e^{-j173.1^\circ}$$



## Lecture Problem Solution

The voltage phasor across the inductor is related to the current  $I$  by


$$\begin{aligned}\tilde{V}_L &= j\omega L \tilde{I} \\ &= j4 \times 10^4 \times 2 \times 10^{-4} \times 0.5e^{-j173.1^\circ} \\ &= 4e^{j(90^\circ - 173.1^\circ)} = 4e^{-j83.1^\circ} \quad (\text{V}),\end{aligned}$$

Corresponding Instantaneous Voltage  $V_L(t)$  is:

$$\begin{aligned}v_L(t) &= \Re[\tilde{V}_L e^{j\omega t}] \\ &= \Re[4e^{-j83.1^\circ} e^{j4 \times 10^4 t}] \\ &= 4\cos(4 \times 10^4 t - 83.1^\circ)\end{aligned}$$
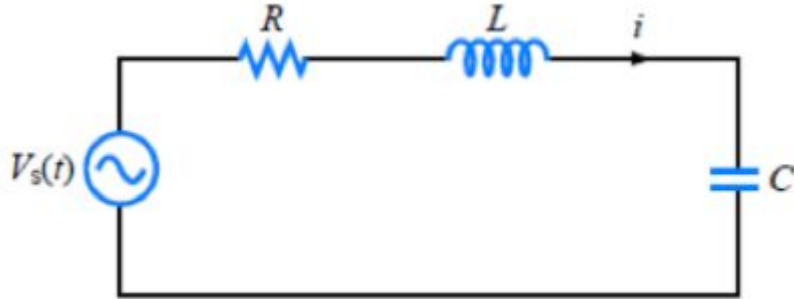
## Problem 33.4 - Phasor Method

A series RLC AC circuit has:  $R = 425\ \Omega$ ,  $L = 1.25\ \text{H}$ ,  $C = 3.50\ \mu\text{F}$ ,  $\omega = 377\ \text{s}^{-1}$ , and  $\Delta V_{\text{max}} = 150\ \text{V}$ .




- Determine the inductive reactance and the capacitive reactance of the circuit.
- Find the impedance and phase angle between the current and voltage.
- Find the maximum current in the circuit.
- Find both the maximum voltage and the instantaneous voltage across each element.



# AC Phasor Analysis

## Step 1


Adopt Cosine Reference  
(Time Domain)

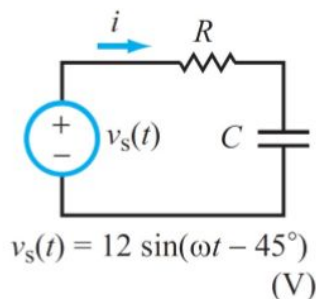
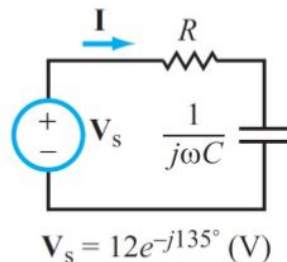
## Step 2

Transfer to Phasor Domain

$$\begin{aligned} i &\rightarrow \mathbf{I} \\ v &\rightarrow \mathbf{V} \\ R &\rightarrow \mathbf{Z}_R = R \\ L &\rightarrow \mathbf{Z}_L = j\omega L \\ C &\rightarrow \mathbf{Z}_C = 1/j\omega C \end{aligned}$$



## Step 3

Cast Equations in  
Phasor Form

$$\mathbf{I} \left( R + \frac{1}{j\omega C} \right) = \mathbf{V}_s$$

(apply Ohm's and Kirchhoff's laws)

## Step 4

Solve for Unknown Variable  
(Phasor Domain)

$$\mathbf{I} = \frac{\mathbf{V}_s}{R + \frac{1}{j\omega C}}$$

## Step 5

Transform Solution  
Back to Time Domain

$$\begin{aligned} i(t) &= \Re \{ \mathbf{I} e^{j\omega t} \} \\ &= I_0 \cos(\omega t - \phi_i) \text{ (A)} \end{aligned}$$



## Example 33.4 Initial Steps

First create the time domain cosine equation for the given circuit using the information given.

$$V_s(t) = \Delta V_{max} \cos(\omega t + \phi)$$

$$V_s(t) = 150 \cos(377t + \phi)$$

Then transfer the equation into the phasor domain.

$$i \rightarrow \tilde{I}$$

$$L \rightarrow Z_L = j\omega L = jX_L$$


$$V_s(t) = \tilde{V} = \Delta V_{max} e^{j\phi}$$

$$C \rightarrow Z_C = \frac{1}{j\omega C} = -jX_C$$

$$R \rightarrow Z_R = R = 425 \, \Omega$$
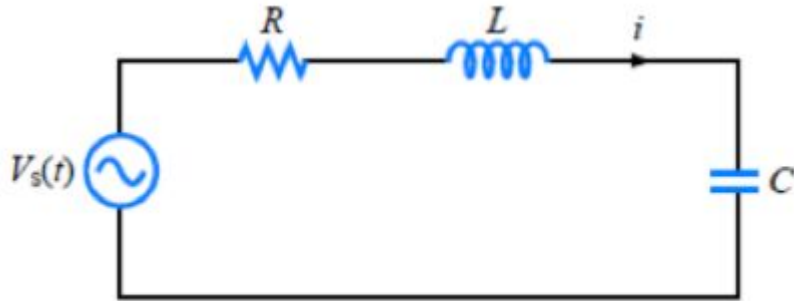
## Example 33.4 Solution to A)

A series RLC AC circuit has:  $R = 425 \, \Omega$ ,  
 $L = 1.25 \, \text{H}$ ,  $C = 3.50 \, \mu\text{F}$ ,  $\omega = 377 \, \text{s}^{-1}$ , and  
 $\Delta V_{\text{max}} = 150 \, \text{V}$ .



- a) Determine the inductive reactance and capacitive reactance of circuit.

$$X_L = \omega L = (377 \text{ s}^{-1})(1.25 \text{ H})$$


$$X_L = 471 \, \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(377 \text{ s}^{-1})(3.50 * 10^{-6} \text{ F})}$$

$$X_C = 758 \, \Omega$$
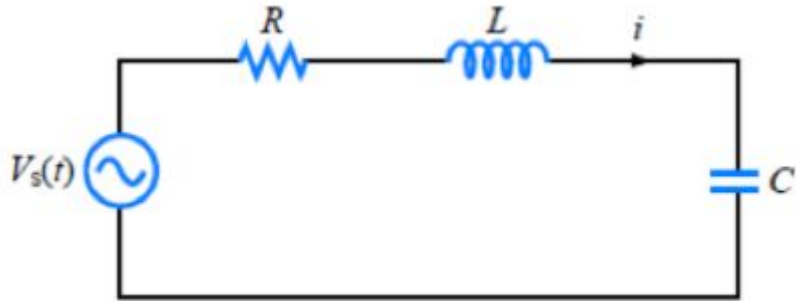
## Example 33.4 Solution to B)

A series RLC AC circuit has:  $R = 425 \, \Omega$ ,  
 $L = 1.25 \, \text{H}$ ,  $C = 3.50 \, \mu\text{F}$ ,  $\omega = 377 \, \text{s}^{-1}$ , and  
 $\Delta V_{\text{max}} = 150 \, \text{V}$ .



- b) Find the impedance and phase angle between current and voltage

$$Z = Z_R + Z_L + Z_C = R + jX_L - jX_C$$

$$Z = 425 + 471j - 758j$$


$$Z = 425 - 287j \, \Omega$$

Convert to phasor using method from before.

$$Z \cong 513 \, \Omega \angle -34.0^\circ$$
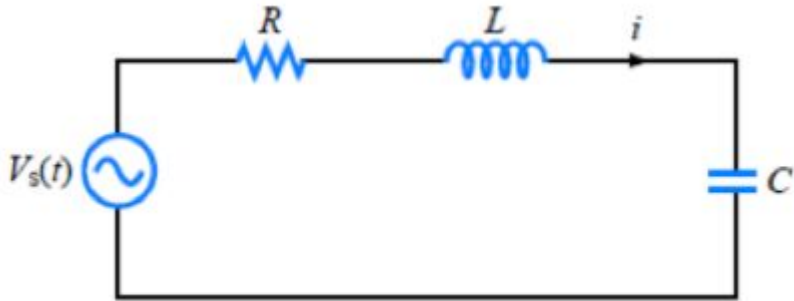
## Example 33.4 Solution to C)

A series RLC AC circuit has:  $R = 425 \, \Omega$ ,  $L = 1.25 \, \text{H}$ ,  $C = 3.50 \, \mu\text{F}$ ,  $\omega = 377 \, \text{s}^{-1}$ , and  $\Delta V_{\text{max}} = 150 \, \text{V}$ .



- c) Find the maximum current by applying Kirchhoff's Rules in phasor form and solve for unknowns.

$$\tilde{V} = V_R + V_L + V_C$$

$$\tilde{I} = (Z_R + Z_L + Z_C) = \tilde{I}Z$$


$$\tilde{I} = \frac{\tilde{V}}{Z}$$

The max current occurs when:  $\tilde{V} = \Delta V_{\text{max}}$

$$\tilde{I}_{\text{max}} = \frac{\Delta V_{\text{max}}}{|Z|} = \frac{150 \, \text{V}}{513 \, \Omega} = 0.292 \, \text{A}$$
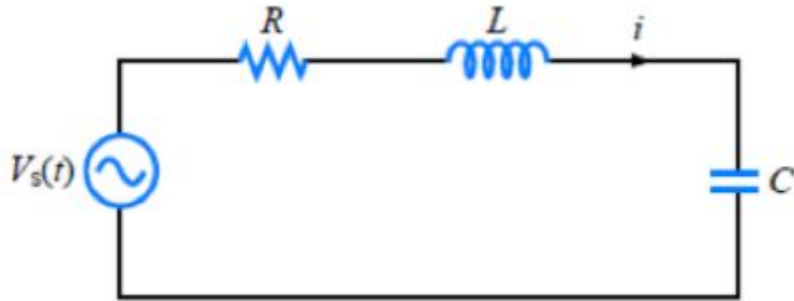
## Example 33.4 Solution to D) Max Voltage

A series RLC AC circuit has:  $R = 425 \, \Omega$ ,  
 $L = 1.25 \, \text{H}$ ,  $C = 3.50 \, \mu\text{F}$ ,  $\omega = 377 \, \text{s}^{-1}$ , and  
 $\Delta V_{\text{max}} = 150 \, \text{V}$ .



- c) Find both the maximum voltage and the instantaneous voltage across each element.

Max voltage occurs when:  $\tilde{I} = \tilde{I}_{\text{max}}$

$$\Delta V_R = \tilde{I}_{\text{max}} Z_R = (0.292 \, \text{A})(425 \, \Omega)$$

$$\Delta V_R = 124 \, \text{V}$$

$$\Delta V_L = \tilde{I}_{\text{max}} Z_L = (0.292 \, \text{A})(471j \, \Omega)$$


$$\Delta V_L = 138j \, \text{V}$$

$$\Delta V_C = \tilde{I}_{\text{max}} Z_C = (0.292 \, \text{A})(-758j \, \Omega)$$

$$\Delta V_C = -222j \, \text{V}$$
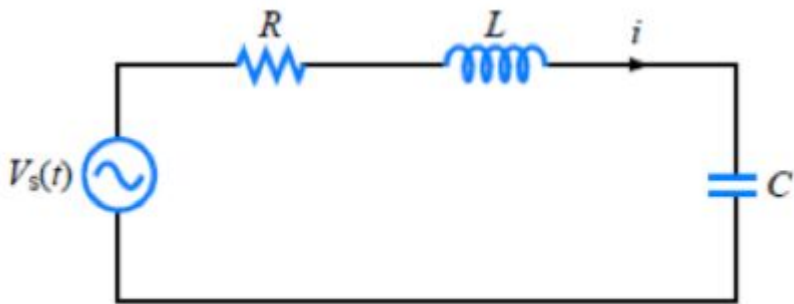
## Example 33.4 Solution to D) Instantaneous Voltage

A series RLC AC circuit has:  $R = 425 \, \Omega$ ,  
 $L = 1.25 \, \text{H}$ ,  $C = 3.50 \, \mu\text{F}$ ,  $\omega = 377 \, \text{s}^{-1}$ , and  
 $\Delta V_{\text{max}} = 150 \, \text{V}$ .



- c) Find both the maximum voltage and the instantaneous voltage across each element.

Transform all solutions back to time domain.

$$v(t) = \Re [V_0 e^{j\phi} e^{j\omega t}] = V_0 \cos(\omega t + \phi)$$


$$\Delta V_R = V_0 e^{j\phi} = 124 \, \text{V}$$

$$\Delta V_L = V_0 e^{j\phi} = 138j = 138e^{j\frac{\pi}{2}} \, \text{V}$$

$$\Delta V_C = V_0 e^{j\phi} = -222j = 222e^{-j\frac{\pi}{2}} \, \text{V}$$
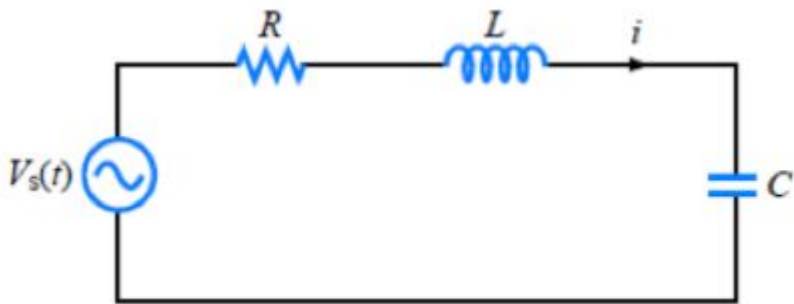
## Example 33.4 Solution to D) Instantaneous Voltage

A series RLC AC circuit has:  $R = 425 \, \Omega$ ,  $L = 1.25 \, \text{H}$ ,  $C = 3.50 \, \mu\text{F}$ ,  $\omega = 377 \, \text{s}^{-1}$ , and  $\Delta V_{\text{max}} = 150 \, \text{V}$ .



- c) Find both the maximum voltage and the instantaneous voltage across each element.

$$v(t) = \Re [V_0 e^{j\phi} e^{j\omega t}] = V_0 \cos(\omega t + \phi)$$

$$v_R(t) = \Re [\Delta V_R e^{j\omega t}] = \Re [124 e^{j377t}]$$

$$v_R(t) = 124 \cos 377t$$

$$v_L(t) = \Re [\Delta V_L e^{j\omega t}] = \Re \left[ 138 e^{\frac{j\pi}{2}} e^{j377t} \right]$$

$$v_L(t) = 138 \sin 377t$$

$$v_C(t) = \Re [\Delta V_C e^{j\omega t}] = \Re \left[ 222 e^{\frac{-j\pi}{2}} e^{j377t} \right]$$

$$v_C(t) = -222 \sin 377t$$





## Example 2.1

A transmission line of length  $l$  connects to a sinusoidal voltage source with an oscillation frequency  $f$ . Assuming that the velocity of wave propagation on the line is  $c$ , for which of the following situations is it reasonable to ignore the presence of the transmission line in the solution of the circuit.

- a)  $l = 20 \text{ cm}, f = 20 \text{ kHz},$
- b)  $l = 50 \text{ km}, f = 60 \text{ Hz}$
- c)  $l = 20 \text{ cm}, f = 600 \text{ MHz},$
- d)  $l = 1 \text{ mm}, f = 100 \text{ GHz},$

## Example 2.1 Solution

Transmission line effects are negligible when  $\frac{l}{\lambda} < 0.01$

It may be necessary to account for both the phase shift due to time delay and the presence of reflected signals that may have bounced back.

The diagram shows the equation  $\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{lf}{c} = \frac{lf}{3 \times 10^8 \text{ m/s}}$  enclosed in a rectangular box. Red arrows point from labels outside the box to the corresponding variables inside:

- Line length** points to  $l$ .
- Wavelength** points to  $\lambda$ .
- Velocity of wave propagation** points to  $u_p$ .
- Speed of light** points to  $c$ .
- Frequency of the oscillating wave** points to  $f$  in the final term of the equation.

$$\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{lf}{c} = \frac{lf}{3 * 10^8 \text{ m/s}}$$

## Example 2.1 Solution

$$a) \quad l = 20 \text{ cm}, f = 20 \text{ kHz} \quad = \frac{lf}{3 * 10^8 \text{ m/s}} = \frac{20 * 10^{-3} \text{ m} * 20 * 10^3 \text{ Hz}}{3 * 10^8 \text{ m/s}} = 1.33 * 10^{-5} \quad \leftarrow \text{negligible}$$

$$b) \quad l = 50 \text{ km}, f = 60 \text{ Hz} \quad = \frac{lf}{3 * 10^8 \text{ m/s}} = \frac{50 * 10^3 \text{ m} * 60 \text{ Hz}}{3 * 10^8 \text{ m/s}} = 0.01 \quad \leftarrow \text{included}$$

$$c) \quad l = 20 \text{ cm}, f = 600 \text{ MHz}, \quad = \frac{lf}{3 * 10^8 \text{ m/s}} = \frac{20 * 10^{-2} \text{ m} * 600 * 10^6 \text{ Hz}}{3 * 10^8 \text{ m/s}} = 0.4 \quad \leftarrow \text{included}$$


$$d) \quad l = 1 \text{ mm}, f = 100 \text{ GHz}, \quad = \frac{lf}{3 * 10^8 \text{ m/s}} = \frac{1 * 10^{-3} \text{ m} * 100 * 10^9 \text{ Hz}}{3 * 10^8 \text{ m/s}} = 0.33 \quad \leftarrow \text{included}$$

## Example 2.4

A 1 GHz parallel-plate transmission line consists of 1.2 cm wide copper strips separated by a 0.15 cm thick layer of polystyrene.

Appendix B gives  $\mu_c = \mu_0 = 4\pi * 10^{-7} \text{ H/m}$  and  $\sigma_c = 5.8 * 10^7 \text{ S/m}$  for copper, and  $\epsilon_r = 2.6$

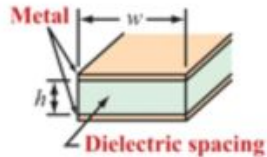for polystyrene. Use Table 2-1 to determine the line parameters of the transmission line. Assume that  $\mu_c = \mu_0$  and  $\sigma \approx 0$  for polystyrene.



## Example 2.4 Solution

From table 2-1, the following parameter formulas can be determined for a parallel-plate:

$$\begin{aligned} R' &= \frac{2R_s}{w} \\ L' &= \frac{\mu h}{w} \\ G' &= \frac{\sigma w}{h} \\ C' &= \frac{\epsilon w}{h} \end{aligned} \quad R_s = \sqrt{\frac{\pi f \mu_c}{\sigma_c}}$$

For copper:

$$\begin{aligned} w &= 1.2 \text{ cm} = 0.012 \text{ m} \\ \mu_c &= \mu_0 = 4\pi * 10^{-7} \text{ H/m} \\ \sigma_c &= 5.8 * 10^8 \text{ S/m} \end{aligned}$$

Other values:

$$\begin{aligned} f &= 1 \text{ GHz} = 1 * 10^9 \text{ Hz} \\ \epsilon &= 8.854 * 10^{-12} \text{ F/m} \end{aligned}$$

For Polystyrene:

$$\begin{aligned} h &= 0.15 \text{ cm} = 0.0015 \text{ m} \\ \mu &= \mu_0 = 4\pi * 10^{-7} \text{ H/m} \\ \sigma &= 0 \\ \epsilon_r &= 2.6 \end{aligned}$$

## Example 2.4 Solution

From table 2-1, the following parameter formulas can be determined for a parallel-plate:

$$\begin{aligned} R' &= \frac{2R_s}{w} & R' &= \frac{2}{w} \sqrt{\frac{\pi f \mu_c}{\sigma_c}} = \frac{2}{1.2 * 10^{-2}} \sqrt{\frac{\pi * 1 * 10^9 * 4\pi * 10^{-7}}{5.8 * 10^7}} = 1.38 \, \Omega/m \\ L' &= \frac{\mu h}{w} & L' &= \frac{\mu h}{w} = \frac{4\pi * 10^{-7} * 0.0015}{0.012} = 1.57 * 10^{-7} \, H/m \\ G' &= \frac{\sigma w}{h} & G' &= \frac{\sigma w}{h} = 0 \, S/m \\ C' &= \frac{\epsilon w}{h} & C' &= \frac{\epsilon w}{h} = \frac{\epsilon_0 \epsilon_r w}{h} = \frac{8.854 * 10^{-12} * 2.6 * 0.012}{0.0015} = 1.84 * 10^{-10} \, F/m \end{aligned}$$