

## ENGPYHS 2A04 Winter 2022 – Assignment 4 Solutions

DUE MONDAY FEBRUARY 14<sup>th</sup>, 8AM

1. Consider a coaxial air line with inner diameter 13 mm, and outer diameter 15 mm. Both conductors are made of copper (refer to your textbook for material constants).
  - a. Compute the transmission line parameters for a signal at 10 kHz.

**Solution:**

$$\text{Copper: } \mu_{Cu} = 1\mu_0 = 4\pi \times 10^{-7} \frac{H}{m}, \sigma_{Cu} = 5.8 \times 10^7 \frac{S}{m}$$

$$a = \frac{13mm}{2} = 6.5mm, b = \frac{15mm}{2} = 7.5mm$$

$$R_S = \sqrt{\frac{\pi f \mu_c}{\sigma_c}} = \sqrt{\frac{\pi(10000)(4\pi \times 10^{-7})}{(5.8 \times 10^7)}} = 2.609 \times 10^{-5}$$

$$R' = \frac{R_S}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right) = \frac{2.609 \times 10^{-5}}{2\pi} \left( \frac{1}{6.5 \times 10^{-3}} + \frac{1}{7.5 \times 10^{-3}} \right) = 1.19 \times 10^{-3} \Omega/m$$

$$L' = \frac{\mu}{2\pi} \ln \left( \frac{b}{a} \right) = \frac{\mu_0}{2\pi} \ln \left( \frac{b}{a} \right) = \frac{4\pi \times 10^{-7}}{2\pi} \ln \left( \frac{7.5}{6.5} \right) = 2.86 \times 10^{-8} H/m$$

$$G' = \frac{2\pi\sigma}{\ln(b/a)} = \frac{2\pi(0)}{\ln(7.5/6.5)} = 0 S/m, \text{ because the insulator is air which has no}$$

conductance.

$$C' = \frac{2\pi\epsilon}{\ln(b/a)} = \frac{2\pi(8.854 \times 10^{-12})}{\ln(7.5/6.5)} = 3.89 \times 10^{-10} F/m$$

- b. Compute the attenuation constant and the phase constant of the transmission line at the specified operating frequency.


**Solution:**

$$\omega = 2\pi f = 2\pi(10000) = 20000\pi$$

$$\begin{aligned} \gamma &= \sqrt{(R' + j\omega L')(G' + j\omega C')} \\ &= \sqrt{(1.19 \times 10^{-3} + j(20000\pi)(2.86 \times 10^{-8}))(0 + j(20000\pi)(3.89 \times 10^{-10}))} \\ &= \sqrt{(1.19 \times 10^{-3} + j1.80 \times 10^{-3})(j2.44 \times 10^{-5})} \\ &= \sqrt{-4.392 \times 10^{-8} + j2.904 \times 10^{-8}} = \sqrt{5.265 \times 10^{-8}} e^{j2.557} \\ &= (5.265 \times 10^{-8})^{0.5} e^{j2.557 \cdot 0.5} = 2.295 \times 10^{-4} e^{j1.279} = 6.6 \times 10^{-5} + j2.2 \times 10^{-4} \\ \alpha &= \Re\{\gamma\} = 6.6 \times 10^{-5} Np/m \end{aligned}$$

$$\beta = \Im\{\gamma\} = 2.2 \times 10^{-4} rad/m$$

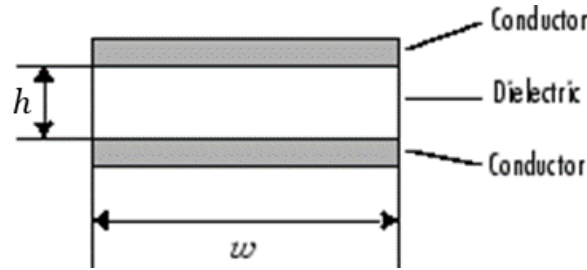2. Calculate the phase velocity of a  $3\text{kHz}$  signal travelling on a parallel-plate transmission line. Assume the conductors are gold, and assume the dielectric is air. The conductors are  $5\text{mm}$  wide, separated by a  $2\text{mm}$  dielectric. Does this value make sense?



**Solution:**

Because of the resistances of the conductors and the dielectric,  $G' = 0$ . This results in:

$$\beta = \Im m \left\{ \sqrt{(R' + j\omega L')(j\omega C')} \right\} = \Im m \left\{ \sqrt{(j\omega R' - \omega^2 L')(C')} \right\} = \Im m \left\{ \sqrt{(j\omega R' C' - \omega^2 L' C')} \right\}$$

From  $L' C' = \mu \epsilon$ :

$$\beta = \Im m \left\{ \sqrt{j\omega R' C' - \omega^2 \mu \epsilon} \right\}$$

Substituting in expressions for  $R'$  and  $C'$ :

$$\beta = \Im m \left\{ \sqrt{j\omega \frac{2R_s \epsilon w}{w h} - \omega^2 \mu \epsilon} \right\} = \Im m \left\{ \sqrt{j\omega \frac{2R_s \epsilon}{h} - \omega^2 \mu \epsilon} \right\} = \Im m \left\{ \sqrt{j\omega \frac{2\sqrt{\pi f \mu_c / \sigma_c \epsilon}}{h} - \omega^2 \mu \epsilon} \right\}$$

Inputting the known values:


$$\begin{aligned} \beta &= \\ &= \Im m \left\{ \sqrt{j(2\pi(3 \times 10^3)) \frac{2\sqrt{\pi(3 \times 10^3)(4\pi \times 10^{-7})/(4.1 \times 10^7)} 8.854 \times 10^{-12}}{2 \times 10^{-3}} - (2\pi(3 \times 10^3))^2 \mu_0 \epsilon_0} \right\} \\ &= \Im m \left\{ \sqrt{j(18849.6) \frac{2(1.6996 \times 10^{-5}) 8.854 \times 10^{-12}}{2 \times 10^{-3}} - (3.553 \times 10^8)(4\pi \times 10^{-7})(8.854 \times 10^{-12})} \right\} \\ &= \Im m \left\{ \sqrt{j2.837 \times 10^{-9} - 3.953 \times 10^{-9}} \right\} = \Im m \left\{ \sqrt{10^{-9}(-3.953 + j2.837)} \right\} \\ &= \Im m \left\{ \sqrt{(4.8657 \times 10^{-9}) e^{j2.5191}} \right\} = \Im m \{ 6.975 \times 10^{-5} e^{j1.2596} \} \\ &= \Im m \{ 2.136 \times 10^{-5} + j6.64 \times 10^{-5} \} = 6.64 \times 10^{-5} \text{ rad/s} \end{aligned}$$

Calculating phase velocity based on this:

$$u_p = \frac{\omega}{\beta} = \frac{2\pi f}{6.64 \times 10^{-5}} = \frac{2\pi(3000)}{6.64 \times 10^{-5}} = 2.84 \times 10^8 \text{ m/s}$$

Yes, it makes sense because it is slightly less than the speed of light in a vacuum.

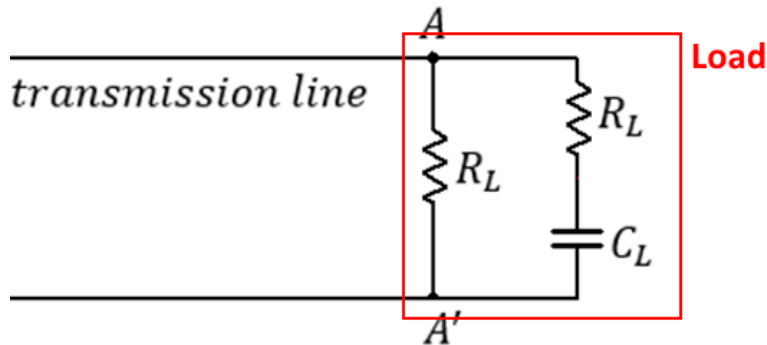3. The following load is placed at the end of a  $120\Omega$  transmission line carrying a 2MHz signal, with  $R_L = 80\Omega$  and  $C_L = 11nF$ :



Calculate the voltage reflection coefficient at the load, and report it in polar form. Explain the meaning of this coefficient.

**Solution:**

Calculate the impedance of the load.

$$\begin{aligned} Z_{load} &= \left( \frac{1}{R_L} + \frac{1}{R_L + Z_C} \right)^{-1} = \left( \frac{1}{R_L} + \frac{1}{R_L - \frac{j}{\omega C}} \right)^{-1} = \left( \frac{1}{R_L} + \frac{1}{R_L - \frac{j}{2\pi f C}} \right)^{-1} \\ &= \left( \frac{1}{80} + \frac{1}{80 - \frac{j}{2\pi(2 \times 10^6)(11 \times 10^{-9})}} \right)^{-1} = \left( 0.0125 + \frac{1}{80 - j7.234} \right)^{-1} \\ &= (0.0125 + (0.01240 + j1.121 \times 10^{-3}))^{-1} = (0.0249 + j1.121 \times 10^{-3})^{-1} \\ &= 40.1 - j1.805 = 40.1e^{-j0.0450} \end{aligned}$$

Next, compute the normalized load impedance.

$$z_L = \frac{Z_{Load}}{Z_0} = \frac{40.1e^{-j0.0450}}{120} = 0.334e^{-j0.0450} = 0.334 - j0.0150 \Omega$$

From here, the voltage reflection coefficient can be computed.

$$\Gamma = \frac{z_L - 1}{z_L + 1} = \frac{0.334 - j0.0150 - 1}{0.334 - j0.0150 + 1} = \frac{-0.666 - j0.0150}{1.334 - j0.0150} = 0.5e^{-j3.1}$$

**This coefficient gives the ratio of amplitudes of the reflected and incident voltage waves.**

4. A 10-metre section of a  $100\Omega$  lossless transmission line is driven by a source with  $v_g(t) = 12 \cos\left(2\pi \times 10^6 t - \frac{\pi}{3}\right)$  (V), and  $Z_g = 150\Omega$ . The line has relative permittivity  $\epsilon_r = 2.1$ , and is terminated by a load with impedance  $Z_L = (120 - j40)\Omega$ . Express complex values in polar form. Determine:
- $\lambda$  on the line.
  - The reflection coefficient at the load.
  - The input impedance.
  - The input voltage  $\tilde{V}_i$ .
  - The time-domain input voltage  $v_i(t)$ .

**Solution:**

a) Lossless, so  $u_p = \frac{c}{\sqrt{\epsilon_r}} = \frac{3 \times 10^8}{\sqrt{2.1}} = 2.07 \times 10^8 \text{ m/s}$ . Then,

$$\lambda = \frac{2\pi u_p}{\omega} = \frac{2\pi(2.07 \times 10^8)}{2\pi \times 10^6} = 207 \text{ m}$$

b) The reflection coefficient is given by:

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(120 - j40) - 100}{(120 - j40) + 100} = \frac{20 - j40}{220 - j40} = 0.12 - j0.16 = 0.2e^{-j0.927} (\Omega)$$

c) First need to find  $\beta l$ :

$$\beta = \frac{\omega}{u_p} = \frac{2\pi \times 10^6}{2.07 \times 10^8} = 0.00966\pi \left(\frac{\text{rad}}{\text{m}}\right)$$

$$\beta l = 0.03035(10) = 0.0966\pi \text{ (rad)}$$

$$Z_i = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} = 100 \frac{(120 - j40) + j100 \tan 0.3035}{100 + j(120 - j40) \tan 0.3035} = 93.62 - j38.98 = 101.4e^{-j0.395} \Omega$$

d) Now that input impedance is found:

$$\widetilde{V}_i = \frac{\widetilde{V}_g Z_i}{Z_g + Z_i} = \frac{12e^{-j\frac{\pi}{3}} 101.4e^{-j0.395}}{150 + 101.4e^{-j0.395}} = \frac{1216.8e^{-j1.442}}{246.7e^{-j0.1588}} = 4.9e^{-j1.28}$$

e) Converting the above to time domain:

$$\begin{aligned} v_i(t) &= \Re\{\widetilde{V}_i e^{j\omega t}\} = \Re\{4.9e^{-j1.28} e^{j\omega t}\} = \Re\{4.9e^{j(\omega t - 1.28)}\} \\ &= 4.9 \cos(2\pi \times 10^6 t - 1.28) \end{aligned}$$

5. Using McMaster's library catalogue, Google Scholar, or some other resource, find an academic paper that discusses an application of transmission lines. In fewer than 5 sentences, summarize the paper's topic, and **explain how it is related to the transmission line theory covered in class**. Cite your source using IEEE, APA, or some comparable format.
6. BONUS: In addition to not dissipating power, a lossless line has two important features: (1) it is dispersionless ( $u_p$  independent of frequency), and (2) its characteristic impedance  $Z_0$  is purely real. Sometimes, it is not possible to design a transmission line such that  $R' \ll \omega L'$  and  $G' \ll \omega C'$ , but it is possible to choose the dimensions of the line and its material properties to satisfy the condition

$$R'C' = L'G' \quad (\text{distortionless line})$$

Such a line is called a *distortionless* line, because despite the fact that it is not lossless, it nonetheless possesses the previously mentioned features of the lossless line. Show that for a distortionless line:

$$\begin{aligned} \alpha &= R' \sqrt{\frac{C'}{L'}} = \sqrt{R'G'} \\ \beta &= \omega \sqrt{L'C'} \end{aligned}$$

$$Z_0 = \sqrt{\frac{L'}{C'}}$$

**Solution:** Using the distortionless condition in Eq. (2.22) gives

$$\begin{aligned}\gamma = \alpha + j\beta &= \sqrt{(R' + j\omega L')(G' + j\omega C')} \\ &= \sqrt{L'C'} \sqrt{\left(\frac{R'}{L'} + j\omega\right) \left(\frac{G'}{C'} + j\omega\right)} \\ &= \sqrt{L'C'} \sqrt{\left(\frac{R'}{L'} + j\omega\right) \left(\frac{R'}{L'} + j\omega\right)} \\ &= \sqrt{L'C'} \left(\frac{R'}{L'} + j\omega\right) = R' \sqrt{\frac{C'}{L'}} + j\omega \sqrt{L'C'}.\end{aligned}$$

Hence,

$$\alpha = \Re(\gamma) = R' \sqrt{\frac{C'}{L'}}, \quad \beta = \Im(\gamma) = \omega \sqrt{L'C'}, \quad u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{L'C'}}.$$

Similarly, using the distortionless condition in Eq. (2.29) gives

$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} = \sqrt{\frac{L'}{C'}} \sqrt{\frac{R'/L' + j\omega}{G'/C' + j\omega}} = \sqrt{\frac{L'}{C'}}.$$

## ASSIGNMENT SUBMISSION INSTRUCTIONS

- Each question is worth equal points, except for bonus questions.
- Show all your work for full marks.
- Clearly label your name and student number at the top of the first page of your assignment.
- All assignments should be submitted in pdf format to the assignments drop box on Avenue to Learn.
- No late assignments will be accepted. A grade of 0% will be given for late assignments. If you have completed part of the assignment, submit the portion you have completed before the deadline for partial marks.