

# Lecture 11: Field Effect Transistors (FETs) (2)


MOSFET structure, Characteristics and parameters, Biasing of MOSFET, examples

# MOSFET Transistor

The metal oxide semiconductor FET uses an insulated gate to isolate the gate from the channel. Two types are the enhancement mode (E-MOSFET) and the depletion mode (D-MOSFET).

An E-MOSFET has no channel until it is induced by a voltage applied to the gate, so it operates only in enhancement mode. An  $n$ -channel type is illustrated here; a positive gate voltage induces the channel.

## E-MOSFET

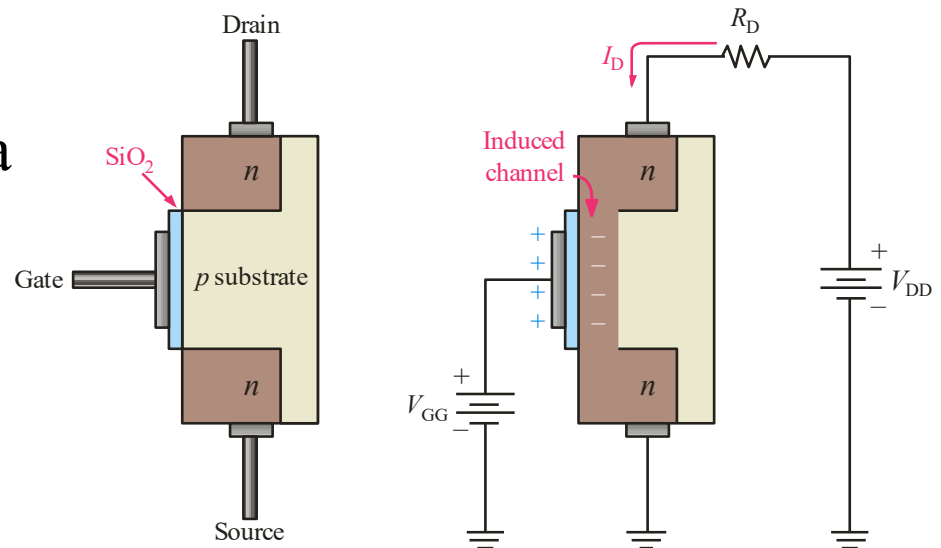


# D-MOSFET

The D-MOSFET has a channel that can be controlled by the gate voltage. For an  $n$ -channel type, a negative voltage depletes the channel; and a positive voltage enhances the channel.


A D-MOSFET can operate in either mode, depending on the gate voltage.

## D-MOSFET

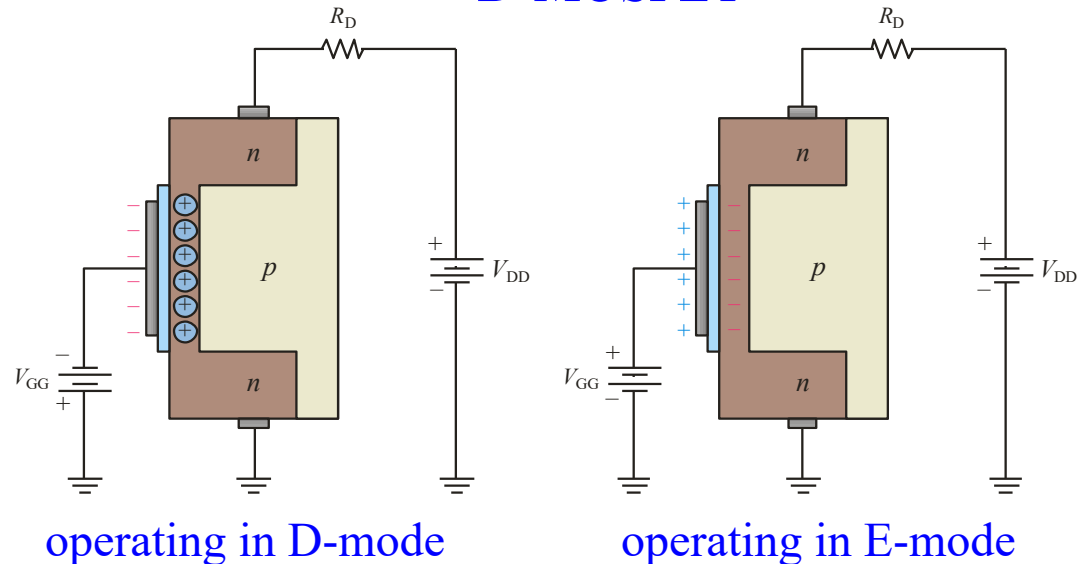
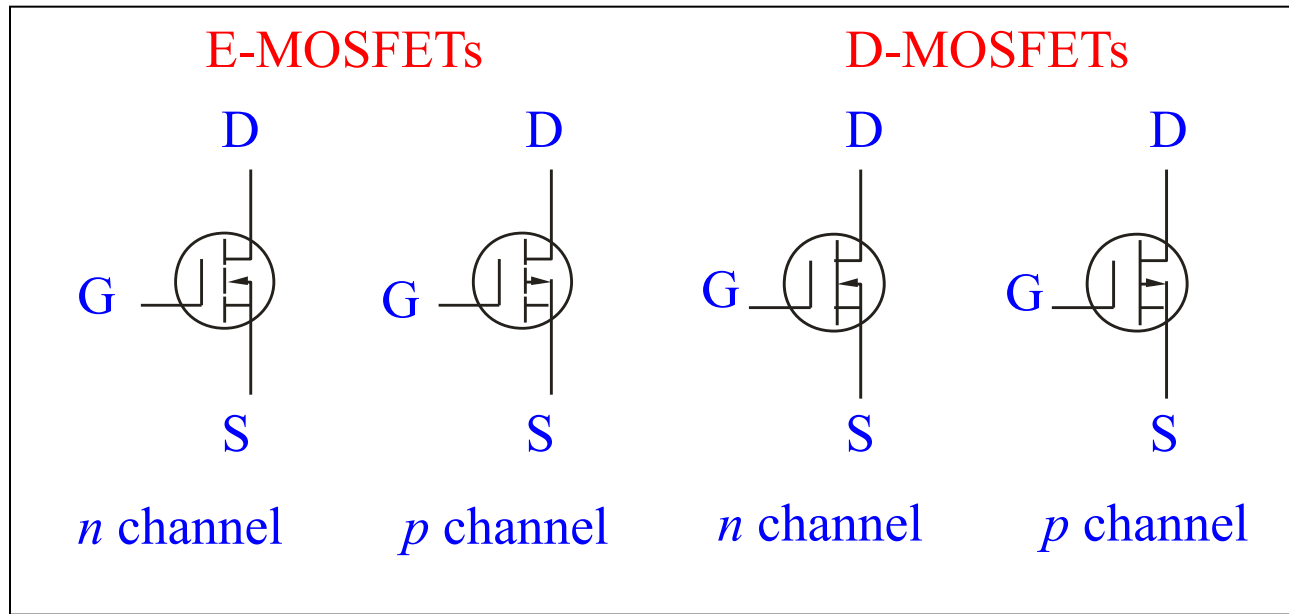
# Circuit Symbols of MOSFETs


MOSFET symbols are shown. Notice the broken line representing the E-MOSFET that has an induced channel. The  $n$  channel has an inward pointing arrow.


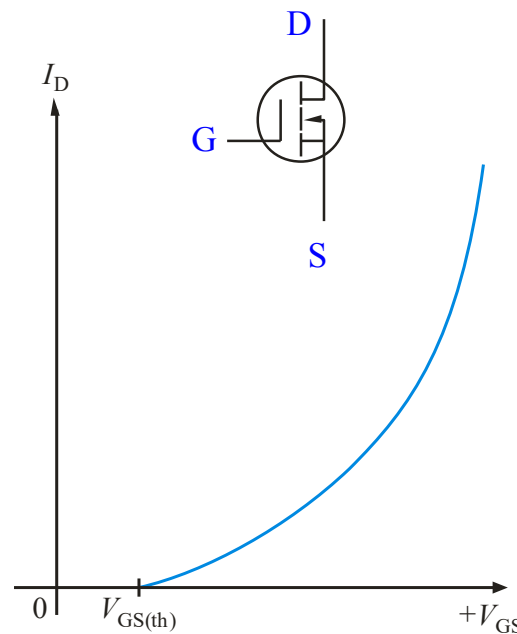
# Transfer Curves of E-MOSFET

The transfer curve for a MOSFET has the same parabolic shape as the JFET but the position is shifted along the  $x$ -axis. The transfer curve for an  $n$ -channel E-MOSFET is entirely in the first quadrant as shown

The curve starts at  $V_{GS(th)}$ , which is a nonzero voltage that is required to have channel conduction. The equation for the drain current is  $I_D = K(V_{GS} - V_{GS(th)})^2$



# Example for E-MOSFET Drain Current

**Problem 1:** The datasheet for an E-MOSFET gives  $I_{D(ON)} = 500 \text{ mA}$  (minimum) at  $V_{GS} = 10 \text{ V}$  and  $V_{GS(th)} = 1 \text{ V}$ . Determine the drain current for  $V_{GS} = 5 \text{ V}$ .

**Solution 1:**

$$K = \frac{I_{D(ON)}}{(V_{GS} - V_{GS(th)})^2}$$


$$I_{D(ON)} = I_{D1}$$

$$K = \frac{500 \text{ mA}}{(10 \text{ V} - 1 \text{ V})^2} = 6.17 \text{ mA/V}^2$$

Using  $V_{GS} = 5 \text{ V}$ ,

$$I_{D2} = K(V_{GS} - V_{GS(th)})^2 = (6.17 \text{ mA/V}^2)(5 \text{ V} - 1 \text{ V})^2$$
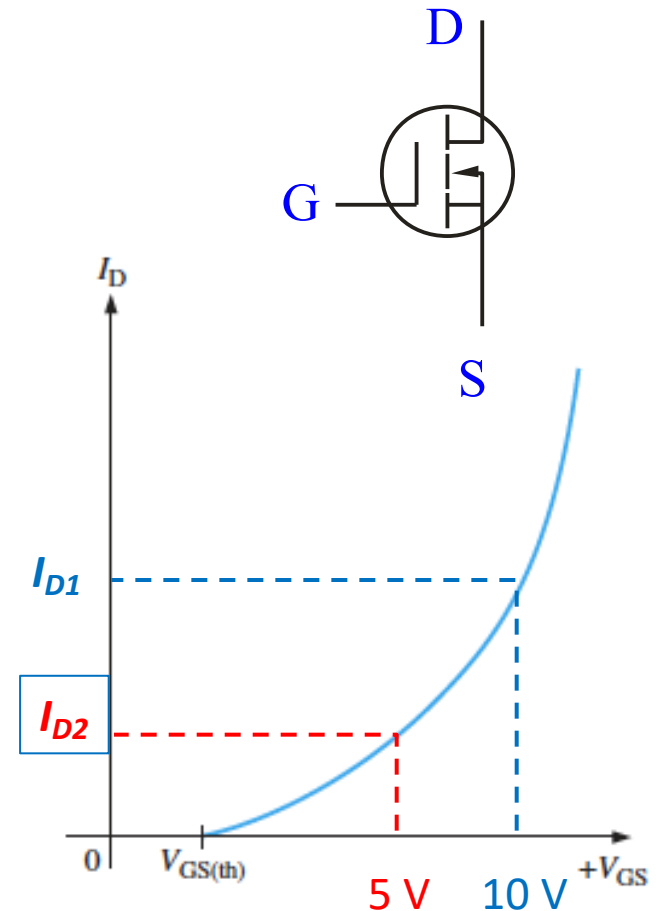
$$I_{D2} = (6.17 \text{ mA/V}^2)(5 \text{ V} - 1 \text{ V})^2 = 98.7 \text{ mA}$$




# Transfer Curves of D-MOSFET

Recall that the D-MOSFET can be operated in either mode. For the  $n$ -channel device illustrated, operation to the left of the  $y$ -axis means it is in depletion mode; operation to the right means it is in enhancement mode.

As with the JFET,  $I_D$  is zero at  $V_{GS(off)}$ . When  $V_{GS}$  is 0, the drain current is  $I_{DSS}$ , which for this device is *not* the maximum current. The equation for drain current is
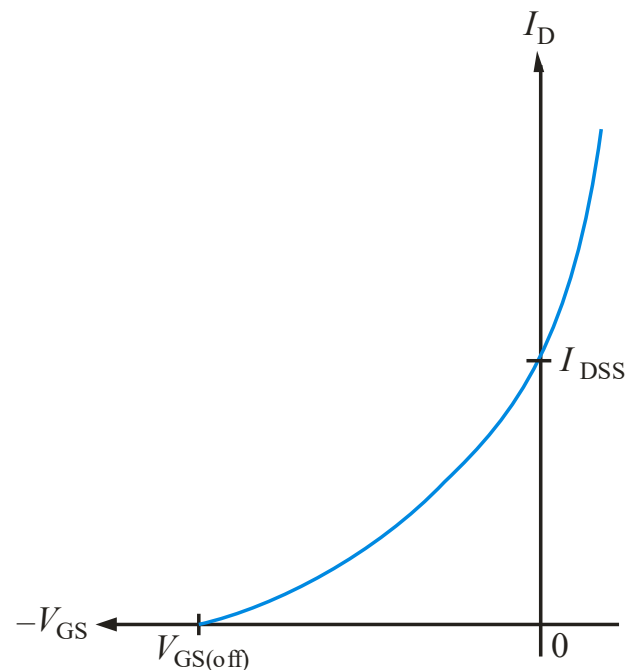
$$I_D \cong I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$



# Example for D-MOSFET Drain Current

**Problem 2:** For a certain D-MOSFET,  $I_{DSS} = 10 \text{ mA}$  and  $V_{GS(off)} = -8 \text{ V}$ . Is this an n-channel or a p-channel? Calculate  $I_D$  at  $V_{GS} = \pm 3 \text{ V}$ .

## Solution 2:

This is an n-channel MOSFET because it has negative  $V_{GS}$ .


$$I_{D1} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

$$I_{D1} = 10 \text{ mA} \times \left( 1 - \frac{-3 \text{ V}}{-8 \text{ V}} \right)^2$$

$$I_{D1} = 3.91 \text{ mA}$$

$$I_{D2} = 10 \text{ mA} \times \left( 1 - \frac{+3 \text{ V}}{-8 \text{ V}} \right)^2$$


$$I_{D2} = 18.9 \text{ mA}$$

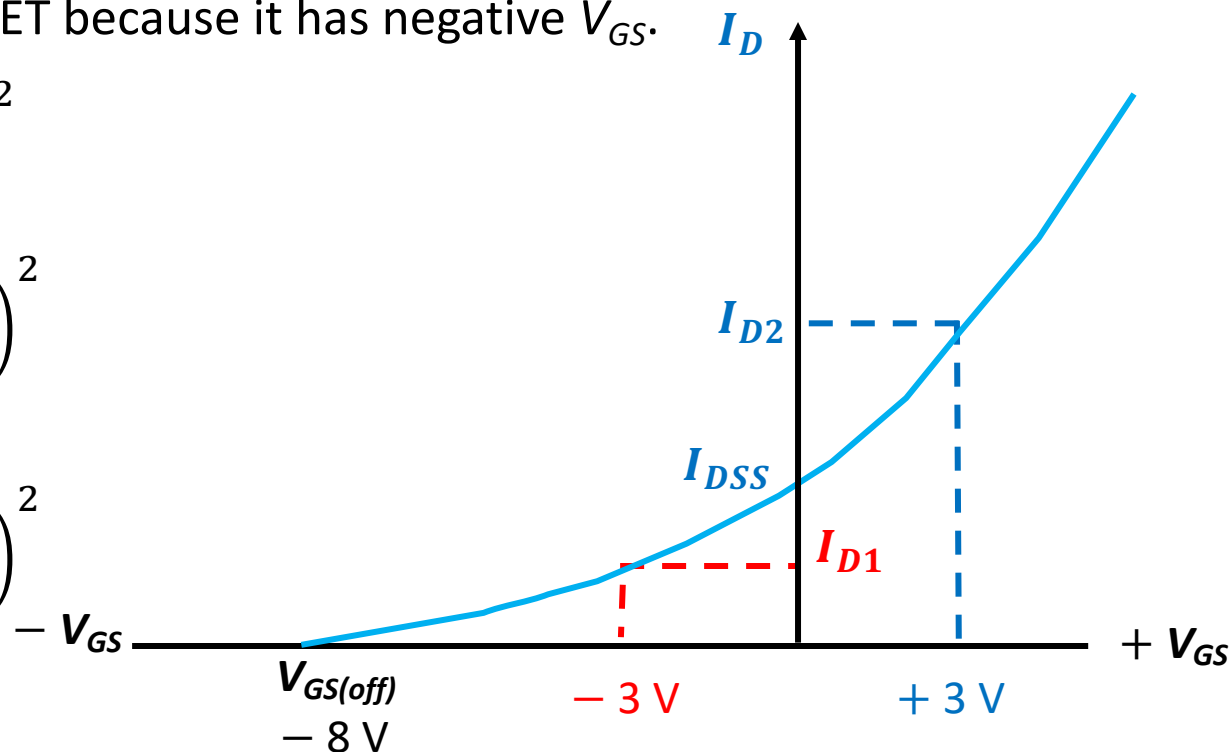



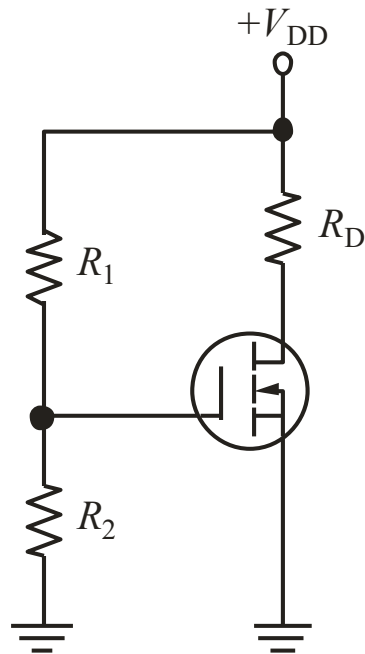
# Biasing of E-MOSFET

E-MOSFETs can be biased using bias methods like the JFETs and BJTs. Voltage-divider bias and drain-feedback bias are illustrated for  $n$ -channel devices.



Voltage-divider bias

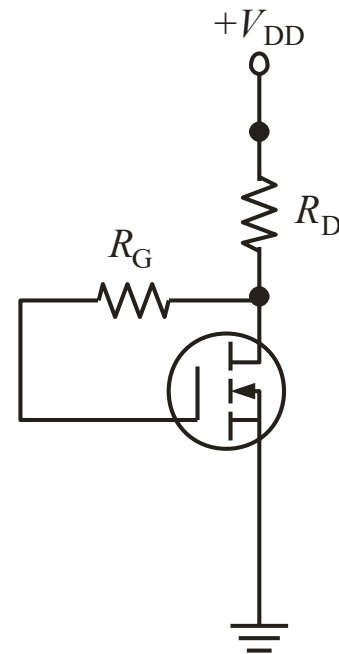

Drain-feedback bias

# Example for Drain Current and $V_{DS}$

**Problem 3:** The datasheet for this E-MOSFET shows that  $I_D = 10 \text{ mA}$  when  $V_{GS} = V_{DS}$ . Find  $I_D$  and  $V_{DS}$ .

## Solution 3:


Since no current flows in  $R_G$

$$V_{GS} = V_{DS} \quad I_D = 10 \text{ mA}$$

$$V_{DS} = V_{DD} - I_D R_D$$


$$V_{DS} = 20 \text{ V} - 10 \text{ mA} \times 1 \text{ k}\Omega = 10 \text{ V}$$

$$V_{DS} = V_{GS} = 10 \text{ V}$$

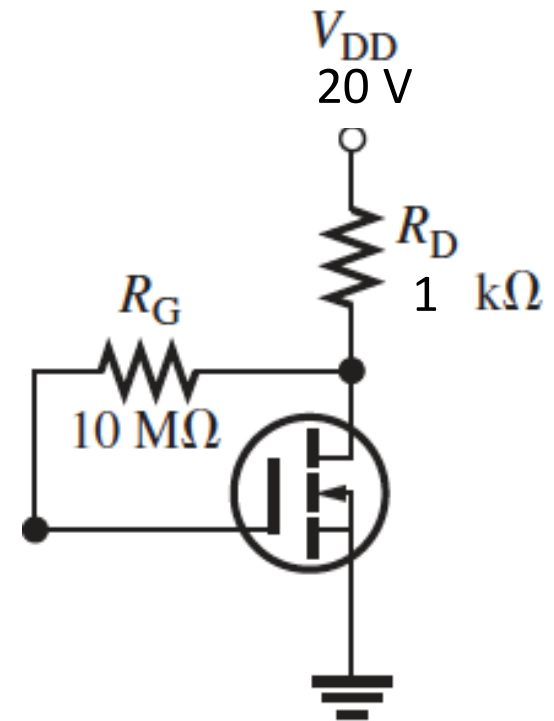
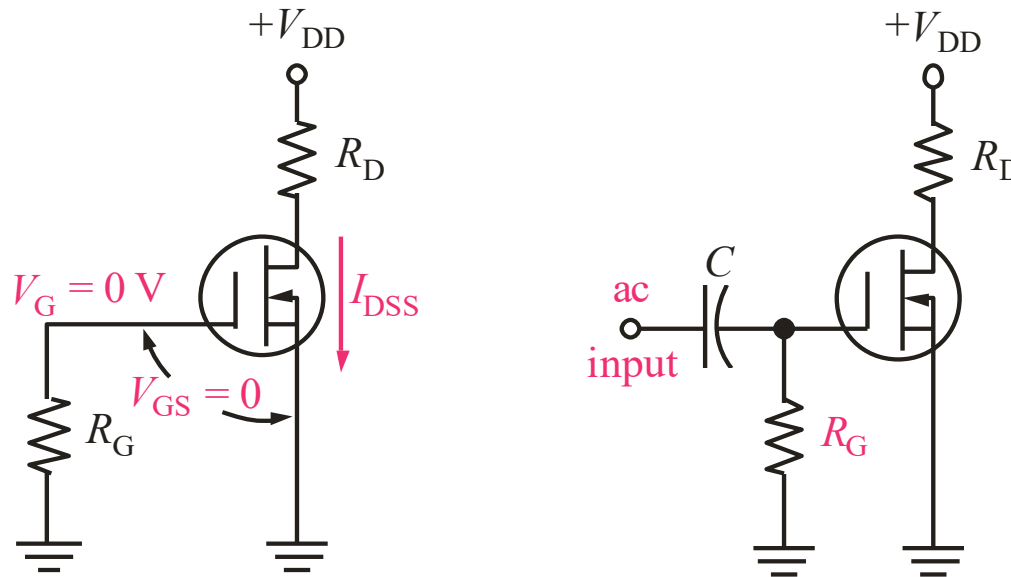
# Biasing of a D-MOSFET

The simplest way to bias a D-MOSFET is with zero bias. This works because the device can operate in either depletion or enhancement mode, so the gate can go above or below 0 V.



# Example for Drain to Source Voltage

**Problem 4:** Determine the drain-to-source voltage in the given circuit. The MOSFET datasheet gives  $V_{GS(off)} = -8\text{ V}$  and  $I_{DSS} = 12\text{ mA}$ .

## Solution 4:

No current flows in  $R_G$

$$V_{GS} = 0 \quad I_D = I_{DSS}$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_{DS} = 18\text{ V} - 12\text{ mA} \times 620\Omega = 10.56\text{ V}$$

$$V_{DS} = 10.56\text{ V}$$

