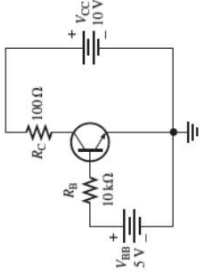



Example for Transistor's Parameters

Problem 1: Determine I_B , I_C , I_E , V_{BE} , V_{CE} , and V_{CE} in the circuit given below. The transistor has a $\beta_{DC} = 150$.




Example for Current Gain


Problem 2: Sketch an ideal family of collector curves for the shown transistor with $\beta_{DC} = 100$ for I_B varying from 5 μA to 25 μA .

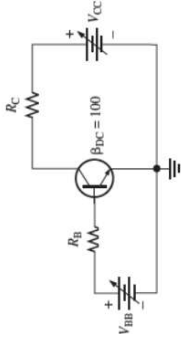

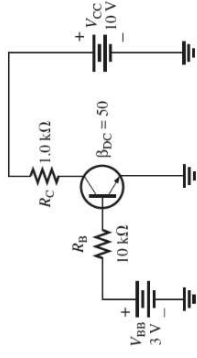
Problem 1: Determine whether or not the following BJT transistor is in saturation. Assume $V_{CE(sat)} = 0.2 \text{ V}$.




Problem 2: (a) For the transistor circuit given below, what is V_{CE} when $V_{IN} = 0 \text{ V}$?
 (b) What minimum value of I_B is required to saturate this transistor if β_{DC} is 200? Neglect $V_{CE(sat)}$.
 (c) Calculate the maximum value of R_B that will put the transistor in saturation assuming $\beta_{DC} = 200$ when $V_{IN} = 5 \text{ V}$.

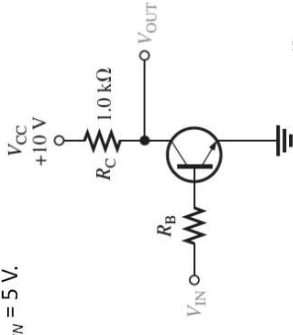


Problem 1: Determine V_{CE} and I_C in the shown voltage-divider biased transistor circuit if $\beta_{DC} = 100$, and $V_{CE(sat)} = 0.2 \text{ V}$. Is this transistor in saturation?

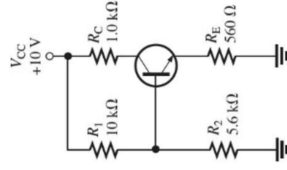


Problem 2: Determine the Q-point (I_C , V_{CE}) for the shown circuit if $\beta_{DC} = 200$ and $V_{CE(sat)} = 0.2 \text{ V}$.

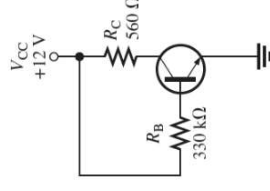

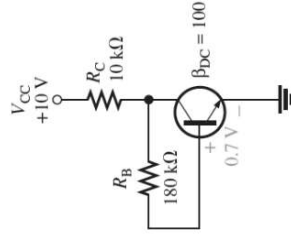Problem 3: Find the Q-point values (I_C and V_{CE}) for the given circuit if $\beta_{DC} = 100$ and $V_{CE(sat)} = 0.2 \text{ V}$.



Problem 1: Determine the Q-point for the circuit given below and draw the dc load line. Find the maximum peak value of base current and collector current to avoid distortion. Assume $V_{CE(sat)} = 0$, and $\beta_{DC} = 200$

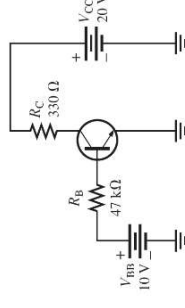

Problem 2: Determine the r'_e of a transistor that is operating with a dc emitter current of 1.62 mA.