 


Stepper Motor ASIP

- We will build a simple ASIP that has instruction set specifically aimed at controlling stepper motors
- Instruction set
 - Move motor by a number of (half-)steps
 - Pause between moves
 - Add/subtract, branch, set registers, move data between registers
 - To support loops
 - Move motor to an absolute position (bonus)

Real-World Example

- Such controllers are actually sold as real products



- STP100 motor controller from Pontech
- Contains motor drivers (H bridges)
 - We will build ours on the protoboard

ASIP Requirements

- We want to build a microprocessor whose instruction set directly supports stepper motor control
 - Move motor clockwise/counter-clockwise by a number of steps/half-steps (all combinations)
 - Automatically pause between moves to accommodate the motor's inertia
 - Keep track of motor position
 - Move motor to a desired position (optional)
 - Explicit “pause” instruction
 - Other common instructions to support basic loops

ASIP Architecture

- Very simple
 - 8-bit instructions and data
 - Instruction ROM
 - Register file with 4 registers
 - 2 general purpose (R0 and R1)
 - 2 special purpose
 - R2 – stores motor's position (in half steps)
 - R3 – determines delay between steps/half-steps
 - Stepper ROM
 - Stores the basic sequence of signals used to drive the motor
 - ALU
 - Performs basic computation
 - Delay logic
 - Implements delay between steps
 - PC, decoder, branch logic, multiplexers

ASIP Instruction Set

- `MOVR reg`
 - Move the motor by a number of full steps specified in the register
 - The number in the register is **signed**, so the motor can move in either direction
 - After each step, wait for the amount of time specified in the `delay` register before proceeding
- `MOVRHS reg`
 - Move the motor by a number of half-steps specified in a register
 - All other requirements are the same as for `MOVR`

ASIP Instruction Set...

- PAUSE
 - Wait for the amount of time specified inside the delay register
- CLR reg
 - Clear (i.e. set to 0) the specified register
- ADDI reg, imm3
 - Add the 3-bit **unsigned** immediate operand to the specified register; store the result into the register
- SUBI reg, imm3
 - Subtract the 3-bit **unsigned** immediate operand from the specified register; store the result into the register

ASIP Instruction Set...

- `SR0 imm4`
 - Set (fill) 4 lower bits of register 0 with the 4-bit immediate operand
- `SRH0 imm4`
 - Set (fill) 4 higher bits of register 0 with the 4-bit immediate operand
- `MOV regd, regs`
 - Move the content of the `regs` (source) register into `regd` (destination) register

ASIP Instruction Set...

- BR imm5
 - Branch (unconditionally) to $PC + imm5$, where PC is current program counter and imm5 is **signed** 5-bit immediate
- BRZ imm5
 - If register R0 is zero, branch to $PC + imm5$, where PC is current program counter and imm5 is **signed** 5-bit immediate

ASIP Instruction Set...

- `MOVA reg`
 - Move the motor to an absolute position specified in the register
 - If the number in the register is different from the current position (R2) move the motor in an appropriate direction until they are the same
 - May involve a combination of steps and half-steps
 - After each step (or half-step), wait for the amount of time specified in the `delay` register before proceeding
 - BONUS
 - If you implement this instruction, you get 1% bonus
 - We will not include it in the class discussion

Instruction Encoding

- Instructions are encoded as binary numbers
- I = immediate
- R = register
- R_s = source register
- R_D = destination register

1	0	0	I	I	I	I	I	BR imm5
1	0	1	I	I	I	I	I	BRZ imm5
0	0	0	I	I	I	R	R	ADDI reg, imm3
0	0	1	I	I	I	R	R	SUBI reg, imm3
0	1	0	0	I	I	I	I	SR0 imm4
0	1	0	1	I	I	I	I	SRH0 imm4
0	1	1	0	0	0	R	R	CLR reg
0	1	1	1	R _D	R _D	R _S	R _S	MOV regd, regs
1	1	0	0	0	0	R	R	MOVA reg (BONUS)
1	1	0	0	0	1	R	R	MOVR reg
1	1	0	0	1	0	R	R	MOVRHS reg
1	1	1	1	1	1	1	1	PAUSE

Instruction Encoding Example

- ADDI R1,5

0	0	0	I	I	I	R	R
---	---	---	---	---	---	---	---

- R1 → 01

- 5 → 101

- ADDI R1,5 → 00010101 = 0x13
-

- BR -3

1	0	0	I	I	I	I	I
---	---	---	---	---	---	---	---

- -3 → 11101

- BR -3 → 10011101 = 0x9D
-

- MOVR R0

1	1	0	0	0	1	R	R
---	---	---	---	---	---	---	---


- R0 → 00

- MOVR R0 → 11000100 = 0xC4

Implementing the ASIP

- Create FSMD
- Draw datapath
 - Write Verilog
- Create FSM for the controller
 - Write Verilog
- Put them together
 - Write Verilog
- Test and debug
- You will be given quite a bit of skeleton code, to save you time on unnecessary typing

Creating FSMD

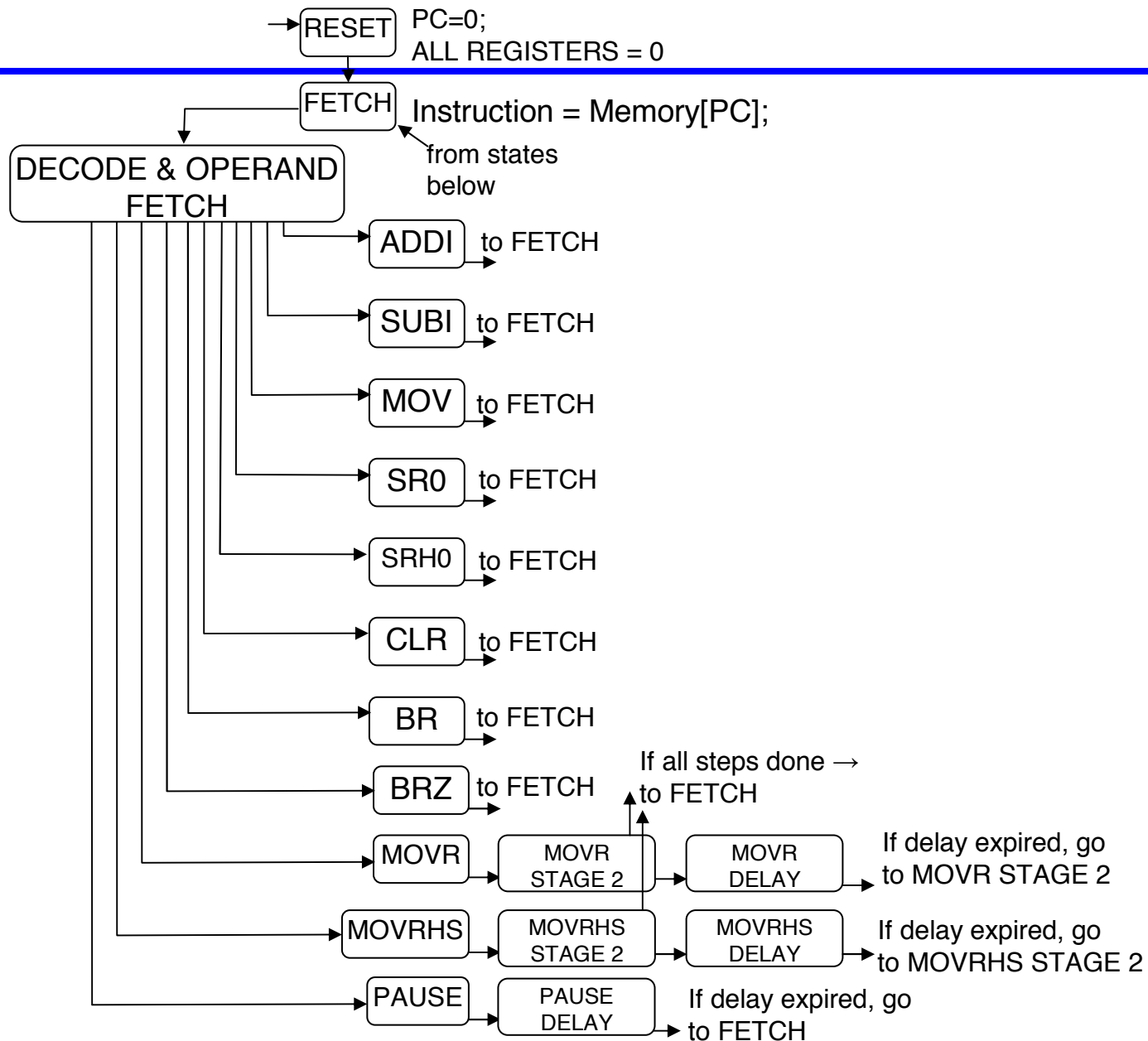

FSMD Operations

- Need to specify the actions taken in each stage of the FSMD
 - Based on previous description of the instructions

- Examples

- `ADDI reg, imm3`

- `SUBI reg, imm3`

ADDI

$\text{RF}[\text{reg}] \leftarrow \text{RF}[\text{reg}] + \text{imm3}$
 $\text{PC} \leftarrow \text{PC} + 1$

SUBI

$\text{RF}[\text{reg}] \leftarrow \text{RF}[\text{reg}] - \text{imm3}$
 $\text{PC} \leftarrow \text{PC} + 1$

- `RF[reg]` means register `reg` in the register file (RF)

FSMD Operations...

- MOV regd, regs

MOV

$RF[regd] \leftarrow RF[regs]$
 $PC \leftarrow PC + 1$

SR0 imm4

SR0

$RF[0] \leftarrow \{RF[0]_{7:4}, imm4\}$
 $PC \leftarrow PC + 1$

- SRH0 imm4

SRH0

$RF[0] \leftarrow \{imm4, RF[0]_{3:0}\}$
 $PC \leftarrow PC + 1$

CLR reg

CLR

$RF[reg] \leftarrow 0$
 $PC \leftarrow PC + 1$

- BR imm5

BR

$PC \leftarrow PC + sext(imm5)$


BRZ imm5

BRZ

if ($RF[0] == 0$)
 $PC \leftarrow PC + sext(imm5)$
else
 $PC \leftarrow PC + 1$


FSMD Operations...

- PAUSE

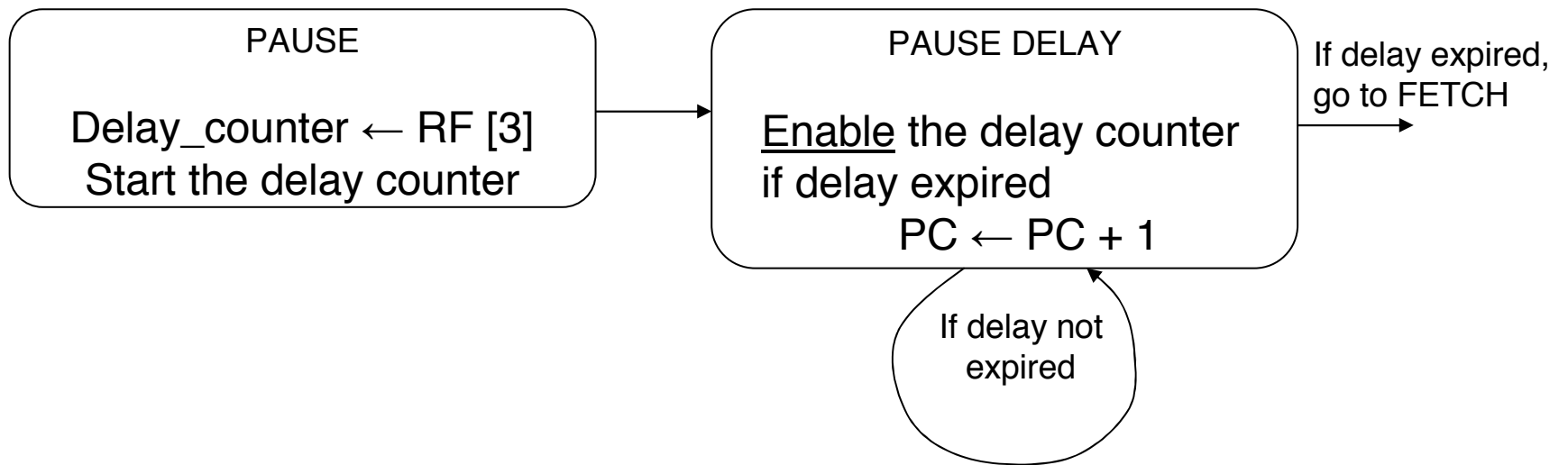


FSMD Operations...

- MOVR reg

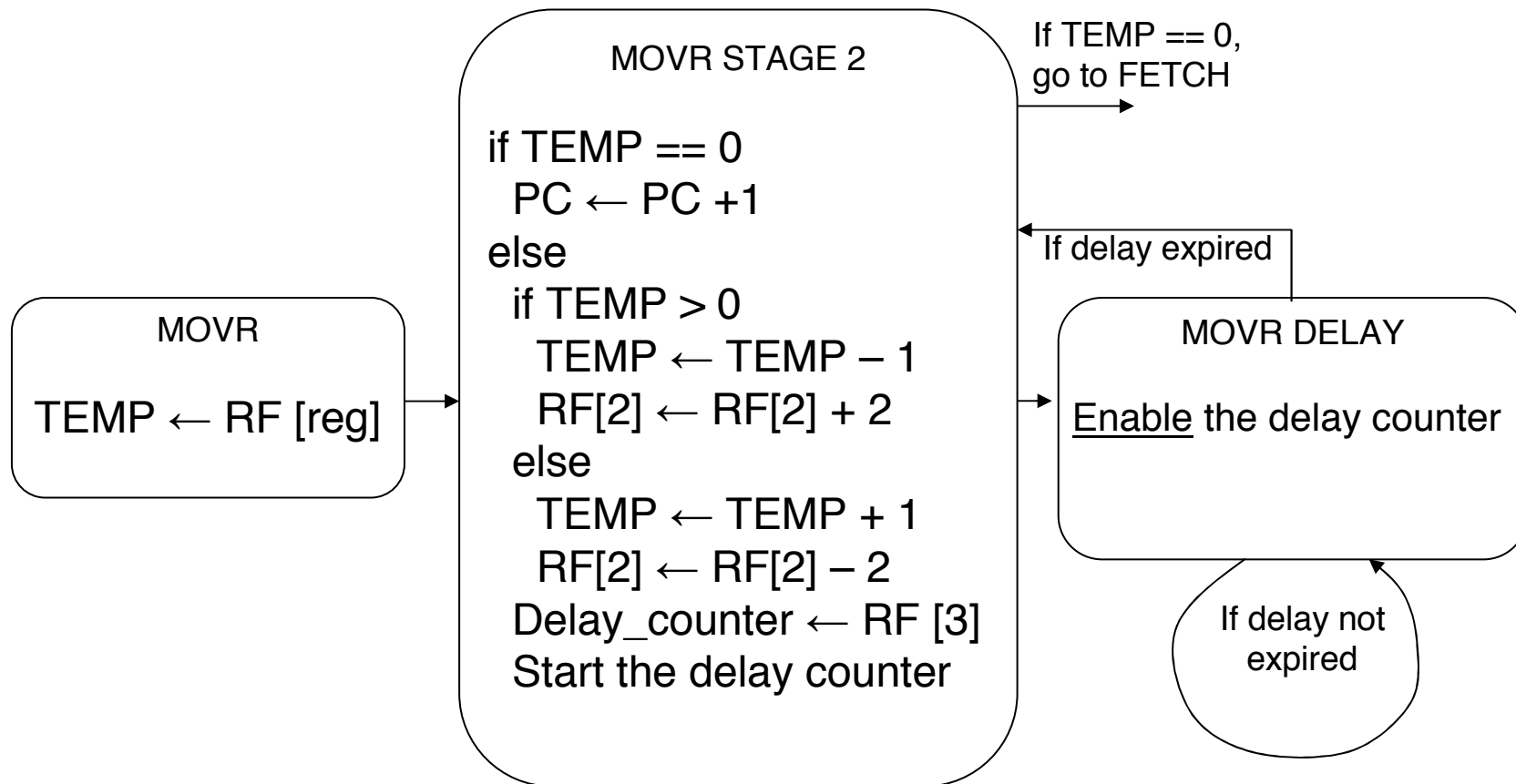

FSMD Operations...

- MOVRHS reg

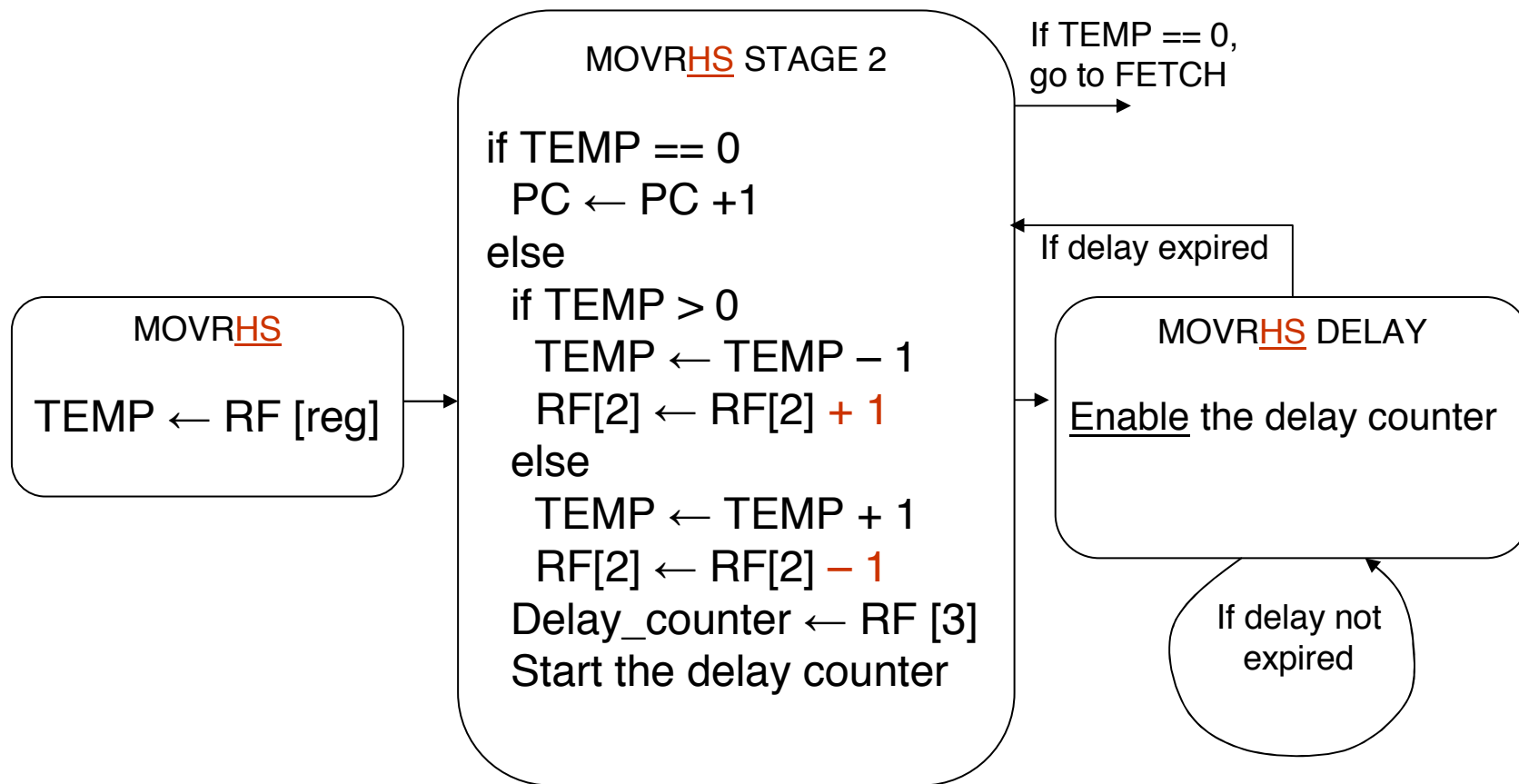


Datapath

- FSMD is complete
- We need to develop datapath that can implement this FSMD
- We could follow the procedure provided in Vahid
 - Many circuit components
 - We will partly follow this procedure, but will simplify things where possible


Datapath: PC

 - Fetching instructions
 - Need a program counter and instruction memory
 - Program counter should be able to count by 1 (be able to increment itself) and be loaded with a new value (on branch)




Datapath: Decode and Operand Fetch

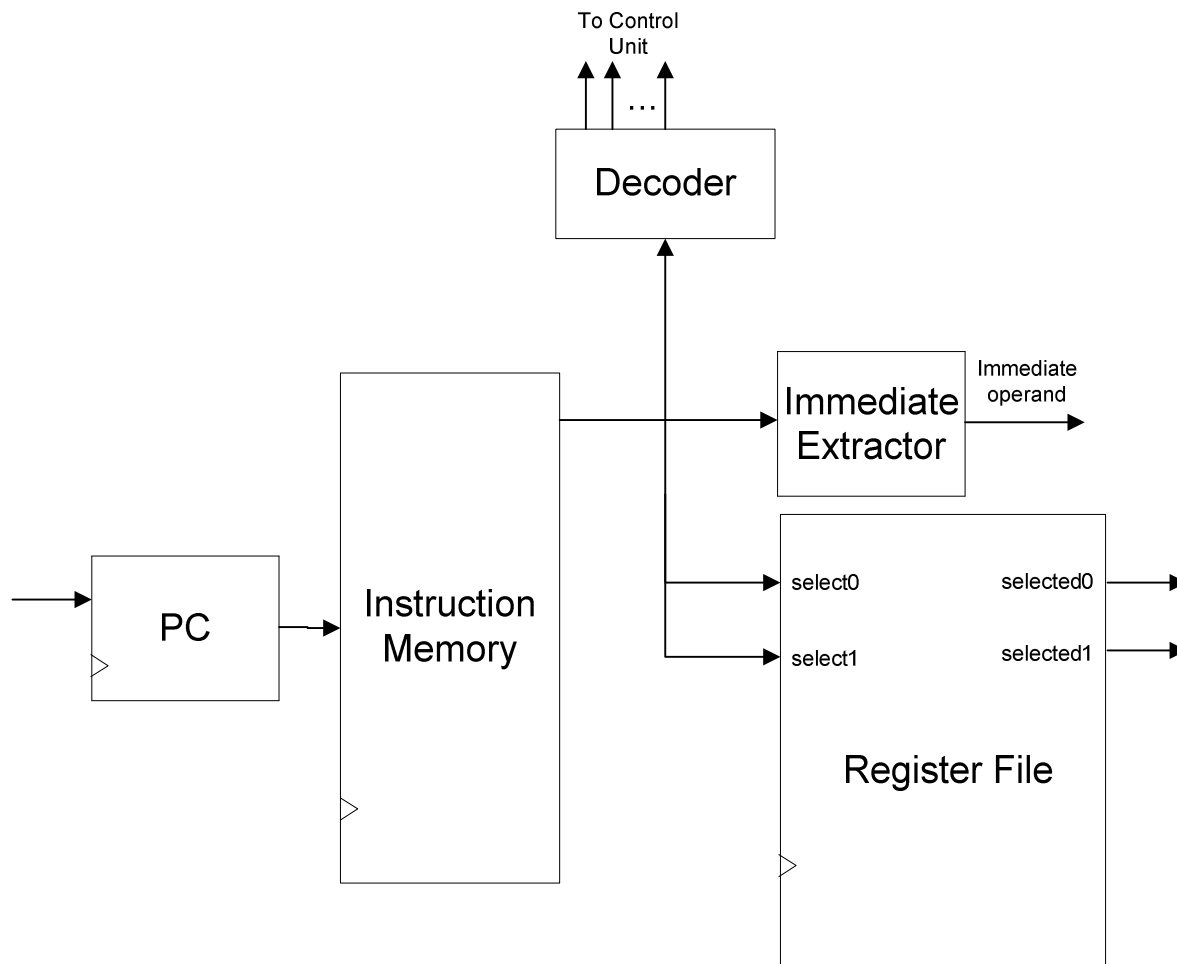- Once the instruction is fetched, it should be decoded and operands should be fetch




Datapath: Computation

 - We will have one ALU for most of computing tasks
 - ALU stands for Arithmetic and Logic Unit
 - Our unit should be able to
 - Add (for ADDI, BR, BRZ, MOVR, MOVRHS)
 - Subtract (for SUBI, MOVR, MOVRHS)
 - Set lower 4 bits of a register (for SR0)
 - Set higher 4 bits of a register (for SRH0)




Datapath: Operand Selection

 - ALU computes many different operations
 - Also on different operands
 - Need multiplexers to choose one of several possible operands
- *Operand a* can be
 - PC (for BR)
 - Register specified by the instruction (for ADDI, SUBI,...)
 - Special register
 - R2 (i.e. RF[2], which contains position, for MOVR, MOVRHS)
 - R0 (for SR0, SRH0)




Datapath: Operand Selection...

 - *Operand b* can be
 - Register specified by the instruction (for MOVA – bonus)
 - Immediate (for ADDI, SUBI,...)
 - Constant value 1 (for MOVRHS)
 - Constant value 2 (for MOVR)




Datapath: ALU + Muxes

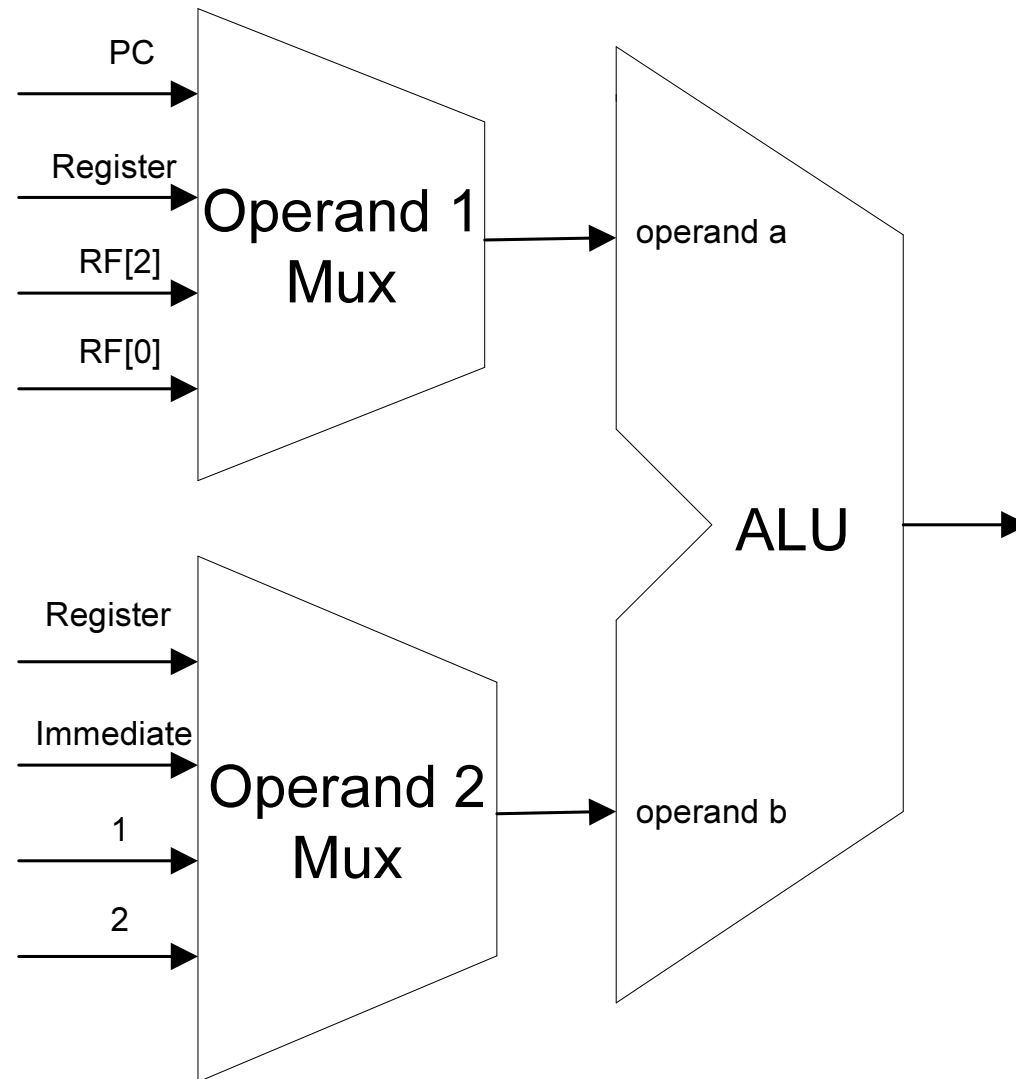

Datapath: Computation

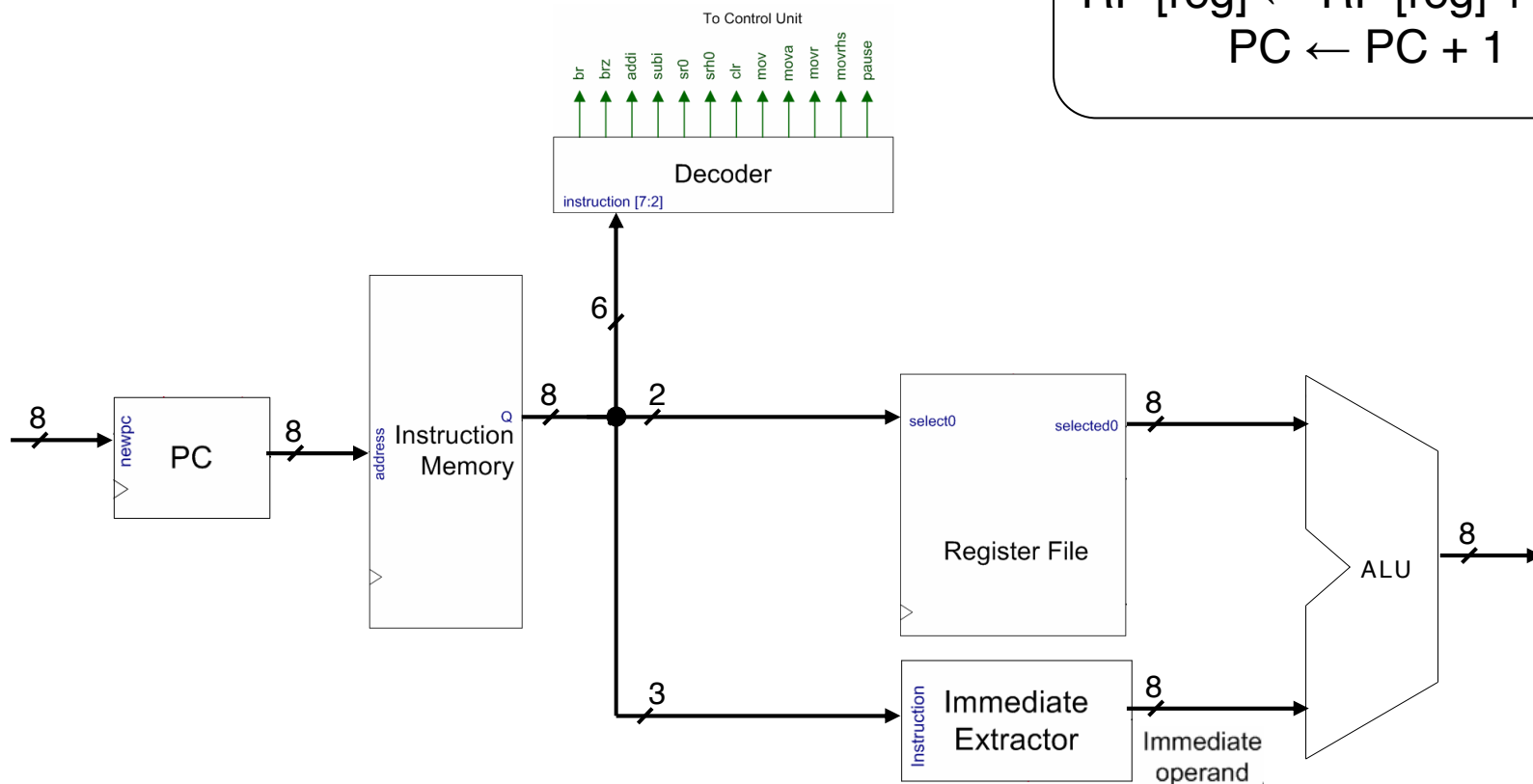- One ALU will perform all functions
 - ADDI reg, imm3
 - For ADDI it will perform addition




ADDI

$$\text{RF}[\text{reg}] \leftarrow \text{RF}[\text{reg}] + \text{imm3}$$
$$\text{PC} \leftarrow \text{PC} + 1$$

Datapath: Writing the Result

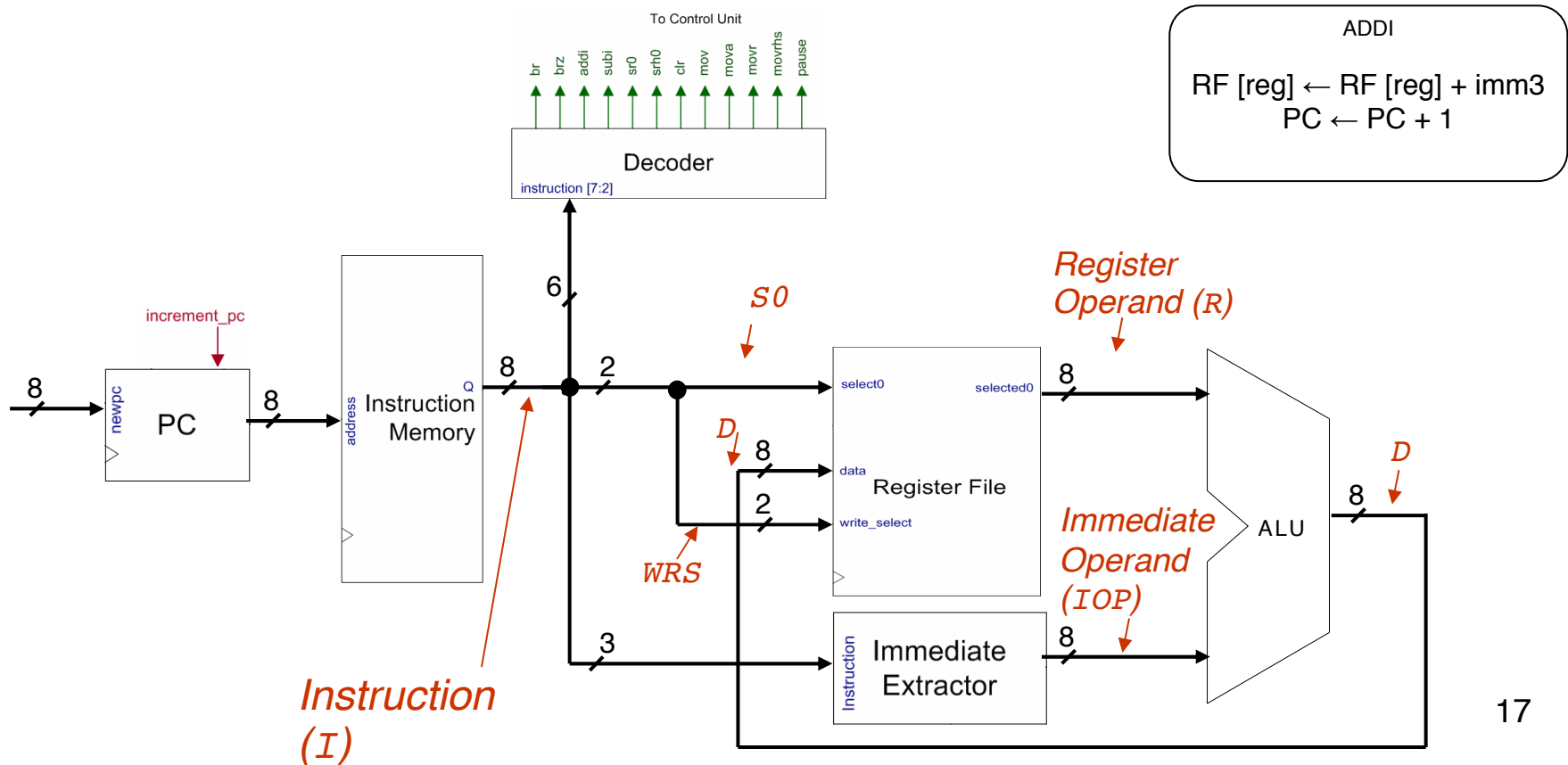- ADDI reg, imm3
- The result is written back to the same register




ADDI: Cycle by Cycle

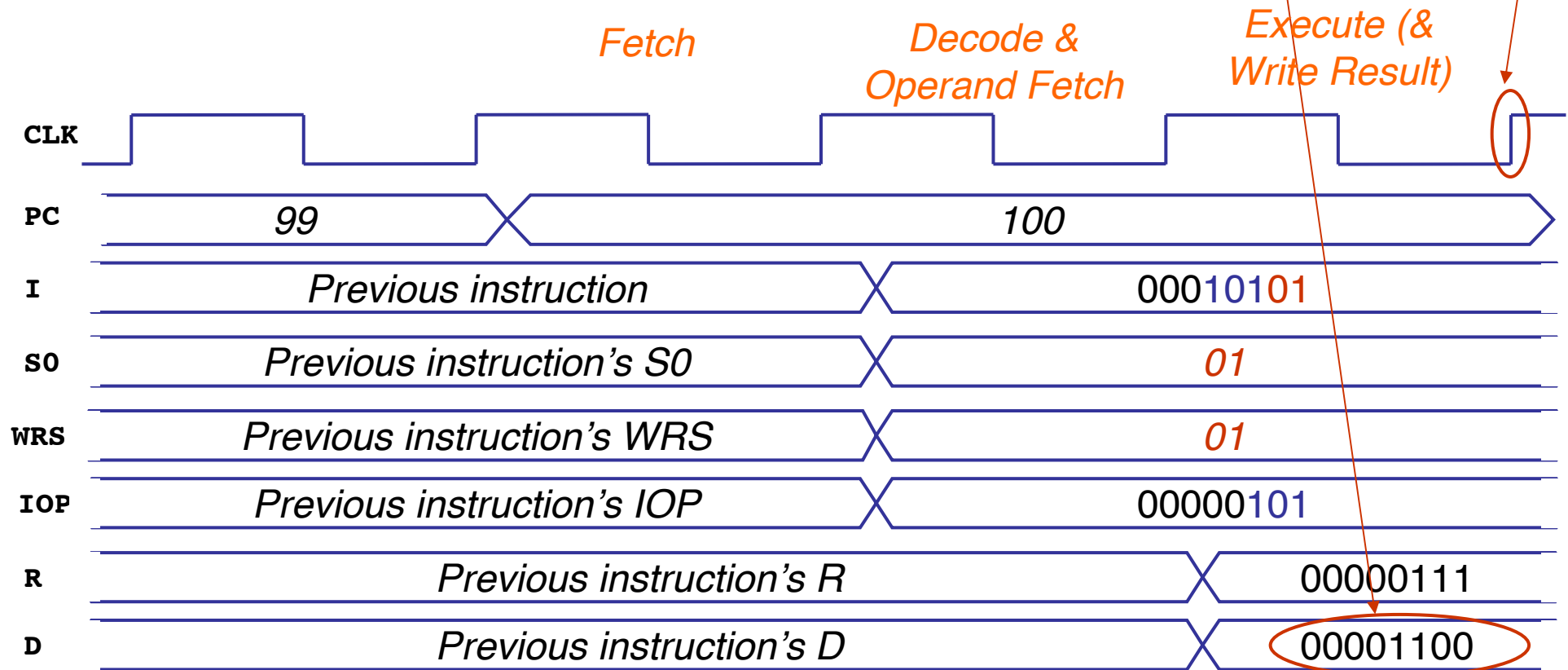- Example: Execute instruction ADDI R1,5 at memory address 100


- Assume that R1 contained 7 before this instruction executes
- ADDI R1,5 → 00010101

Result gets written on this positive clock edge




Datapath: BRZ

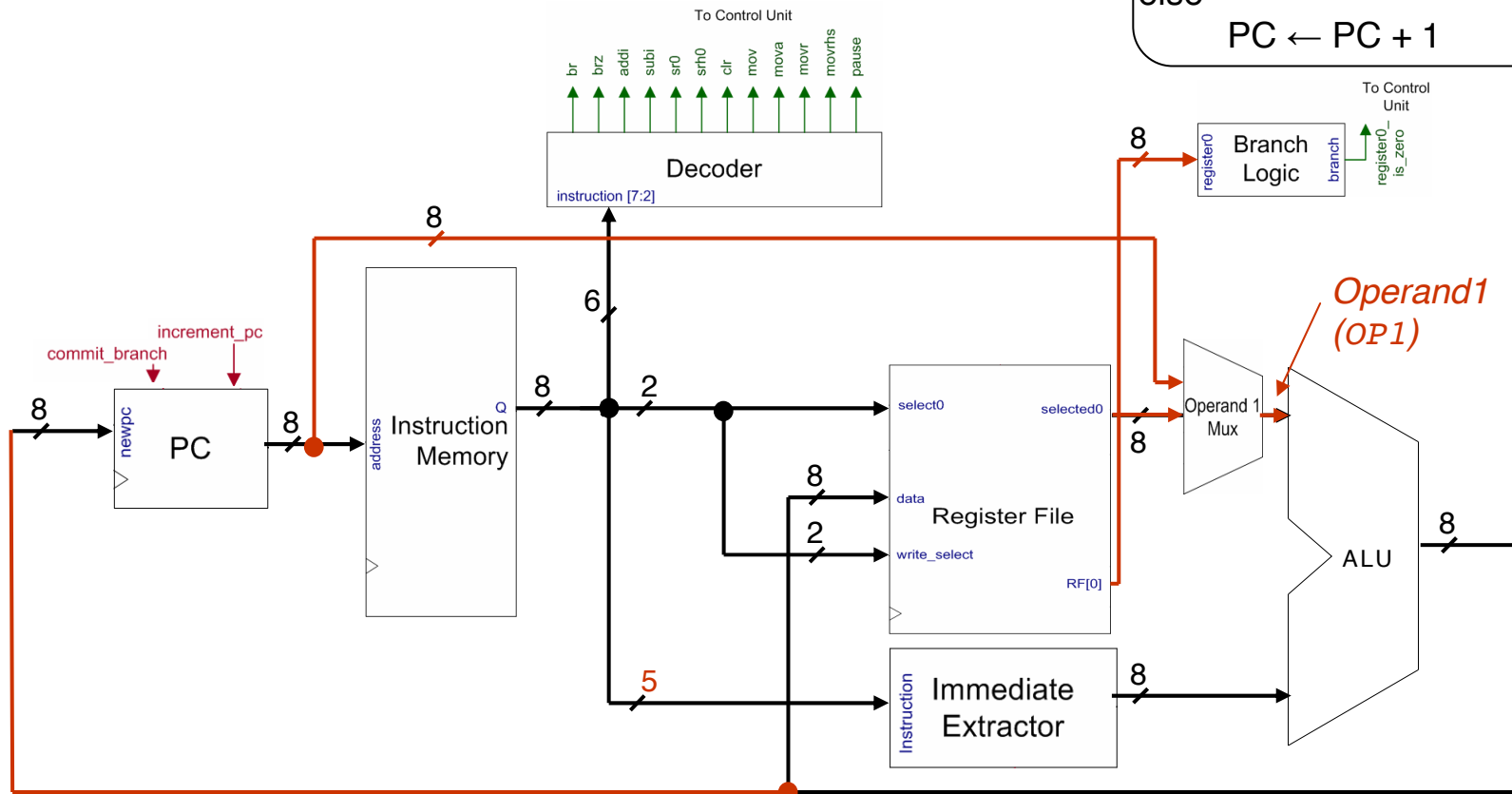
- What do we need to add to the datapath to implement the BRZ instruction
 - BRZ imm5



BRZ: Cycle by Cycle (Branch Taken)

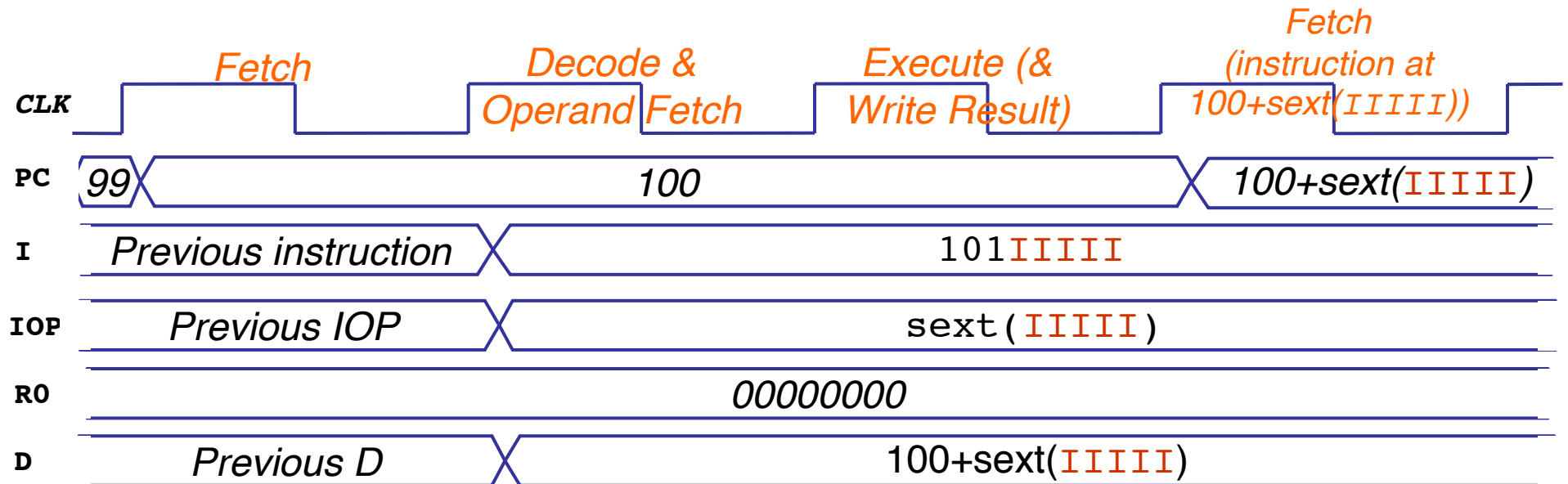


BRZ: Cycle by Cycle (Branch Not Taken)

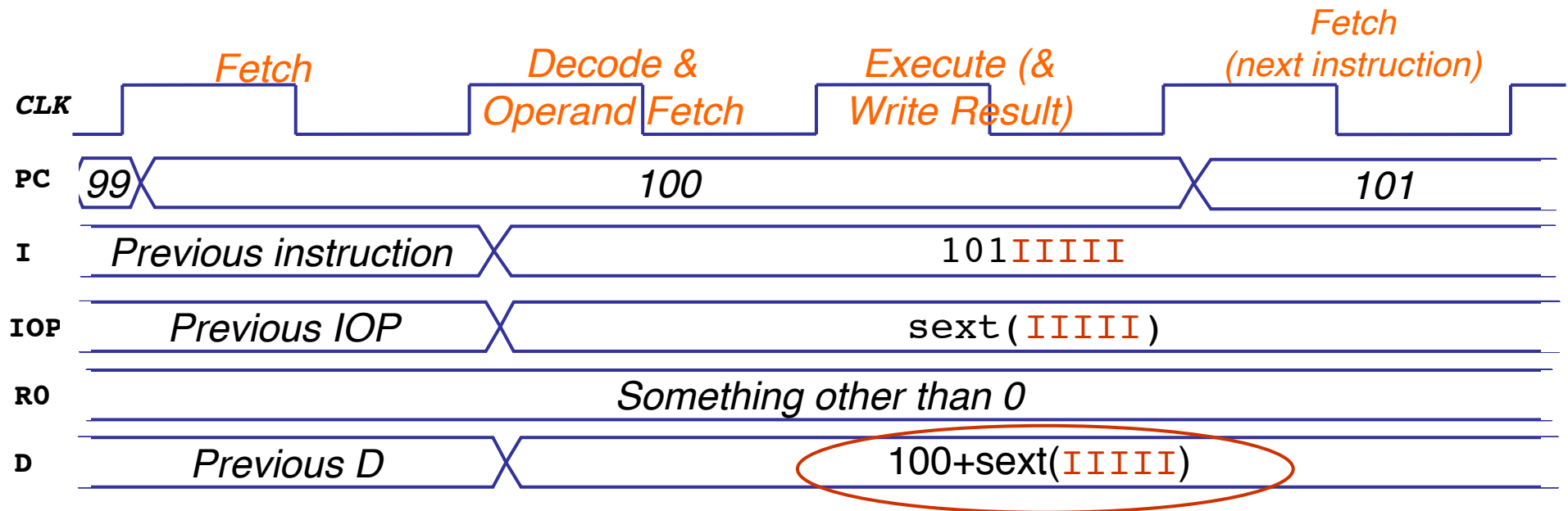

*May or may not
compute this:
**It doesn't matter
because it's not
used!***

Datapath: MOVR

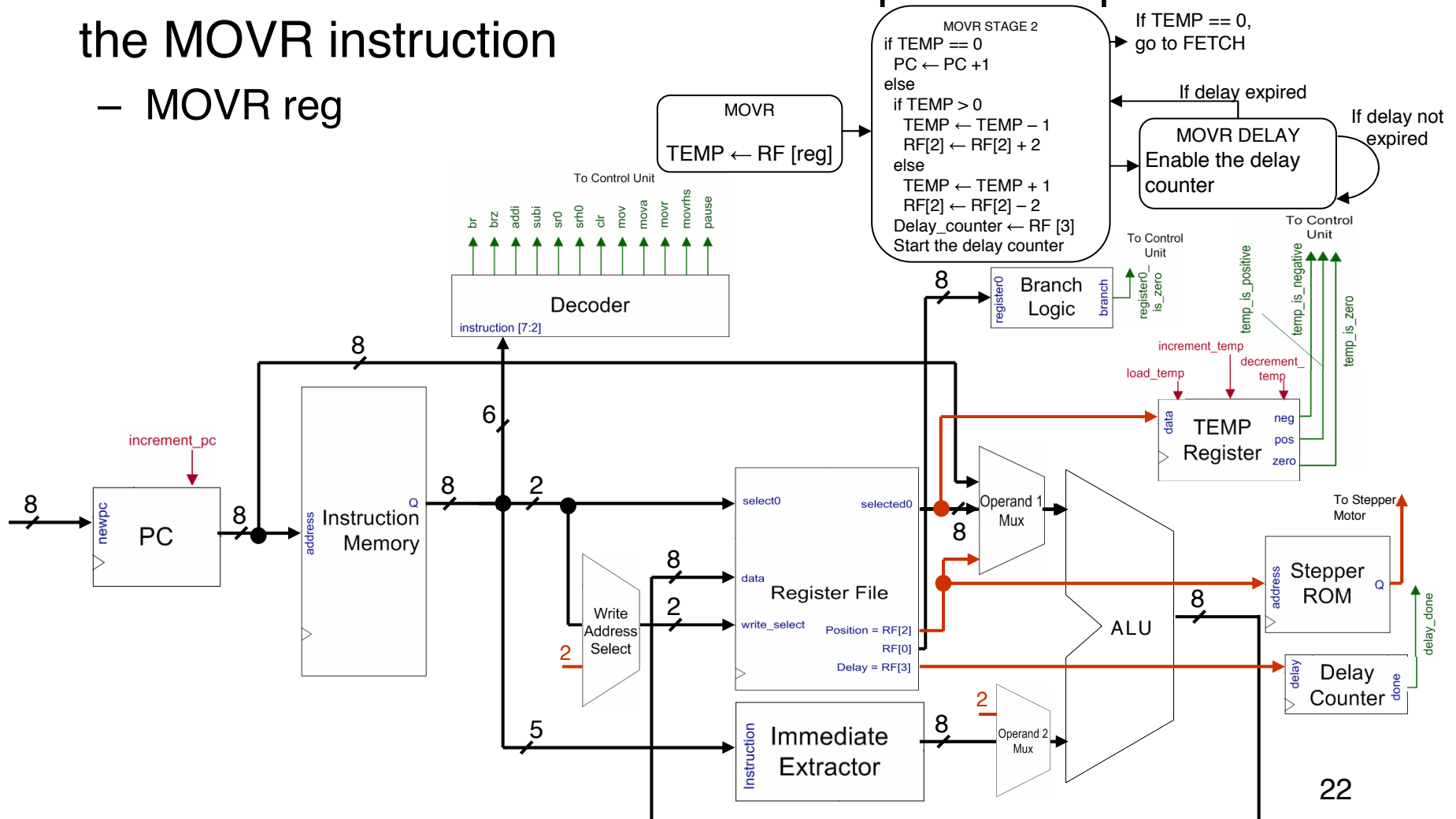- What do we need to add to the datapath to implement the MOVR instruction
 - MOVR reg




Stepper ROM

- How does stepper ROM work?
 - It contains eight 4-bit combinations
 - Correspond to the table of signals that need to be driven to a stepper motor to perform half-stepping
 - Lowest three bits of the position register are connected to the address port of this ROM
 - Consider what happens when the position is 6 and gets increased by 1 or 2?


Location	b ₃	b ₂	b ₁	b ₀
000	–	–	+	–
001	–	+	+	–
010	–	+	–	–
011	–	+	–	+
100	–	–	–	+
101	+	–	–	+
110	+	–	–	–
111	+	–	+	–

MOVR: Cycle By Cycle

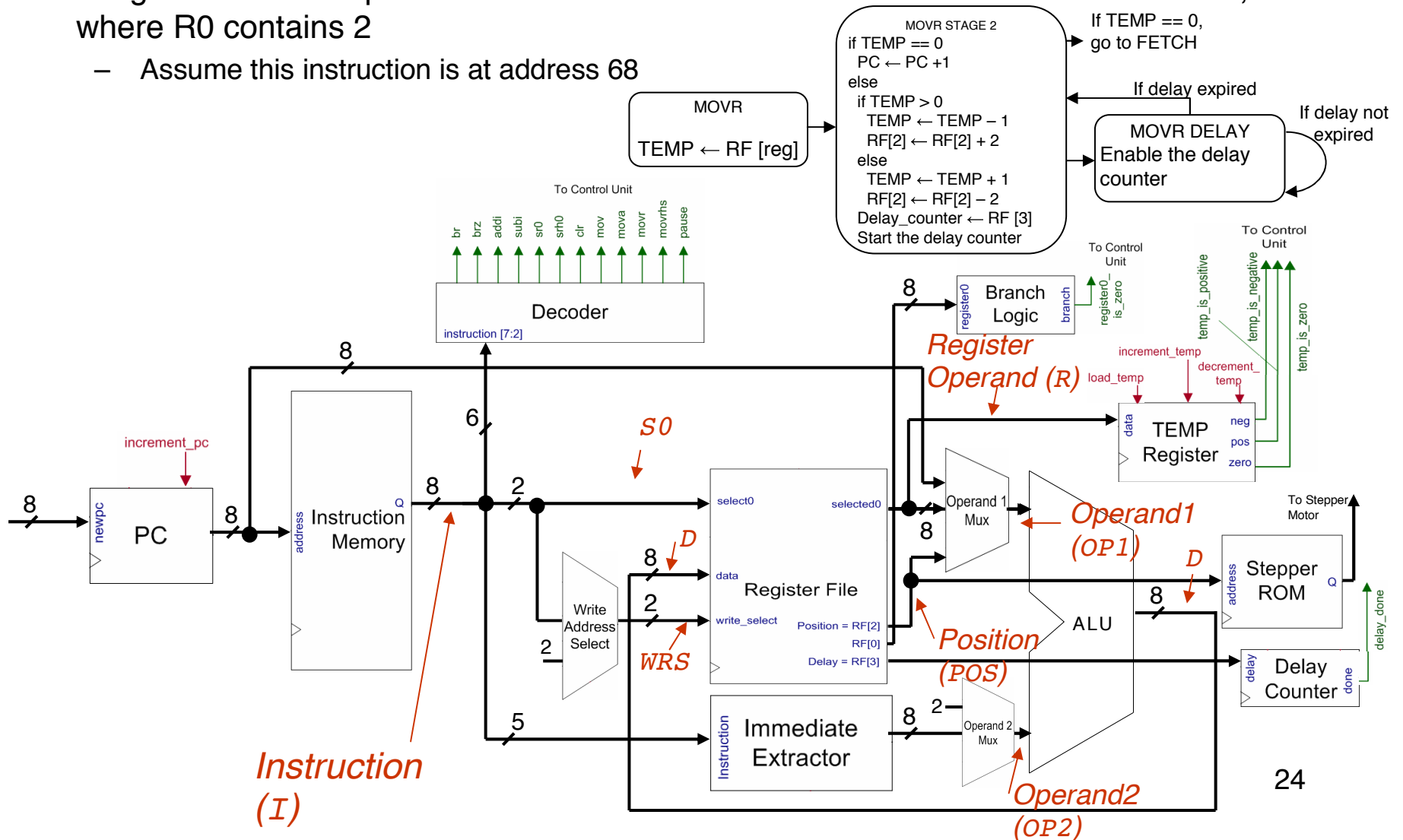- Imagine the current position is 16 and the instruction to be executed is **MOVR R0**, where R0 contains 2
 - Assume this instruction is at address 68




MOVR: Cycle by Cycle

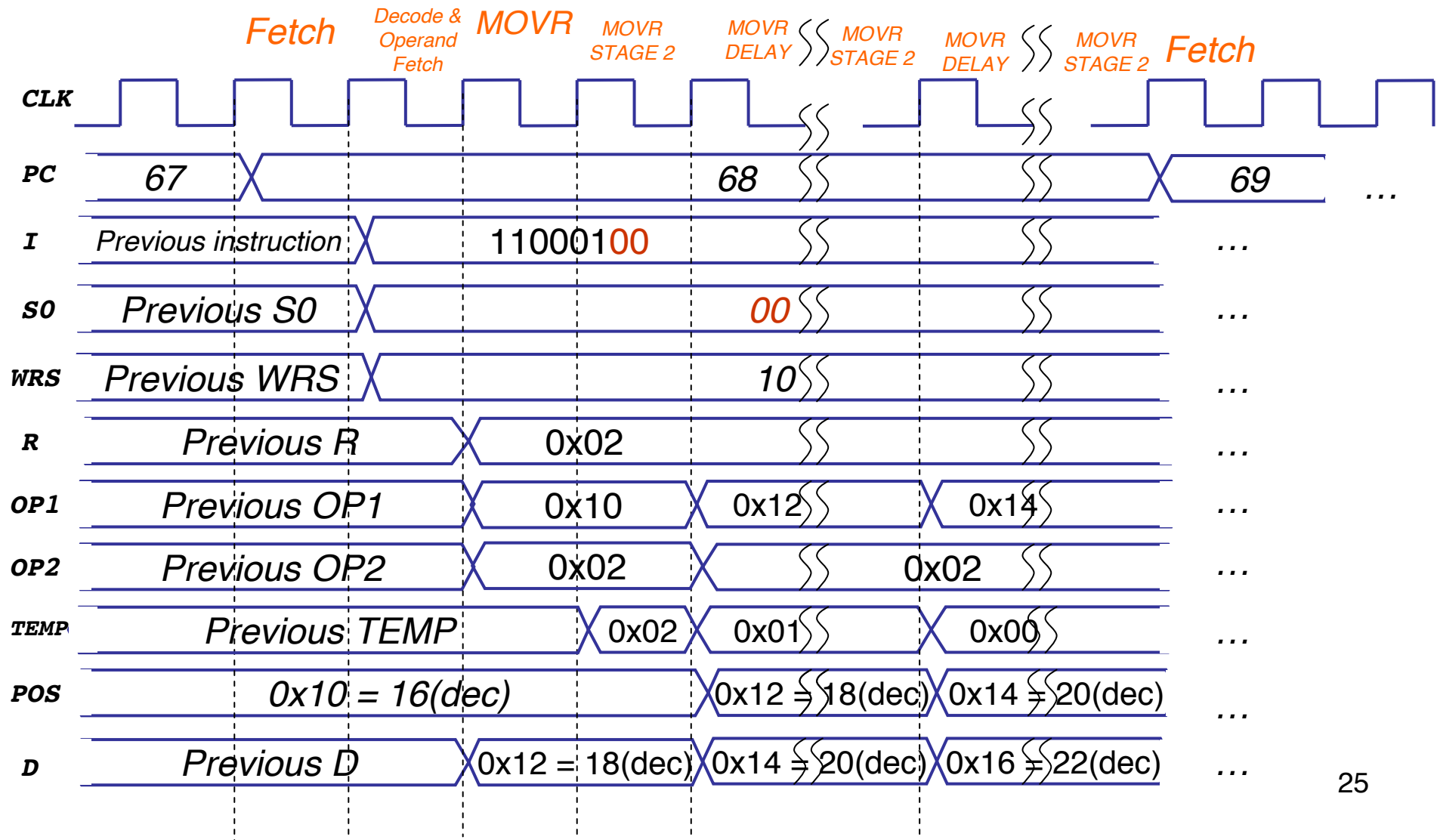

Finishing the Datapath

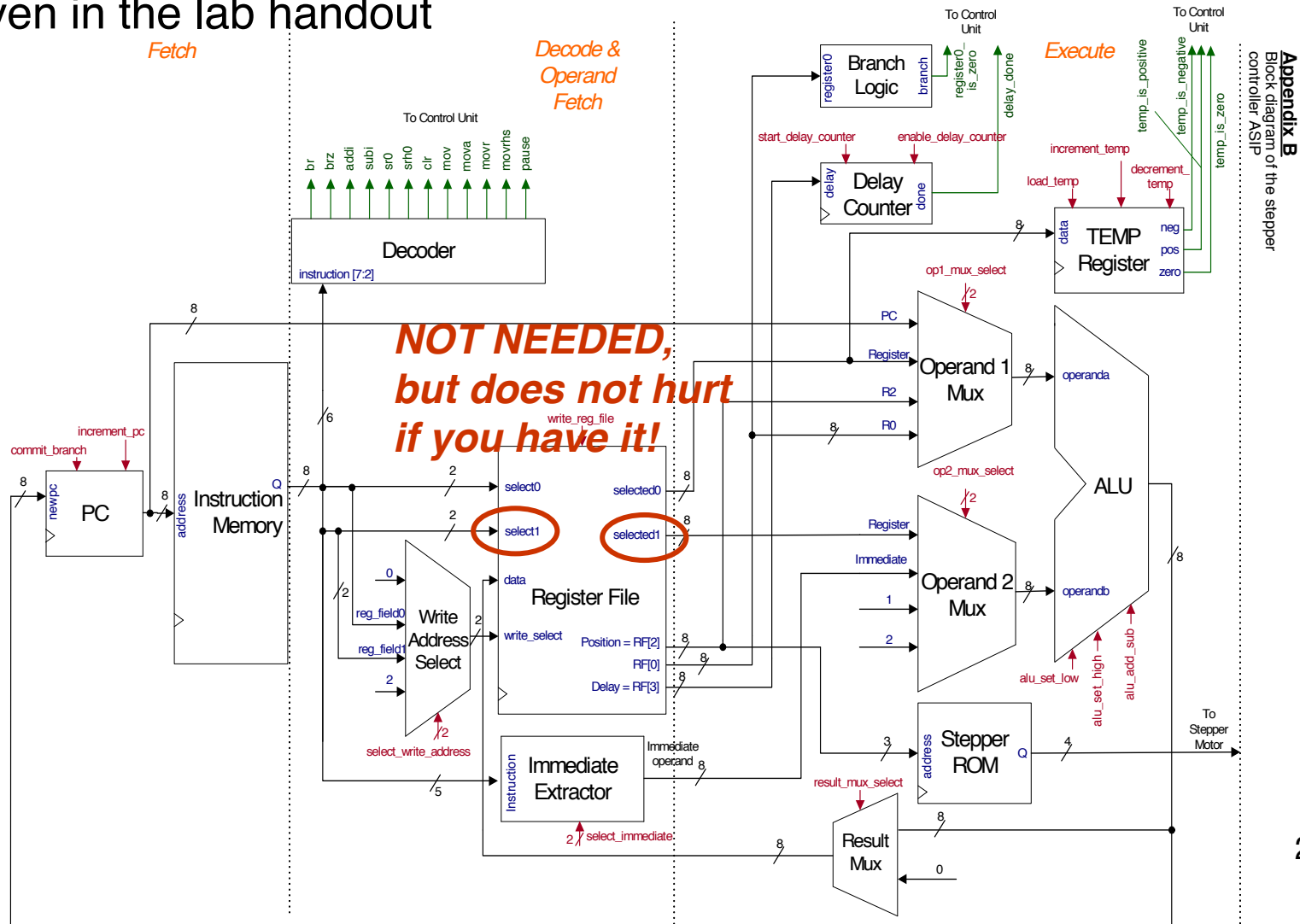- Continuing this procedure for all instructions, gets us to the datapath given in the lab handout




Control Signals

- The datapath includes many control signals, which need to be set appropriately to have the datapath perform the operations we want them to perform
- Analogy
 - Like a pipe system with many valves
 - We need to open correct valves to direct the fluid flow

Determining Control Signals


- To determine how the control signals should be set, we just read the FSMD and look at the datapath
 - Ask yourself: Which “valves” should be open to get the data to flow through the datapath to implement operations specified in the FSMD?
 - This can be done one state at a time
 - No need to worry how states interact; we took care of that when we were designing the FSMD

Control Signals: ADDI

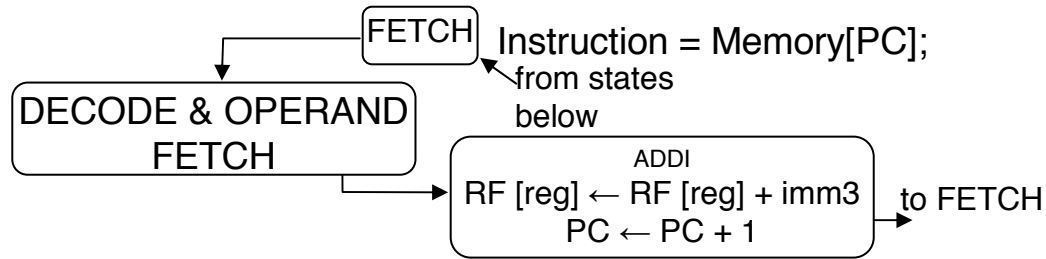

- **State: Fetch**
 - No special considerations (for any instruction)!
- **Decode and operand fetch**
 - No special considerations (for any instruction)!
 - You could set the **select_immediate** signal if it makes you happy 😊
 - Not needed until the next state, so not necessary to select it here because immediate extractor is combinational!

Control Signals: ADDI...

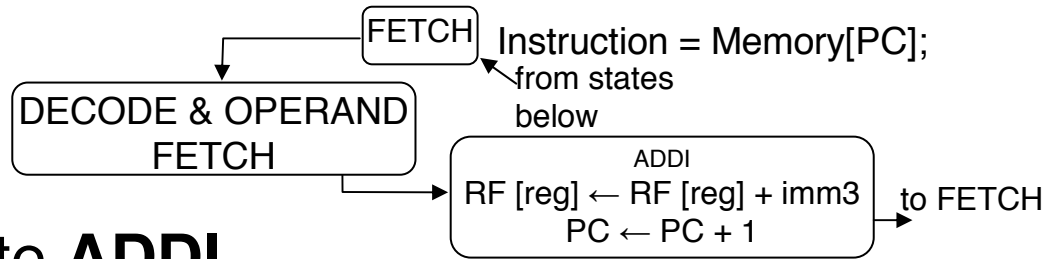

- State **ADDI**

- Select the two operands:
- Operand 1 is RF[reg] → **op1_mux_select** = 2'b01
- Operand 2 is immediate → **op2_mux_select** = 2'b01
- Immediate should be selected to be the 3-bit immediate → **select_immediate** = whichever_code_you_assigned
- Operation should be selected to be addition → **alu_add_sub** = 1'b0
- Result should come from ALU → **result_mux_select** = 1'b1
(providing that is how you implemented result mux)
- Result should be written to RF[reg] → **select_write_address** = 2'b01
- Results should indeed be written → **write_reg_file** = 1'b1
- PC should be incremented → **increment_pc** = 1'b1
- All other signals should be INACTIVE


Control Signals: BRZ

BRZ

```
if (RF[0] == 0)
    PC ← PC + sext(imm5)
else
    PC ← PC + 1
```


- State **BRZ**
 - if **register0_is_zero**
 - Select the two operands
 - Operand 1 is PC → **op1_mux_select** = 2'b00
 - Operand 2 is immediate → **op2_mux_select** = 2'b01
 - Immediate should be selected to be the 5-bit immediate → **select_immediate** = whichever_code_you_assigned
 - Operation should be selected to be addition → **alu_add_sub** = 1'b0
 - Result should be written to PC → **commit_branch** = 1'b1
 - else
 - PC should be incremented → **increment_pc** = 1'b1
 - All other signals should be INACTIVE

Control Signals: MOVR

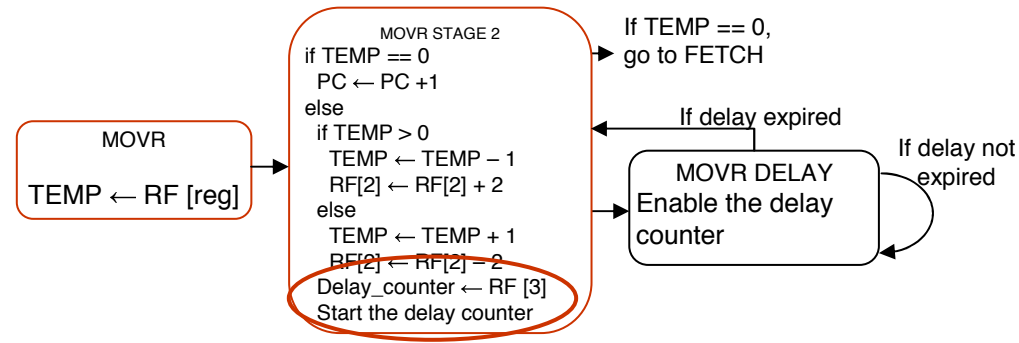


- State **MOVR**
 - RF[reg] is already connected directly to the TEMP register
 - Only need to enable the TEMP register → **load_temp** = 1'b1
- State **MOVR STAGE 2**
 - if **temp_is_zero**
 - **increment_pc** = 1'b1
 - else
 - Delay counter is already connected to RF[3]
 - Only need to enable it → **start_delay_counter** = 1'b1

Control Signals: MOVR...

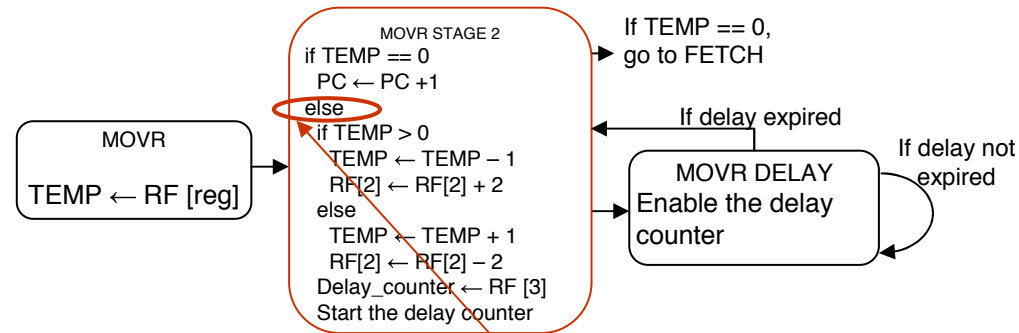


- State **MOVR STAGE 2 (continued)**
- Everything below is under the 'else' branch from the previous slide
 - if **temp_is_positive**
 - **decrement_temp** = 1'b1
 - Select the two operands for $RF[2] \leftarrow RF[2] + 2$
 - Operand 1 is $RF[2]$ → **op1_mux_select** = 2'b10
 - Operand 2 is constant 2 → **op2_mux_select** = 2'b11
 - Operation should be selected to be addition → **alu_add_sub** = 1'b0
 - Result should come from ALU → **result_mux_select** = 1'b1 (providing that is how you implemented result mux)
 - Result should be written to $RF[2]$ → **select_write_address** = 2'b11
 - Results should indeed be written → **write_reg_file** = 1'b1

Control Signals: MOVR...

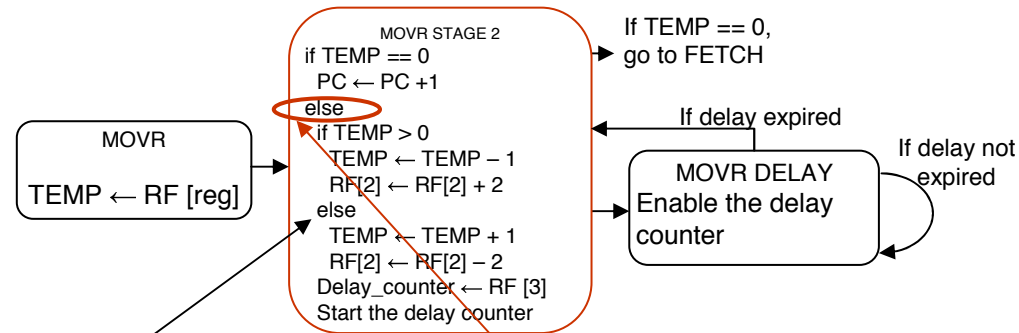

- State **MOVR STAGE 2 (continued)**
- Everything below is under the 'else' branch from the previous slide
 - else (i.e. if **temp_is_negative**)
 - **increment_temp** = 1'b1
 - Select the two operands for $RF[2] \leftarrow RF[2] - 2$
 - Operand 1 is $RF[2]$ → **op1_mux_select** = 2'b10
 - Operand 2 is constant 2 → **op2_mux_select** = 2'b11
 - Operation should be selected to be addition → **alu_add_sub** = 1'b1
 - Result should come from ALU → **result_mux_select** = 1'b1 (providing that is how you implemented result mux)
 - Result should be written to $RF[2]$ → **select_write_address** = 2'b11
 - Results should indeed be written → **write_reg_file** = 1'b1


Control Signals: MOVR...

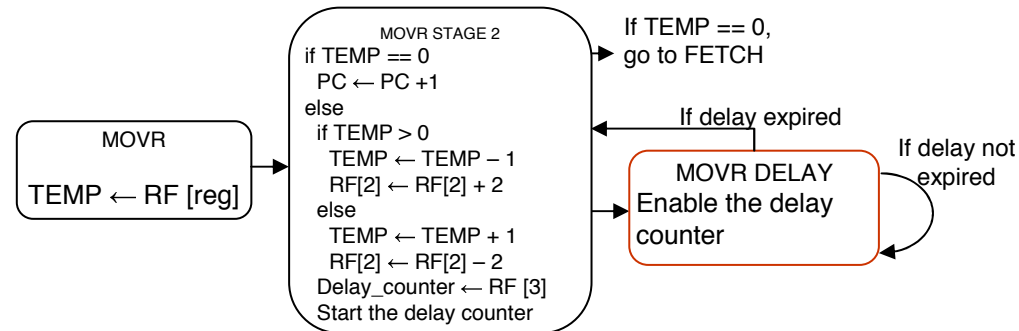

- State **MOVR DELAY**

- We only need to enable the delay counter
- **enable_delay_counter** = 1'b1
- All other signals should be INACTIVE
- For enable-type signals (e.g. load, write, ...), “inactive” means not active
- For other signals (such as select), inactive means that we do not really care what their values are
 - e.g. if nothing is being written to the register file, it doesn't matter which address the Write Address Select multiplexer is selecting

Simulating the Datapath

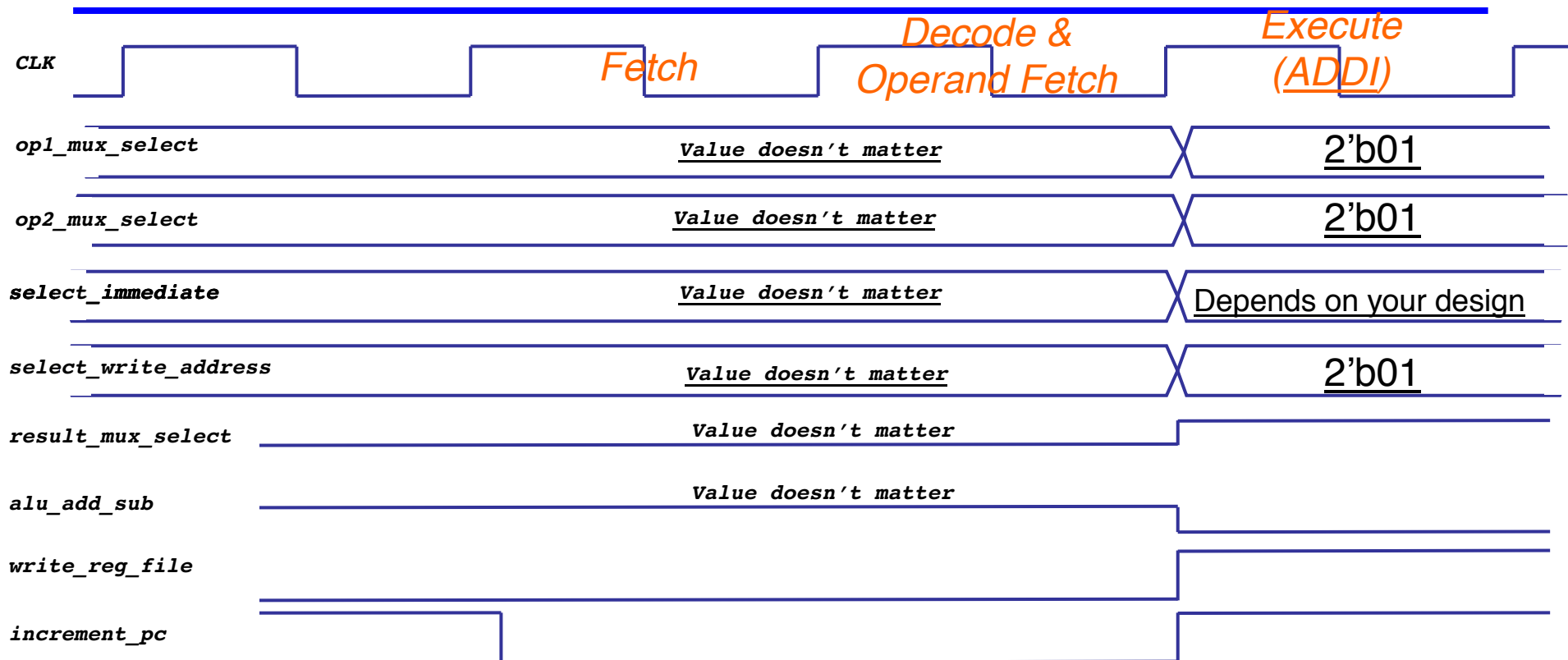

- Assert signals according to the scheme we have developed
 - You will have to put some instructions into the instruction memory to be able to simulate this

Simulating the Conditionals

- When we were devising the control signals to be asserted, we had conditions
 - e.g. State **BRZ**:
 - if `register0_is_zero`
 - ...
 - else
 - ...
- Since you will have full control of the processor, you will know whether the value in the register R0 is 0 or not
 - Therefore, you will know which signals to assert
 - You should test both cases, to make sure that datapath performs correct operation in both branches of the if statement

Simulating the Delay

- As stated in the lab handout, the delay in 1/100's of a second takes long to simulate
 - You should make your delay circuit parameterizable, so that its fundamental delay period can be reduced and the simulation does not take long
 - We will see shortly how this can be done
 - If you are not sure when the delay circuit will produce the **delay_done** signal, simulate it and see, then set other signals that should depend on it appropriately

Verilog: Combinational Logic

- Multiplexers should be easy to implement by now
- ALU and immediate extractor are simply some logic that computes something, followed by a multiplexer
 - One thing that might confuse you is the ALU, because it has more than 2 lines to encode 4 operations

ALU in Verilog

- Imagine you are implementing an ALU, which should compute 4 operations
 - $a+b$
 - $a-b$
 - $b-a$
 - $a*b$
- Imagine there are 3 control signals
 - multiply
 - compute_b_minus_a
 - add_sub
- Meaning of these control signals is as follows
 - If multiply is high, compute $a*b$
 - If compute_b_minus_a is high, compute $b-a$
 - If neither of the above is true
 - If add_sub is 0
 - Compute $a+b$
 - Else
 - Compute $a-b$

ALU in Verilog...

- In Verilog, we could describe this as follows

```
always @(*)
begin
    if (multiply == 1'b1)
        result = a * b;
    else if (compute_b_minus_a == 1'b1)
        result = b - a;
    else if (add_sub == 1'b0)
        // Add
        result = a + b;
    else
        // Subtract
        result = a - b;
end
```

Counter with Load

- We already know how to implement a counter (Lecture 10/11)

```
module counter_n_bit (input clk, input reset, output  
    reg [N-1:0] count);  
parameter N=8;
```

```
always @(posedge clk, posedge reset)
```

*Caution: This reset
is active high!*

```
begin
```

```
    if (reset)
```

```
        count <= {N{1'b0}};
```

```
    else
```

```
        count <= count + 1'b1;
```

```
end
```

```
endmodule
```

- What does this counter count?
 - Number of positive clock edges
- We want to add to it the ability to enable/disable the counting

Counter with Count Enable

- We already know how to implement a counter (Lecture 10/11)

```
module counter_n_bit (input clk, input reset, input cnt_en,  
    output reg [N-1:0] count);  
parameter N=8;  
  
always @(posedge clk, posedge reset)  
begin  
    if (reset)  
        count <= {N{1'b0}};  
    else  
        begin  
            if (cnt_en == 1'b1)  
                count <= count + 1'b1;  
        end  
    end  
end  
  
endmodule
```

- We want to add to it the ability to load an arbitrary value into the counter

Counter with Count Enable and Load


- We already know how to implement a counter (Lecture 10/11)

```
module counter_n_bit (input clk, input reset, input load, input [N-1:0]
    load_data, output reg [N-1:0] count);
parameter N=8;

always @(posedge clk, posedge reset)
begin
    if (reset)
        count <= {N{1'b0}};
    else
    begin
        if (load_data == 1'b1)
        begin
            count <= load_data;
        end
        else
        begin
            if (cnt_en == 1'b1)
                count <= count + 1'b1;
        end
    end
end
endmodule
```

Delay Counter

 - Delay Counter is the only somewhat tricky part of the datapath



- Delay counter loads the amount of delay when the **start_delay_counter** is high
- When the **enable_delay_counter** is high, the counter counts down, until it reaches 0
 - It asserts **delay_done** signal once it reaches 0

Delay Counter Design

- Since counters count clock edges, and our clock's frequency is 50 MHz, we cannot directly count the time intervals specified in 1/100's of a second
- Instead, you should apply the technique that you used when programming AVR's timer
- Employ 2 counters
 - Have one counter that tells you each time a 1/100 of a second has passed
 - The other counter can be loaded with the desired delay, and decremented (i.e. decreased by 1) every time the first counter indicates that a 1/100 of a second has passed
 - Once this other counter reaches 0, the desired interval has passed

Delay Counter Example

- For simplicity of the example, imagine the first counter has period of 3 clock cycles

Counter 1

0

1

2

0

1

2

...



Counter 2

5

4

3

...

  

Modulo-N counter

- We know that binary counters are normally modulo 2^n , where n is the number of bits
- What if we want a counter that counts modulo arbitrary number N , which is not a power of 2?

Modulo-312 counter

- Count: 0, 1, 2, ..., 310, 311, 0, 1, 2, ...
- 312 can be stored in 9 bits

```
always @(posedge clk)
begin
    if (start == 1'b1)
        count <= 9'b0;
    else if ((cnt_enable == 1'b1) && (count < 9'd311))
        count <= count + 1'b1;
    else if ((cnt_enable == 1'b1) && (count == 9'd311))
        count <= 9'b0;
end
```