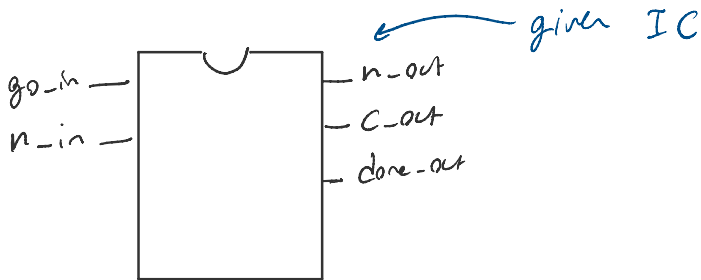


→ collatz algorithm

$$C_{n+1} = \begin{cases} C_n/2 & \text{if } n\%2=0 \\ 3(C_n)+1 & \text{if } n\%2=1 \end{cases}$$

→ collatz conjecture; if you perform collatz algorithm on a number enough, you will reach 1



Algorithm design


```

while (1) {
    while (!go_in);
    n = n_in;
    C = 0;
    while (n > 1) {
        if (n % 2 == 0) {
            n = n / 2;
        } else {
            n = 3 * n + 1;
        }
        count++;
    }
    done_out = 1;
}
    
```


Data path

optimization

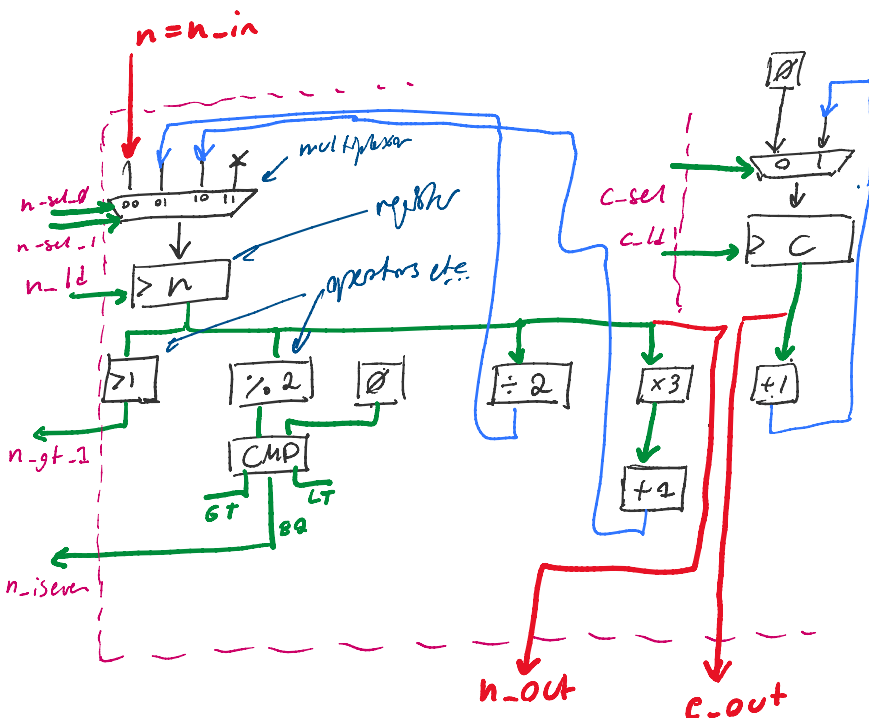
→ typically: boolean signals  
are control signals  
→ floats & integers data



FSM

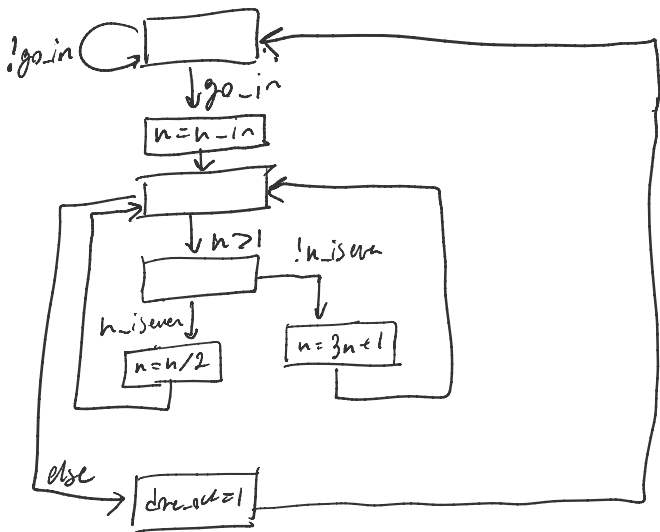

ver 2

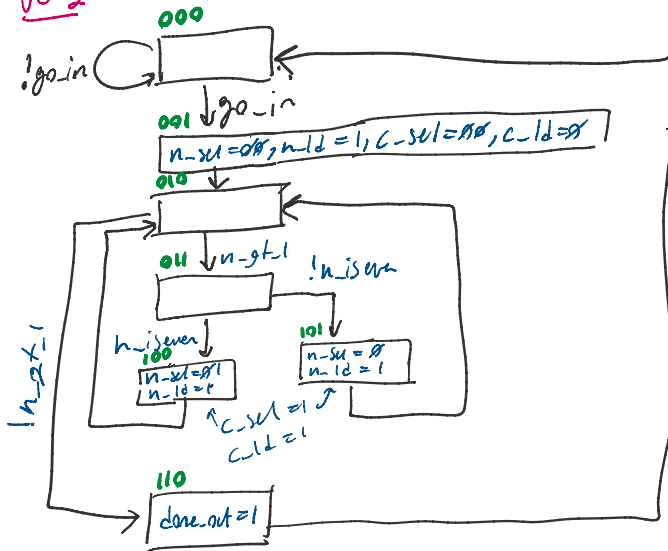

1 bit  
8 bits  
3-bit  
state  
register

State table

X = inputs don't care  
\* = output don't care

need eqns for those

new state  
register values

state register		n_sel	c_sel	n_ld	c_ld	done_out	n > 1	n is even	I <sub>2</sub> I <sub>1</sub> I <sub>0</sub>
Q <sub>2</sub> Q <sub>1</sub> Q <sub>0</sub>	go_in								
000	0	XX	X	0	0	0	*	*	000
001	1	XX	X	0	0	0	*	*	001
010	1	00	0	1	1	0	*	*	010
011	1	XX	X	0	0	0	0	*	110
100	1	XX	X	0	0	0	1	*	011
101	1	XX	X	0	0	0	*	*	101
110	1	01	1	1	1	0	*	*	100
		10	1	1	1	0	*	*	010
		XX	X	0	0	1	*	*	000

Eqns

$$done\_out = Q_2 Q_1 \bar{Q}_0$$

$$n\_ld = c\_ld = (Q_2 + Q_0) \bar{Q}_1$$

$$c\_sel = \bar{Q}_2 \bar{Q}_1 Q_0$$

Q<sub>2</sub> Q<sub>1</sub> Q<sub>0</sub>  
001  
100  
101