

Example for Drain Current

Problem 1: A JFET has the following parameters : $I_{DSS}=5\text{ mA}$ and $V_{GS(off)} = -6\text{ V}$. Find I_D for $V_{GS} = -2.5\text{ V}$.

Example for Drain Current

Problem 2: Determine the transconductance of the given FET when the gate to source voltage changes from -3.5 V to -3.0 V and the drain current changes from 3 mA to 4 mA .

Example for V_{DS} and V_{GS}

Problem 3: Determine V_{DS} and V_{GS} for the given JFET when $I_D=5$ mA and $V_{DD}=15$ V.

Example for I_D and V_{GS}

Problem 4: Determine I_D and V_{GS} for the given JFET if $V_D=7$ V.

Example for E-MOSFET Drain Current


Problem 1: The datasheet for an E-MOSFET gives $I_{D(ON)} = 500 \text{ mA}$ (minimum) at $V_{GS} = 10 \text{ V}$ and $V_{GS(th)} = 1 \text{ V}$. Determine the drain current for $V_{GS} = 5 \text{ V}$.

Example for D-MOSFET Drain Current

Problem 2: For a certain D-MOSFET, $I_{DSS} = 10 \text{ mA}$ and $V_{GS(off)} = -8 \text{ V}$. Is this an n-channel or a p-channel? Calculate I_D at $V_{GS} = \pm 3 \text{ V}$.

Example for Drain Current and V_{DS}

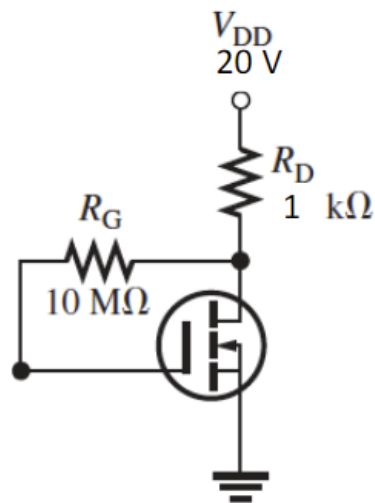Problem 3: The datasheet for this E-MOSFET shows that $I_D = 10 \text{ mA}$ when $V_{GS} = V_{DS}$. Find I_D and V_{DS} .



Example for Drain to Source Voltage

Problem 4: Determine the drain-to-source voltage in the given circuit. The MOSFET datasheet gives $V_{GS(off)} = -8\text{ V}$ and $I_{DSS} = 12\text{ mA}$.

